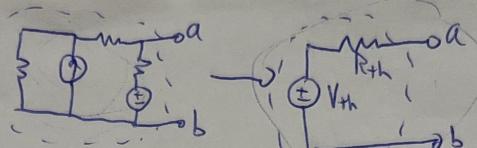



Thevenin

Goal:




?

Process:

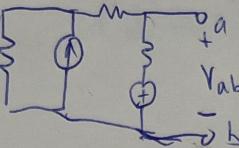

① nodal

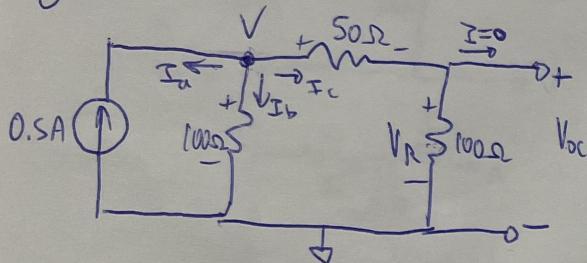

recognize


- $V_{oc} = V_R = V_{th}$
- $I = 0A$

• Find V_{th} → Calculate V_{ab} (nodal, KVL, divider, etc.)

• Find R_{th} → Calculate equivalent resistance

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

②

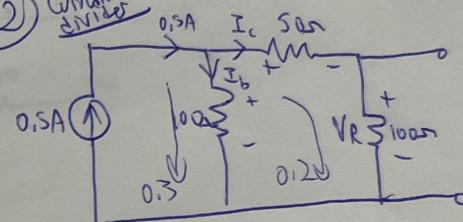

$$V_R = I_c \cdot 100$$

$$I_c = 0.5 \cdot \frac{100}{100 + 150} = 0.2A$$


~~$$V_R = 0.2 \cdot 100 = 20V$$~~

~~WRONG~~

$$V_R = 0.12 \cdot 100 = 12V$$

$$V_R = I_c \cdot 100 \Omega$$

$$V_R = 20V = V_{oc} = V_{th}$$




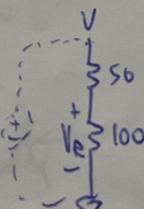


OR

$$V_R = V \cdot \frac{100}{100 + 50} = 20V$$


R_{th}

① equiv.
resistance

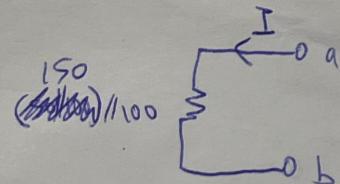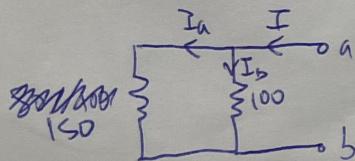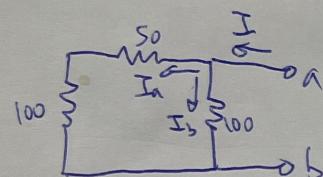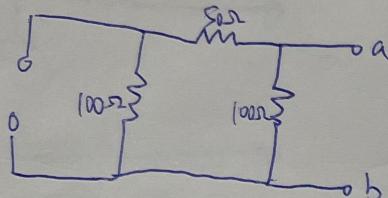


$$R_{th} = 60 \Omega$$

$$② R_{th} = \frac{V_{th}}{I_{sc}}$$

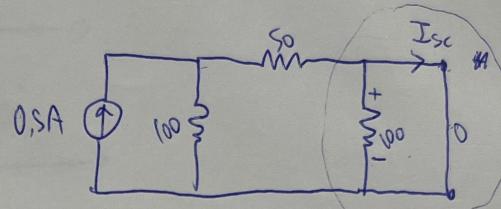
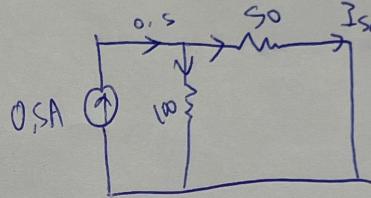
$$R_{eq} = \frac{100 \cdot 0}{100 + 0} = 0$$




$$I_{sc} = 0,5 \cdot \frac{100}{S_0 + 100} = \cancel{0,5} \cdot 0,3 A$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \cancel{\frac{20}{0,5}} = \frac{20 V}{0,3 A} = 60 \Omega$$


R_{th}

Norton

therefore in eq.

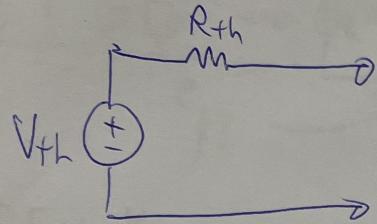

Norton eq.

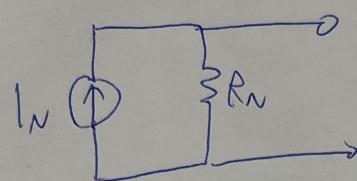


$$R_{th} = R_N$$

$$V_{th} = I_N \cdot R_N$$

$$I_N = \frac{V_{th}}{R_{th}}$$

Thevening

Goal

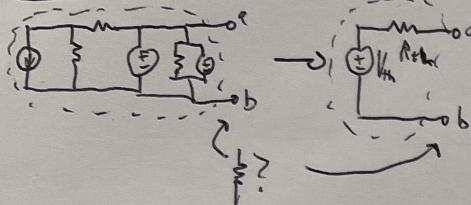

① Find V_{th}


$$\begin{aligned} & \rightarrow V_{th} = V_a - V_b \\ & \rightarrow \text{Calculate } V_{ab} = V_{th} = V_a - V_b \\ & \rightarrow V_{th} = I_{sc} \cdot R_{th} \end{aligned}$$

② Find R_{th}

→ equivalent R
"looking into circuit"

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

Dependent Sources

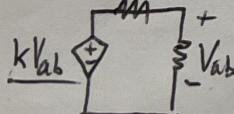

$k = \text{constant}$


① Normal analysis. (kVL, kVB , nodal)
dividers

② Substitution equation

rewrite dependent value

$$\frac{V_R}{s} = \frac{V - e}{s}$$

$$10 = e - 0$$

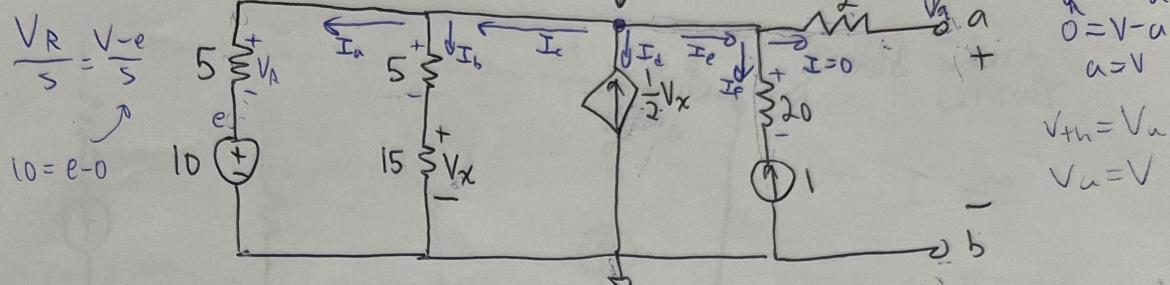

$$\begin{aligned} V_R &= IR = 0 \\ V_A &= 0 \\ V &= V_A \\ 0 &= V_A \\ a &= V \\ V_{th} &= V_a \\ V_a &= V \end{aligned}$$

Goal: Find $V_{th}, R_{th} \rightarrow V_{th} = V_{ab} = V_a - V_b = V$ ★ ONLY true when a-b is open circuit

$$V_b = 0V$$

$$\frac{V}{V_x} = A$$

$$I_c + I_d + I_e = 0$$

$$I_a + I_b - \frac{1}{2}V_x + I_f = 0$$


$$\frac{V - 10}{5} + \frac{V - 0}{20} - \frac{1}{2}V_x - 1 = 0 \quad \text{lea., 2 unk. because of dependent source}$$

$$\frac{V - 10}{5} + \frac{V}{20} - \frac{1}{2}\left(V \cdot \frac{3}{4}\right) - 1 = 0 \quad \text{lea., 1 unk}$$

$$V\left(\frac{1}{5} + \frac{1}{20} - \frac{3}{8}\right) = \frac{10}{5} + 1$$

$$V = -24V = V_{th}$$

Write V_x in terms of V

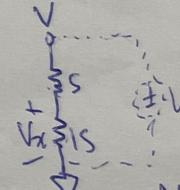


$$V_x = V \cdot \frac{1}{5}$$

~~23/28~~

$$V_x = V \cdot \frac{3}{4}$$
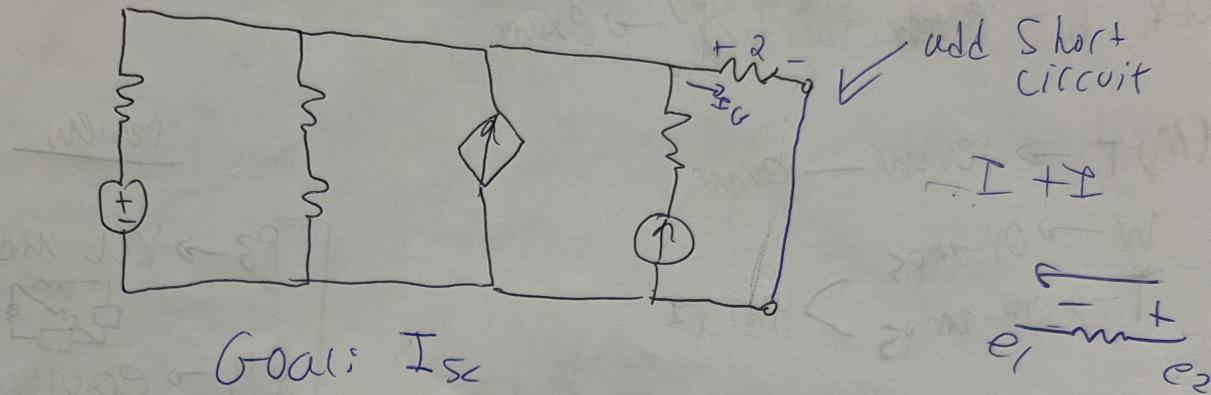
$$R_{th} \rightarrow = \frac{V_{th}}{I_{sc}}$$




add Short circuit

$$I + I$$

A diagram showing a short circuit connection between two nodes, labeled e_1 and e_2 .

$$I_o = \frac{V_{-0}}{2} = \underline{4A} = I_{sc}$$

$V=8V$

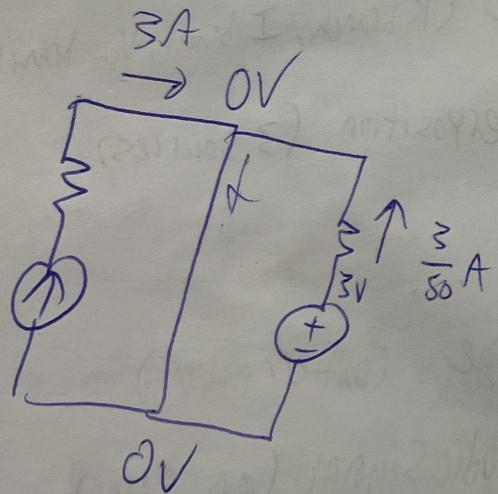

$$\Rightarrow R_{th} = \frac{V_{th}}{I_{sc}} = \frac{-24}{4} = -6\Omega$$

