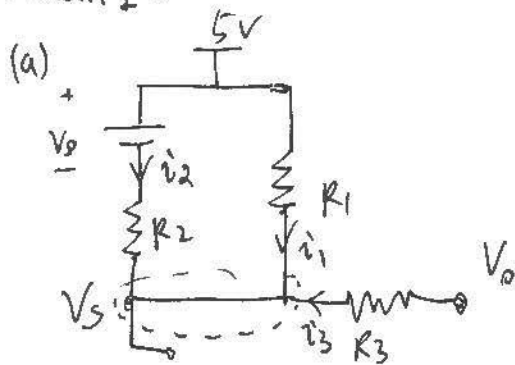


problem 1.



At the boundary. $V_D = V_{th} = 0.7V$. $i_D = i_2 = 0$

KCL:
$$50: V_S = 5 - 0.7 - \underbrace{i_2 \cdot R_2}_{\rightarrow 0} = 4.3 (V)$$

$$i_2 + i_1 + i_3 = 0$$

$$0 + \frac{5 - V_S}{R_1} + \frac{V_0 - V_S}{R_3} = 0$$

(b) Suppose: Diode "ON" when $V_S \leq 4.3V$.

KCL:
$$i_2 + i_1 + i_3 = 0$$

$$\frac{5 - 0.7 - V_S}{R_2} + \frac{5 - V_S}{1.4k} + \frac{V_0 - V_S}{R_3} = 0 \Rightarrow \frac{4.3 - V_S}{3k} + \frac{5 - V_S}{1.4k} + \frac{V_0 - V_S}{2k} = 0$$

$$\Rightarrow V_0 = \frac{13V_S - 42.04}{4.2}$$

Check: $i_D = i_2 = \frac{4.3 - V_S}{3k} \geq 0 \Rightarrow \text{"ON"}$



Assume: Diode "OFF" when $V_S > 4.3V$.

$$i_1 + i_3 = 0$$

$$\frac{5 - V_S}{1.4k} + \frac{V_0 - V_S}{2k} = 0 \Rightarrow$$


$$V_0 = \frac{3.4V_S - 10}{1.4}$$

check. $V_0 = 5 - i_D \cdot R_3 - V_S$
 $< 5 - i_D \cdot R_3 - 4.3$
 $= 0.7 - i_D \cdot R_3$
 $\leq V_{th}$. "OFF"

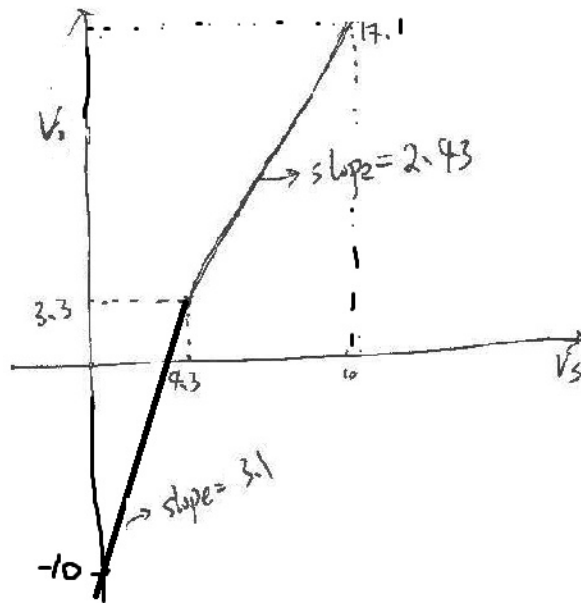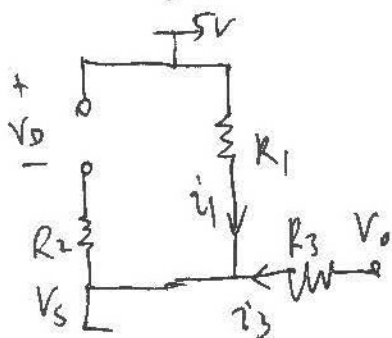

Problem 2.

① Assume. D_1, D_2 Both "ON"

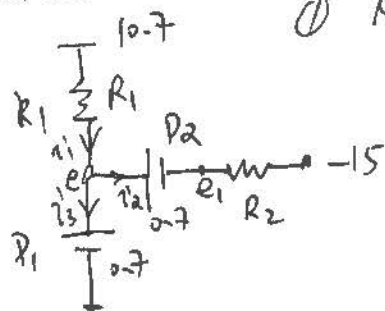

$$e = 0.7; \quad e_1 = 0.$$

$$i_1 = \frac{10.7 - e}{R_1} = \frac{10.7 - 0.7}{10k} = 1mA$$

$$i_2 = \frac{e_1 - (-15)}{R_2} = \frac{0 + 15}{10k} = 1.5mA$$


KCL:

$$i_1 - i_2 - i_3 = 0$$

$$i_3 = i_1 - i_2 = 1 - 1.5mA = -0.5mA.$$

So the Assumption of D_1 "ON" \times

② Assume D_1 "OFF" D_2 "ON"

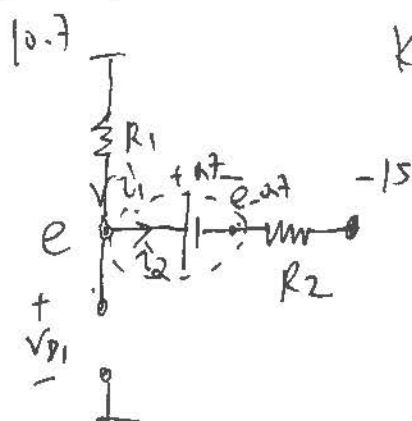

KCL @ supernode:

$$i_1 - i_2 = 0$$

$$\frac{10.7 - e}{R_1} - \frac{e - 0.7 - (-15)}{R_2} = 0$$

$$\frac{10.7 - e}{10k} - \frac{e - 0.7 + 15}{10k} = 0$$

$$10.7 - e - e - 14.3 = 0$$

$$\Rightarrow e = -1.8(V)$$

$$i_1 = \frac{10.7 - (-1.8)}{10k} = 1.25mA; \quad i_2 = \frac{e - 0.7 - (-15)}{R_2} = \frac{-1.8 - 0.7 + 15}{10k}$$

$$i_3 = 0$$

$$= 1.25mA$$

check: $V_{D1} = e - 0 = -1.8 - 0 = -1.8 < V_{th} \checkmark$

Problem 3:

(a): Assume Diode = "ON". Then $V_x = 2 - 0.7 = 1.3V$

Then NMOS:

$$V_{GS} = V_{IN} - 0 = 2 - 0 = 2 > V_T \Rightarrow \text{"ON"}$$

$$V_{DS} = V_x - 0 = 1.3 > V_{GS} - V_T = 2 - 1 = 1(V)$$

\Rightarrow Saturation:

$$\text{So: } i_{DS} = \frac{k}{2} (V_{GS} - V_T)^2 = \frac{5 \times 10^{-3}}{2} (2 - 1)^2 = 2.5 \text{ mA}$$


$$\text{KCL } \textcircled{a} V_x: i_D + i_L - i_{DS} = 0$$

$$\Rightarrow i_D = i_{DS} - i_L$$

$$= 2.5 \text{ mA} - \frac{5 - 1.3}{10 \text{ k}}$$

$$= 2.5 \text{ mA} - 0.37 \text{ mA} > 0$$

Assumption "ON" ✓

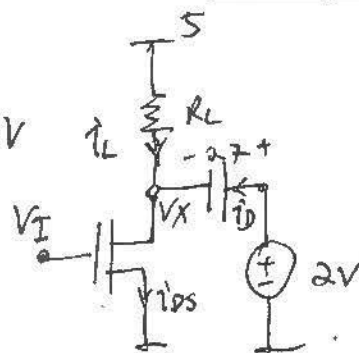

(b). Assume Diode = "ON". $V_x = 2 - 0.7 = 1.3V$.

$$\text{NMOS: } V_{GS} = V_{IN} - 0 = 3 - 0 = 3 > V_T \Rightarrow \text{"ON"}$$

$$V_{DS} = V_x - 0 = 1.3 < V_{GS} - V_T = 3 - 1 = 2$$

\Rightarrow "Triode"

$$R_{on} = \frac{1}{k(V_{GS} - 1)} = \frac{1}{5 \times 10^{-3} (3 - 1)} = 0.1 \text{ k}$$


$$i_{DS} = \frac{V_x - 0}{R_{on}} = \frac{1.3 \text{ V}}{0.1 \text{ k}} = 13 \text{ mA}, \quad i_L = \frac{5 - V_x}{R_L} = \frac{5 - 1.3 \text{ V}}{10 \text{ k}} = 0.37 \text{ mA}$$

KCL $\textcircled{a} V_x$:

$$i_x + i_L - i_{DS} = 0$$


$$\Rightarrow i_x = i_{DS} - i_L = 13 - 0.37 \text{ mA} = 12.63 \text{ (mA)}$$

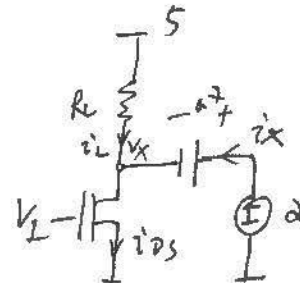Check $i_D = i_x = 12.63 \text{ mA} > 0$, Diode = "ON" ✓



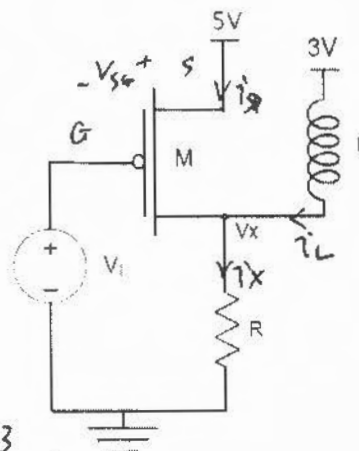Problem 4 (5 pt)

In the circuit below, $R = 3 \Omega$, $L = 1 \text{ H}$. V_1 has been at 5 V for a long time. At $t = 0$, V_1 changes from 5 V to 0 V. Find $V_x(t)$ for $t > 0$. $K_p = \frac{1}{12} \text{ A/V}^2$, $V_{TP} = -1 \text{ V}$. (You need to justify the region of M in SCS model).



When $t > 0$, $V_{SG} = 5 - 0 > |V_{TP}|$ "ON"

finding $V_x(0^+)$ in order to determine transistor region at the very beginning

① at $t = 0^+$, Assume "saturation"


$$i_{SD} = \frac{k}{2} (V_{GS} - V_{TP})^2 = \frac{1}{2} \times \frac{1}{12} \times (5 - 1)^2 = \frac{3}{4} \text{ (A)}$$

KCL @ V_x

$$i_{SD}(0^+) + i_L(0^+) - i_X(0^+) = 0$$

$$\frac{3}{4} \text{ A} + \underbrace{i_L(0^+)}_{= i_L(0^-)} - \frac{V_x(0^+)}{3} = 0$$

find $i_L(0^-)$: when $t < 0$: $V_{SG} = 0 - 0 = 0 < |V_{TP}| \Rightarrow$ "OFF"

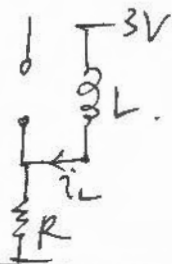

At steady state:

$$i_L = \frac{3}{R} = 1 \text{ (A)} = i_L(0^-)$$


$$\text{So: } V_x(0^+) = 3 \times \left(\frac{3}{4} + i_L(0^-) \right) = 3 \times \left(\frac{3}{4} + 1 \right) = 3 \times 1.75 = 5.25 \text{ (V)}$$

$$V_{SD}(0^+) = 5 - V_x = 5 - 5.25 = -0.25 < V_{SG} - |V_{TP}|$$

Assumption of "saturation" ~~X~~

So Assume: $t = 0^+$, PMOS = Triode

$$R_{ov} = \frac{1}{k(V_{SG} - |V_{TP}|)} = \frac{1}{\frac{1}{2} \times (5-1)} = 3(\Omega)$$

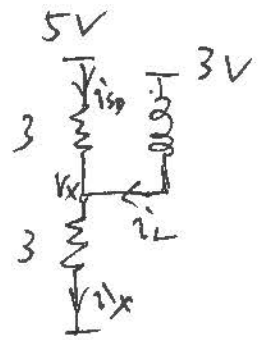

$$i_{SD}(0^+) + i_L(0^+) - i_X(0^+) = 0$$

$$\frac{5-V_X}{3} + i_L(0^+) - \frac{V_X}{3} = 0$$

$$\hookrightarrow i_L(0^+) = 1 \text{ A (Based on previous Analysis)}$$

$$\Rightarrow \frac{5-V_X}{3} + 1 - \frac{V_X}{3} = 0 \Rightarrow V_X(0^+) = 4 \text{ V}$$

$$\text{check: } V_{SD}(0^+) = 5 - 4 = 1 < V_{SG} - |V_{TP}| \Rightarrow \text{"Triode"} \checkmark$$

For $t > 0$, Continue to Assume PMOS = Triode

$$i_{SD} + i_L - i_X = 0$$

$$\frac{5-V_X}{3} + i_L(0^+) + \frac{1}{1} \int (3-V_X) dt - \frac{V_X}{3} = 0$$

$$\text{Diff: } -\frac{1}{3} \frac{dV_X}{dt} + (3-V_X) - \frac{1}{3} \frac{dV_X}{dt} = 0$$

$$-\frac{2}{3} \frac{dV_X}{dt} - V_X = -3$$

$$V_X = 3 + k \cdot e^{-\frac{3}{2}t}$$

$$\text{We know } V_X(0^+) = 4 \text{ V}$$

$$\text{So: } k = 1 \quad \therefore V_X = 3 + e^{-\frac{3}{2}t}$$

check: when $t > 0$:

$$V_{SD} = 5 - V_X = 5 - (3 + e^{-\frac{3}{2}t}) = 2 - e^{-\frac{3}{2}t} < 2 < V_{SG} - |V_{TP}| = 4$$

= "Triode" \checkmark