

# ECE124: Discussion

Discussion #8

Yeonsik Noh, PhD

3.21 Draw (a) the multiple level NAND circuit for the following expression and (b) repeat (a) for a NOR circuit.


$$w(x + y + z) + xyz$$

$$F(w, x, y, z) = w(x + y + z) + xyz$$


$$F' = \{ w(x + y + z) + xyz \}'$$

$$\textcircled{1} \{ wx + wy + wz + xyz \}'$$
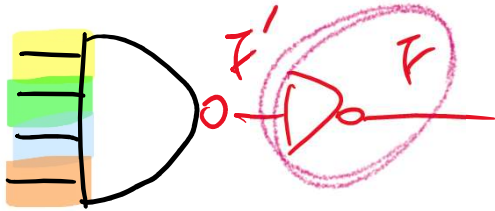
$$F' = (wx)' \cdot (wy)' \cdot (wz)' \cdot (xyz)'$$


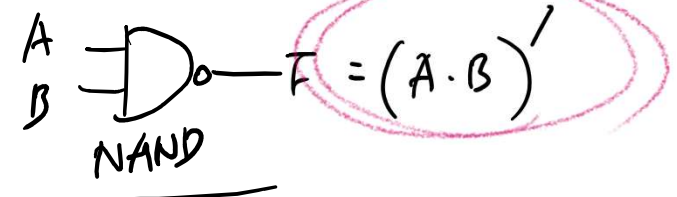
$$(F')' = \{ (wx)' \cdot (wy)' \cdot (wz)' \cdot (xyz)' \}'$$



$$\textcircled{2} F' = \{ w \cdot (x' \cdot y' \cdot z')' + xyz \}'$$

$$= \{ w \cdot (x' \cdot y' \cdot z')' \}' \cdot (xyz)'$$

$$(F')' = \left[ \{ w \cdot (x' \cdot y' \cdot z')' \}' \cdot (xyz)' \right]'$$

3.21 (b) repeat (a) for a NOR circuit.



$$w(x + y + z) + xyz$$

$$F' = \{ w(x + y + z) + xyz \}'$$

$$= \{ w(x + y + z) \}' \cdot (xyz)'$$


$$F = (F')' = \left[ w' + (x + y + z)' \right] \cdot (x' + y' + z')$$
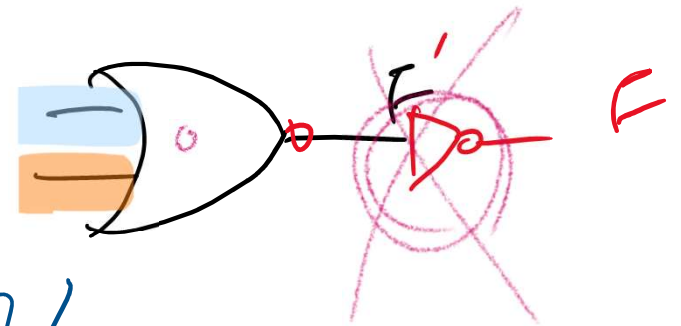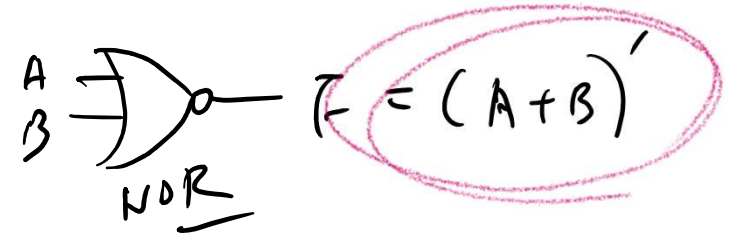
$$F = \left[ \left\{ w' + (x + y + z)' \right\}' + (x' + y' + z')' \right]'$$



3.26 With the use of maps, find the simplest sum-of-products form of the function  $F = fg$ , where

$$f = abc' + c'd + a'cd' + b'cd'$$

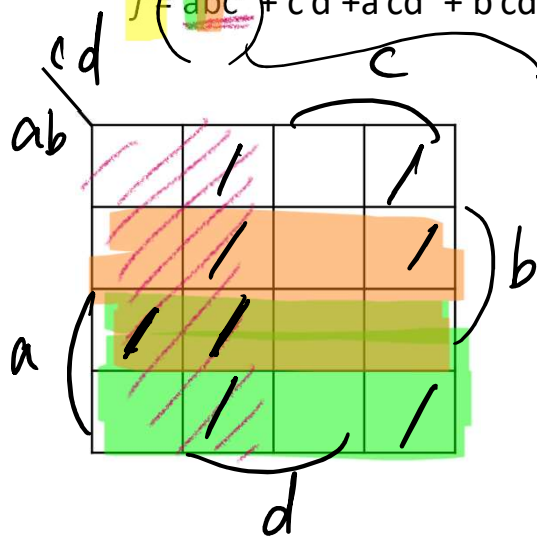

$$\begin{array}{cccc} abc'd & & & \\ 1100 & & & \\ 1101 & & & \end{array}$$


$$g = (a + b + c' + d')(b' + c' + d)(a' + c + d')$$

$$\begin{array}{cccc} 0 & 0 & 1 & 1 \\ \hline & & & \end{array} = M_3$$




/	/	0	1
/	/	1	0
/	0	1	0
/	0	1	1

$$\begin{array}{cccc} a' + & b & c + d' & \\ \hline 1 & 0 & 0 & 1 \\ \hline 1 & 1 & 0 & 1 \end{array}$$

$$\textcircled{G} = \underline{\underline{f + g}}$$

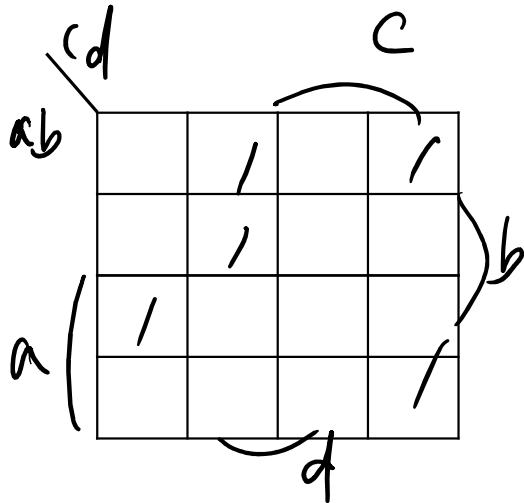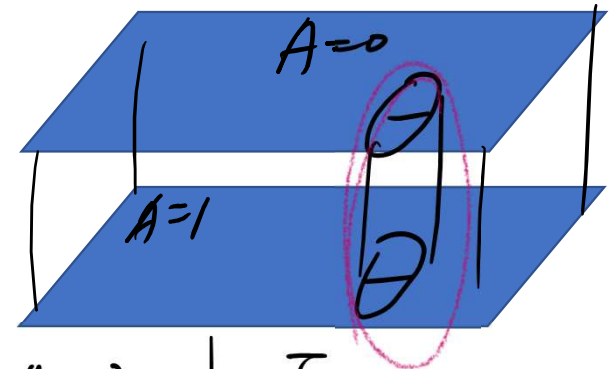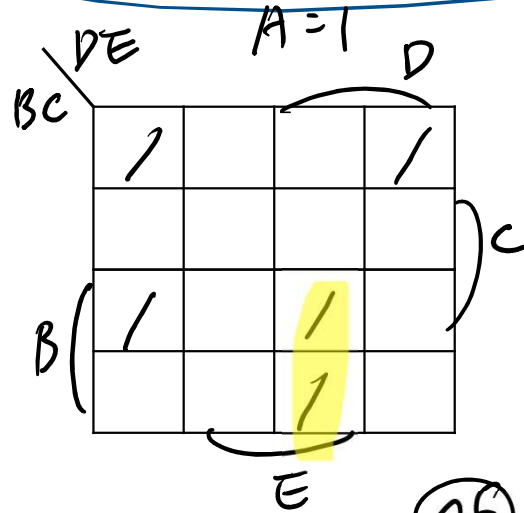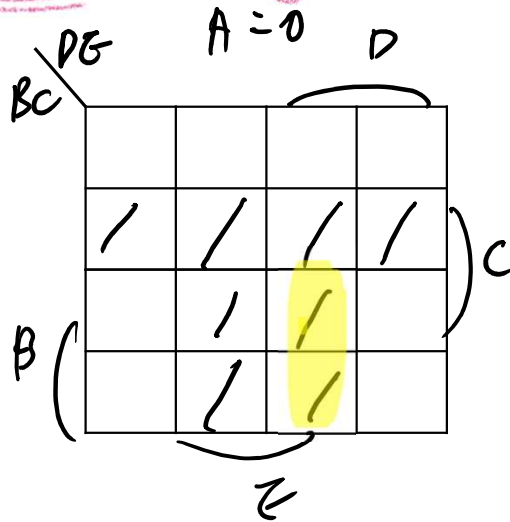- 5 variables K-map:  $F(A, B, C, D, E) = \Sigma(4, 5, 6, 7, 9, 11, 13, 15, 16, 18, 27, 28, 31)$








(cf)

$x$	$y$	$z$	$F$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Orange boxes highlight the 2x2 square groups in the first four rows and the last four rows.

- 6 variables K-map:
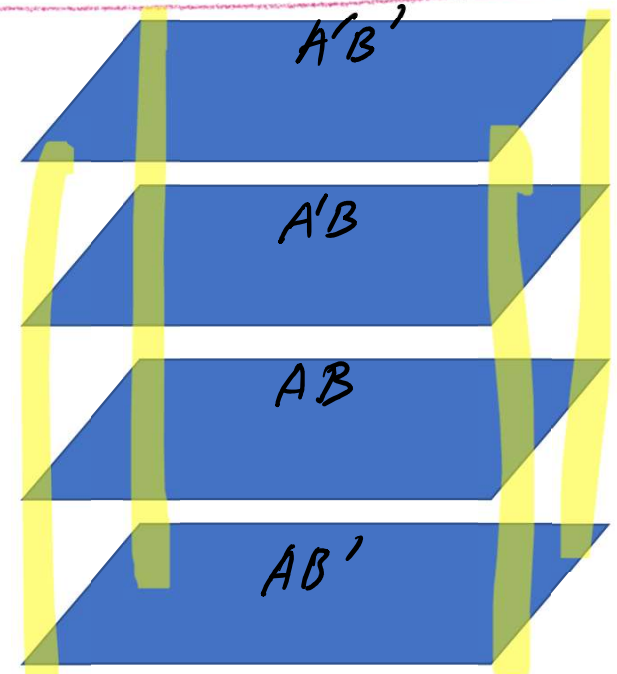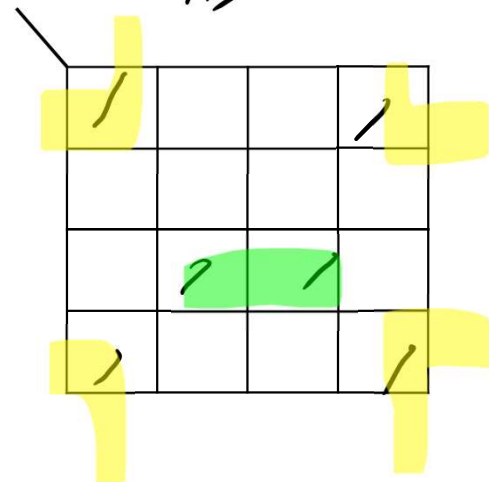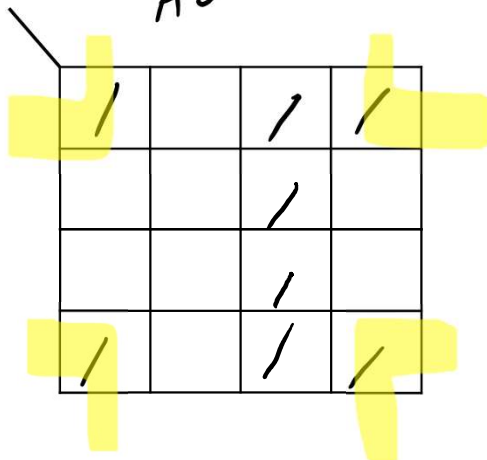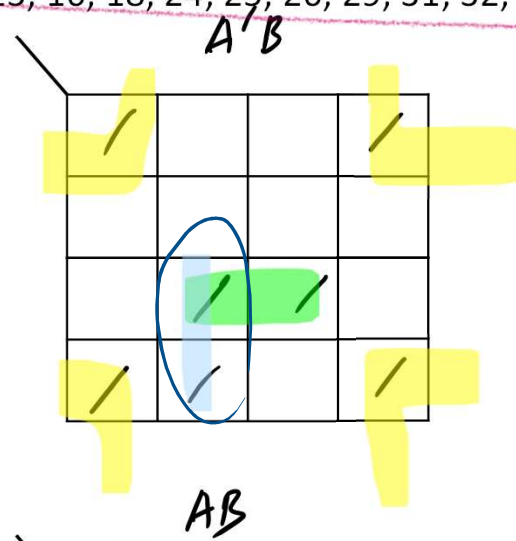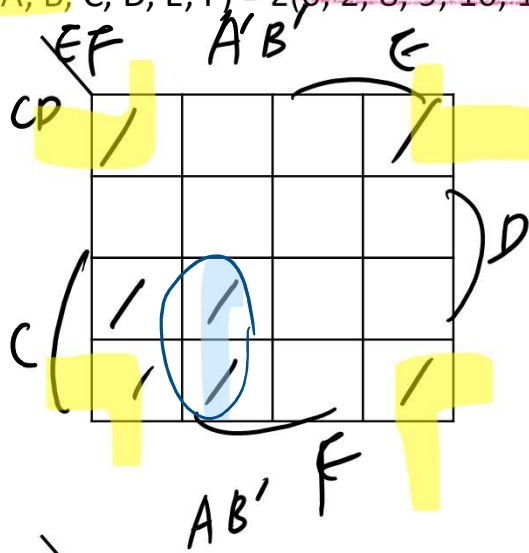
$$F(A, B, C, D, E, F) = \Sigma(0, 2, 8, 9, 10, 12, 13, 16, 18, 24, 25, 26, 29, 31, 32, 34, 35, 39, 40, 42, 43, 47, 48, 50, 56, 58, 61, 63)$$



$$Q : \frac{(A'B' + A'B)}{A'(\underline{C \cdot E' \cdot F})}$$

4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B. In each case, determine the values of the four SUM outputs, the carry C, and overflow V.

	M	A	B
(a)	0	0111	0110
(b)	1	1000	1001

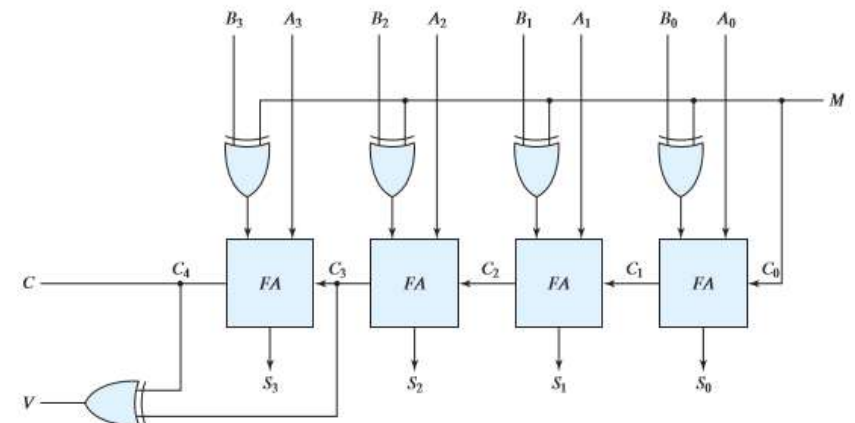


FIGURE 4.13  
Four-bit adder-subtractor (with overflow detection)

4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B. determine the values of the four SUM outputs, the carry C, and overflow V.

(a) M: 0, A: 0111, B: 0110  
 1011(?)  
0101

-8 < 4-bit signed # < +7

$$7 + (-5) = +2$$

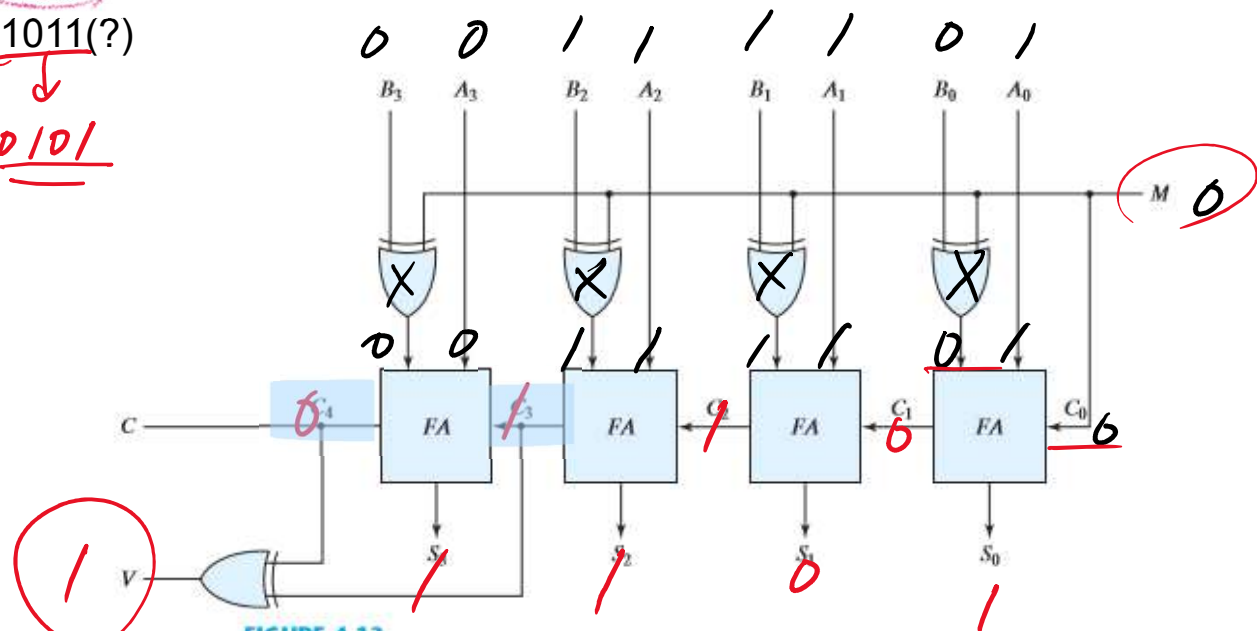


FIGURE 4.13  
Four-bit adder-subtractor (with overflow detection)



4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B. determine the values of the four SUM outputs, the carry C, and overflow V.

(b) M 1  
 A 1000  
 B 1001

$(-8) - (-7)$   
 $\Rightarrow (-8) + (2's\ CR\ of\ (-7))$

$(A) - (B)$   
 $(-A) - (-B)$   
 $\Rightarrow (-A) + (-(-B))$

$$\begin{array}{r} 1000 \\ \underline{1001} \\ 1000 \end{array}$$

$$\begin{array}{r} 1001 \\ \underline{1001} \\ 0111 \end{array}$$

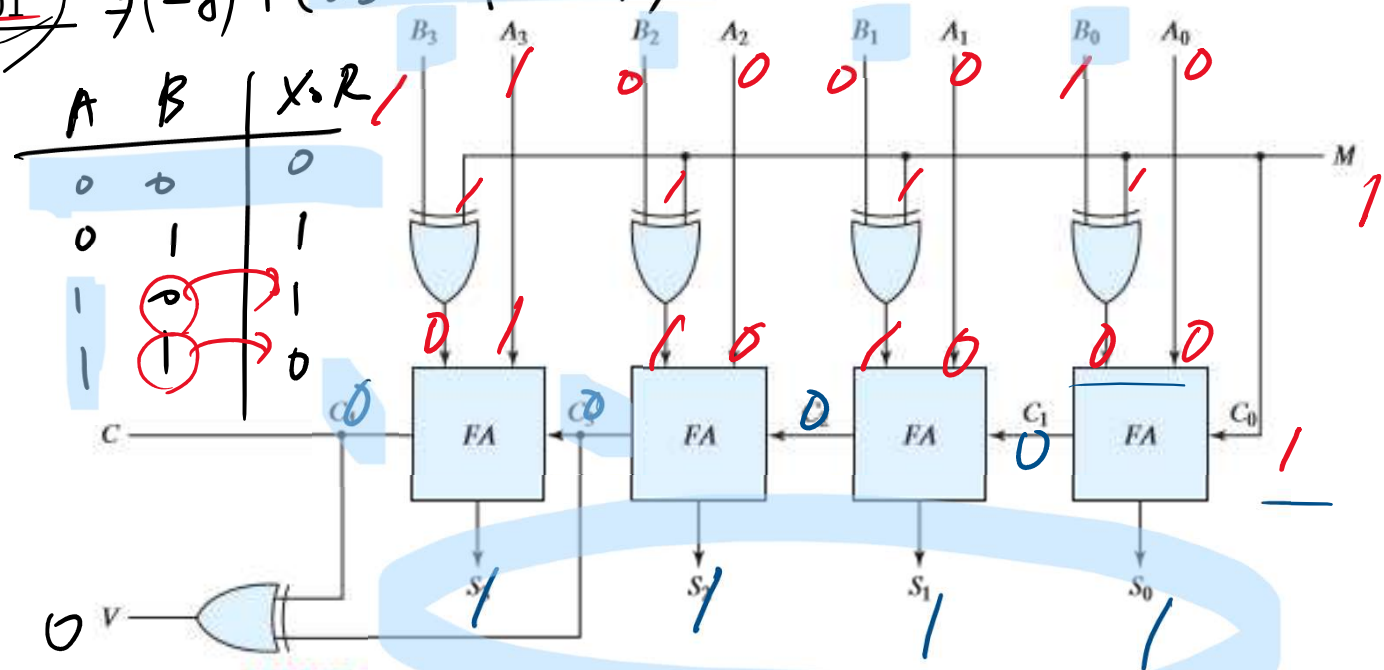


FIGURE 4.13  
 Four-bit adder-subtractor (with overflow detection)