

# ECE124: Discussion



Discussion #12

Yeonsik Noh, PhD

5.16 Design a sequential circuit with two D flip-flops A and B, and on input x\_in.


(b) When  $x_{in} = 0$ , the state of the circuit remains the same. When  $x_{in} = 1$ , the circuit goes through the state transitions from 00 to 11, to 01, to 10, back to 00, and repeat.

Current State		Input	Next State	
A	B	x	A	B
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	1

  

		1			1
			1	1	1

$$B(t+1) = AB + A'B'X + ABX$$

 


$$A(t+1) = A'X + AX'$$

**Modified 6.6** Design a four-bit shift register with parallel load using D flip-flops. There is one control input: shift/Load ( $SH/\overline{LD}$ ). When  $SH/\overline{LD} = 1$ , the content of the register is shifted toward  $A_3$  by one position. New data are transferred into the register when  $SH/\overline{LD} = 0$ .



$SH/LD = 1$  ---> shift mode ( $A_0 - A_3$ )

$SH/LD = 0$  ---> New data


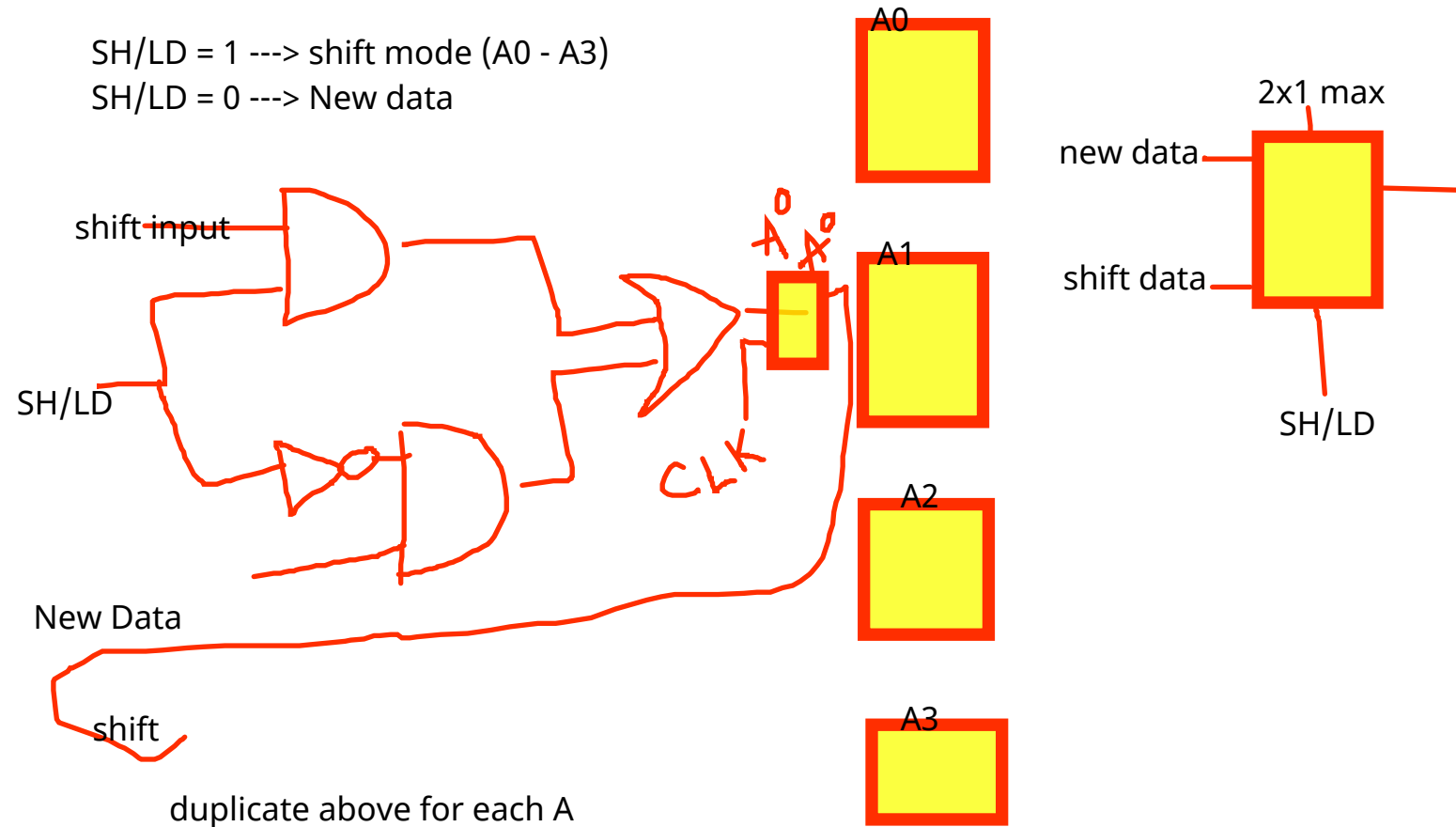


6.7 Draw the logic diagram of a four-bit register with four D flip-flops and four  $4 \times 1$  multiplexers with mode selection inputs  $s_1$  and  $s_0$ . The register operates according to the following function table.

$s_1$	$s_0$	Register Operation
0	0	No change
1	0	Complement the four outputs
0	1	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

  

 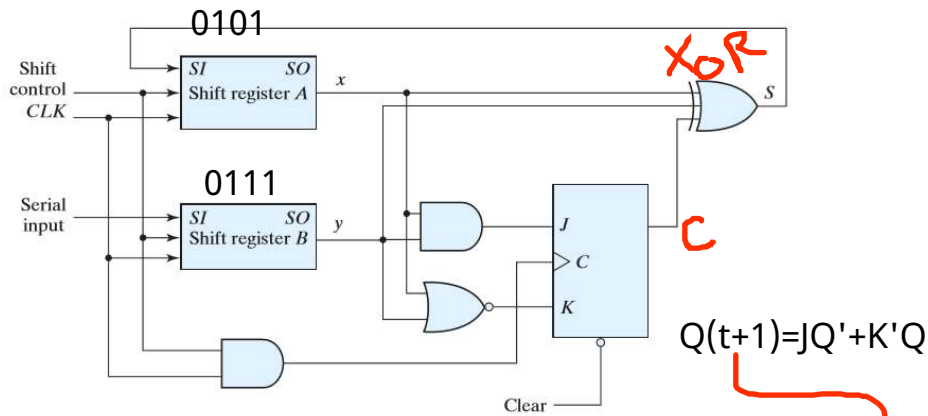6.8 The serial adder of Fig. 6.6 uses two four-bit registers. Register A holds the binary number 0101 and register B holds 0111. The carry flip-flop is initially reset to 0. List the binary values in register A and the carry flip-flop after each shift.



	Reg A	Reg B	X	Y	J	K	S	C
T0	0101	0111	X	X	X	X	X	
T1	0010	X011	1	1	1			1
T2	0001	XX01						
T3	1000	XXX0						
T4	1100	XXXX						

FIGURE 6.6  
Second form of serial adder

$$S = X \oplus Y \oplus C$$

$$C(t+1) = (XY)C' + (X+Y)C$$

$$XYC' + XC + YC$$

$$XYC' + XY'C + XYC + X'YC$$


$$XY + C(XY' + X'Y)$$

6.10 Design a serial 2's complementer with a shift register and a D flip-flop. The binary number is shifted out from one side and its 2's complement shifted into the other side of the shift register.

- Using the characteristic of 2's complement

pick the first 1 in the bit sequence

	0101	0010	100100
1s	1010	1101	011011
2s	1011	1110	011100

 

6.10 Design a serial 2's complementer with a shift register and a D flip-flop. The binary number is shifted out from one side and its 2's complement shifted into the other side of the shift register.


- Using the characteristic of 2's complement

$$Q(t+1) = Q(t) + x$$

$$y = Q(t) \oplus x$$


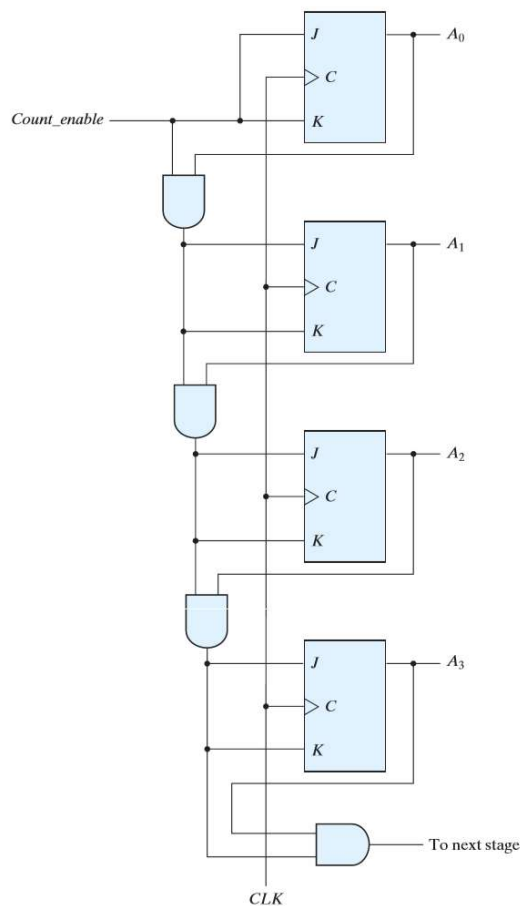
### 6.17 Design a four-bit binary synchronous counter with D flip-flops.



$$T_0 = E$$

$$T_1 = A_0 E$$

$$T_2 = A_1 A_0 E$$

$$T_3 = A_2 A_1 A_0 E$$

$$t_0(t+1) = A_0 \text{ XOR } E$$

$$t_1(t+1) = A_1 \text{ XOR } A_0 E$$

$$t_2(t+1) = A_2 \text{ XOR } A_1 A_0 E$$

$$t_3(t+1) = A_3 \text{ XOR } A_2 A_1 A_0 E$$

ABCD	ABCD
0000	0001
0001	0010
...	...

$$Q(t+1) = A \oplus T$$

FIGURE 6.12  
Four-bit synchronous binary counter



\***Up-Down Counter** Using T flip-flops, design a 2-bit up-down counter with external input x to determine whether Up or Down.

Present state		Input	Next state		FF inputs	
B	A	x	B(t+1)	A(t+1)	$T_B$	$T_A$
0	0	0	0	1	0	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	0	0	1	1
1	0	0	1	1	1	1
1	0	1	0	0	0	1
1	1	0	0	1	1	1
1	1	1	1	0	0	1

