

## ECE 124: Homework 6 Spring 2023

Assigned: Friday, May 5<sup>th</sup> at midnight

Due: Friday, May 12<sup>th</sup> at midnight

Late Submission Due: Saturday, May 13<sup>th</sup> at midnight

**Show your work! (No credit even for correct answers without justification.)**

*Problems from the textbook (Digital Design 6<sup>th</sup> Ed., M. Mano and M. Ciletti)*


**1) 5.3 (20 points)**

Show that the characteristic equation for the complement output of a JK flip-flop is

$$Q'(t+1) = J'Q' + KQ$$

**2) 5.7 (20 points)**

A sequential circuit has one flip-flop Q, two inputs x and y, and one output S. It consists of a full-adder circuit connected to a D flip-flop, as shown in Fig. P5.7. Derive the state table and state diagram of the sequential circuit.

 

**FIGURE P5.7**

**3) 5.9 (20 points)**

A sequential circuit has two JK flip-flops A and B, one input x. The circuit is described by the following flip-flop input equations:

$$J_A = x \quad K_A = B, \quad J_B = x \quad K_B = A'$$

- Derive the state equations  $A(t+1)$  and  $B(t+1)$  by substituting the input equations for the J and K variables.
- Draw the state diagram of the circuit.

**4) 6.6 (20 points)**

Design a four-bit shift register with parallel load using D flip-flops. There is two control inputs: shift and load. When shift = 1, the content of the register is shifted toward A3 by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.

**5) 6.17 (20 points)**

Design a four-bit binary synchronous counter with D flip-flops.