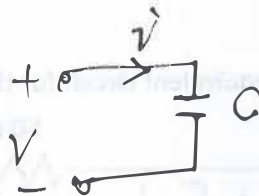


# RC Circuits

review




$$i = \frac{1}{R} \cdot V$$



$$i = C \cdot \frac{dV}{dt}$$

Follow Asso. Var. Convention

eg.1

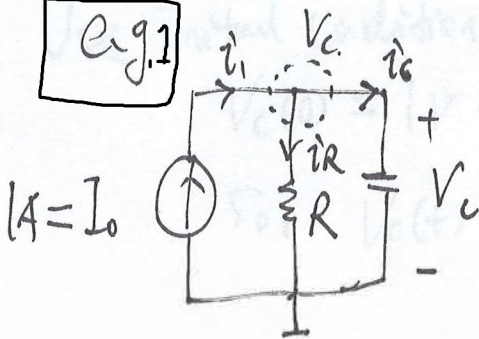

$$I_0 = 1A, V_c(t=0) = 1V$$

$$R = 3\Omega, C = 25F$$

find  $V_c(t)$  ( $t > 0$ ).

① KCL @ node  $V_c$ .

$$i_1 - i_R - i_C = 0$$

$$I_0 - \frac{V_c}{R} - C \cdot \frac{dV_c}{dt} = 0 \Rightarrow \frac{dV_c}{dt} + \frac{1}{RC} \cdot V_c = \frac{I_0}{C}$$

② Generally.. for 1<sup>st</sup> order diff. eq.

$$\frac{dV_c(t)}{dt} + \underbrace{A \cdot V_c(t)}_{\text{constants}} = \underbrace{B}_{\text{constants}}$$

General solution:

$$\text{So: } \boxed{V_c(t) = \frac{B}{A} + k \cdot e^{-A \cdot t}}$$

Arbitrary Constant

(to be determined)

In this case:


$$A = \frac{1}{RC}, \quad B = \frac{I_0}{C}$$

$$\begin{aligned} \text{So: } V_C(t) &= I_0 R + k \cdot e^{-\frac{t}{RC}} \\ &= 1A \cdot 3\Omega + k \cdot e^{-\frac{2}{3}t} = 3 + k \cdot e^{-\frac{2}{3}t} \end{aligned}$$

② Use Initial condition

$$V_C(0) = 1V \Rightarrow V_C(0) = 3 + k \cdot 1 \Rightarrow k = -2$$
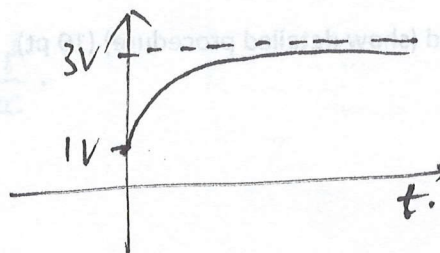
$$\text{So: } V_C(t) = 3 - 2 \cdot e^{-\frac{2}{3}t}$$




Summarize: In general for RC Circuit.

- ① KCL: find the differential equation
- ② find the general solution to the equation
- ③ Use initial conditions to determine the factors in general solution

How to determine the initial condition in a capacitor

\*\*\*

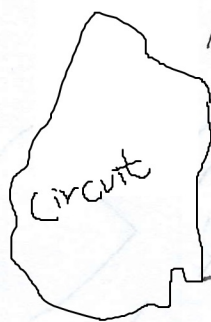

Note the basic property of a capacitor:

The charge amount stored in a capacitor cannot be instantaneously changed.

$$\text{That means: } Q_{C(0^-)} = Q_{C(0^+)} \Rightarrow \frac{Q_{C(0^-)}}{C} = \frac{Q_{C(0^+)}}{C}$$

$$\Rightarrow \boxed{V_{C(0^-)} = V_{C(0^+)}}$$

(or from mathematical perspective.

$$\left[ \begin{aligned} i &= C \cdot \frac{dV_C}{dt} \Rightarrow V_C(0^-) = V_C(0^+) \\ V_C \text{ needs to be continuous.} \end{aligned} \right]$$




So for capacitor:

$$V_C(0^+) = V_C(0^-).$$

The voltage drop across a capacitor can not be instantaneous changed.

e.g. 2

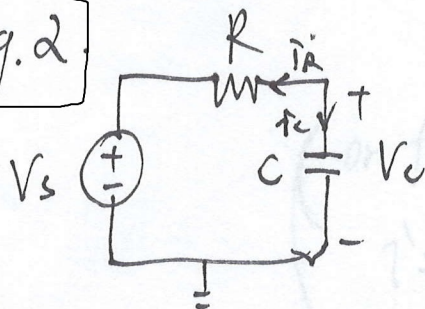


$$V_s = (V_1 - V_0) \cdot u(t) + V_0, \text{ find } V_C(t); t > 0$$

$u(t)$  is a step function

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$

$$\text{or: } u(0^-) = 0, u(0^+) = 1$$

Same as

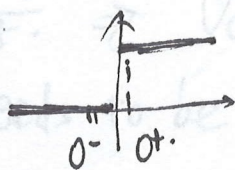

$$\begin{cases} V_s(0^-) = V_0 \\ V_s(0^+) = V_1 \end{cases}$$

① KCL ( $t > 0$ )

$$\text{for } t > 0: V_s(t > 0) = V_1$$

$$-i_C - i_R = 0 \Rightarrow -C \cdot \frac{dV_C}{dt} - \frac{V_C - V_1}{R} = 0$$

$$C \cdot \frac{dV_C}{dt} + \frac{V_C}{R} = \frac{V_1}{R}$$

$$\frac{dV_C}{dt} + \frac{V_C}{RC} = \frac{V_1}{RC}$$

$$\textcircled{2} \text{ So: } \frac{dV_C}{dt} + \frac{1}{RC} \cdot V_C = \frac{V_1}{RC} \quad \left( A = \frac{1}{RC}, B = \frac{V_1}{RC} \right)$$

So general solution:

$$V_C = V_1 + k \cdot e^{-\frac{t}{RC}}$$

③ Initial condition:

① to find  $V_c(0^+) \rightarrow$  is to find  $V_c(0^-)$

②  $V_c(0^-) = V_0$ . (At steady state, a capacitor behaves like an open-circuit)

Sol:  $V_c(0^+) = V_0 = V_1 + k \cdot e^{-0}$   
 $= V_1 + k \Rightarrow k = V_0 - V_1$

Sol:  $V_c = V_1 + (V_0 - V_1) \cdot e^{-\frac{t}{RC}}$

