
ECE 213 Spring 2024

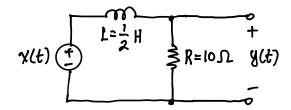Example 5.3: Consider a periodic input signal¹

$$x(t) = \sum_{n=-\infty}^{\infty} \frac{1}{1+jn} e^{j4n\pi t}.$$

It is applied to the following circuit as input.



- (a) Find the amplitude-phase version of the Fourier series for x(t).
- (b) Find the output y(t) using phasor analysis.

Solution:

(a) First, we recognize

$$\omega_0 = 4\pi \text{ (rad/s)}, \ T_0 = \frac{2\pi}{\omega_0} = 0.5 \text{ (s)}.$$
 (E1)

For the amplitude-phase representation,

$$c_0 = x_0 = \frac{1}{1+j0} = 1,$$
 (E2)

$$c_n = 2|x_n| = \frac{2}{\sqrt{1+n^2}},$$
 (E3)

$$\phi_n = \angle x_n = -\tan^{-1} n. \tag{E4}$$

¹Note that $x_{-n} = x_n^*$. x(t) is a real-valued signal.

ECE 213 Spring 2024

Therefore,

$$x(t) = 1 + \sum_{n=1}^{\infty} \frac{2}{\sqrt{1+n^2}} \cos(4n\pi t - \tan^{-1} n)$$
. (E5)


(b) First, (E5) can be put in phasor form:

$$x(t) = X_0 + \sum_{n=1}^{\infty} \text{Re} \{X_n e^{j4n\pi t}\},$$
 (E6)

where

$$X_0 = 1, \ X_n = \frac{2}{\sqrt{1+n^2}} e^{-j \tan^{-1} n} \ (n = 1, 2, ...).$$
 (E7)

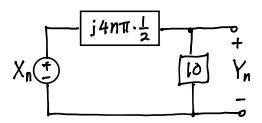For the *n*-th component (at $\omega = 4n\pi$), the circuit has a phasor form below.



We find

$$Y_n = X_n \frac{10}{10 + j2n\pi},\tag{E8}$$

UMass Amherst E-2 Kwon

ECE 213 Spring 2024

from which the magnitude and phase are found to be

$$|Y_n| = |X_n| \frac{10}{\sqrt{100 + (2n\pi)^2}} = \frac{20}{\sqrt{1 + n^2} \sqrt{100 + (2n\pi)^2}},$$
(E9)
$$\angle Y_n = \angle X_n + \angle \frac{10}{10 + j2n\pi} = -\tan^{-1} n - \tan^{-1} \frac{n\pi}{5}.$$
(E10)


Together with $Y_0 = X_0 = 1$, we find

$$y(t) = Y_0 + \sum_{n=1}^{\infty} \text{Re} \left\{ Y_n e^{j4n\pi t} \right\}$$

$$= 1 + \sum_{n=1}^{\infty} \frac{20}{\sqrt{1 + n^2} \sqrt{100 + (2n\pi)^2}}$$

$$\times \cos \left(4n\pi t - \tan^{-1} n - \tan^{-1} \frac{n\pi}{5} \right)$$
(E11)

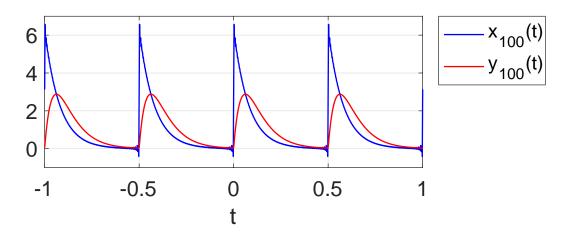Truncated series for the input and output with N = 100 are shown below.



UMass Amherst E-3 Kwon