

ECE 202, Exercist E6: Current, Voltage and Power Absorbed
for a charging inductor ($V_0 = 5V$, $R = 2\text{ohm}$, $L = 10\text{mH}$)

