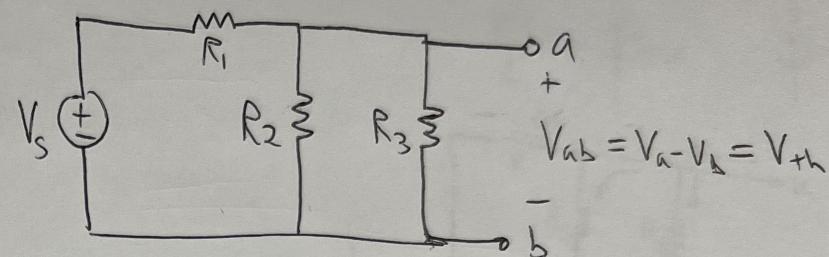


## Exam topics


- Thvenin/Norton — {HW5}
- Op-amps — {HW6  
HW7-9, p1}
- R.C — {HW7}
- RL — {HW8}
- RLC — {HW9}
- Dependent Sources — {HW5, p3  
HW7,8, p2}

## Thvenin/Norton

Given




Goal

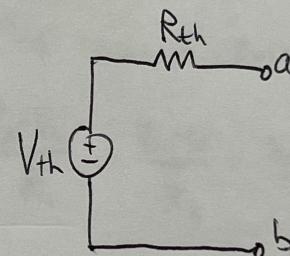

Thevenin  
equivalent  
circuit

or

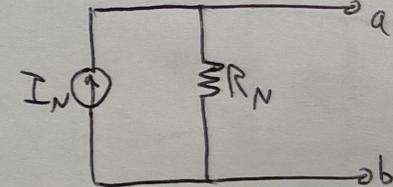


Norton  
equivalent  
circuit



$$I_N = \frac{V_{th}}{R_{th}}$$


$$R_N = R_{th}$$

① Find  $V_{th}$

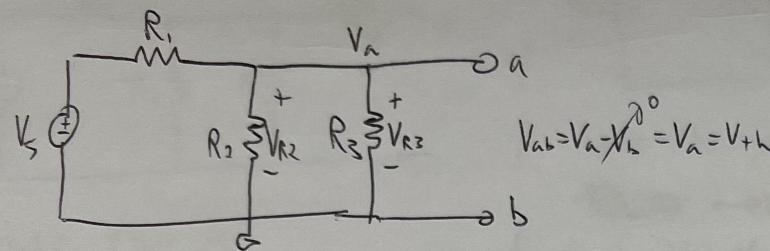
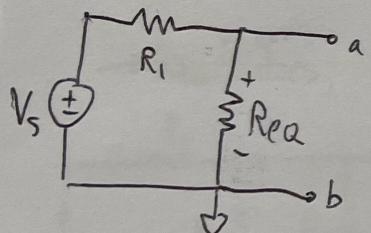
## Easy way - Voltage divider



$$\bullet \underbrace{V_{R_3} = V_{R_2}}_{\text{in parallel}} = V_{ab} = V_{+b}$$




$$V_{ab} = V_s \frac{R_{eq}}{R_1 + R_{eq}} = V_{th}$$

② Find Rth


- turn off SourceS

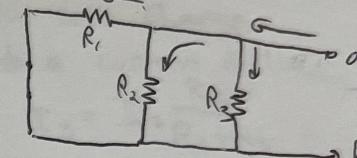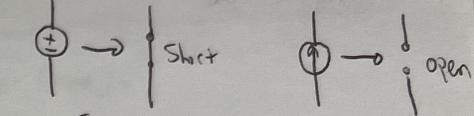

$$\downarrow R_2 // R_3 = R_{eo}$$

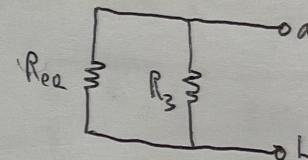
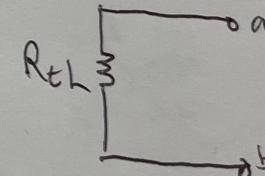
$$\downarrow R_{eq} // R_3 = \underline{R_{th}}$$




## Nodal analysis

@ Va node, all currents leaving..

$$\frac{V_a - V_s}{R_1} + \frac{V_a - 0}{R_2} + \frac{V_a - 0}{R_3} = 0$$

$$V_a = \underline{\underline{m}} = V_{+n}$$


What if's...

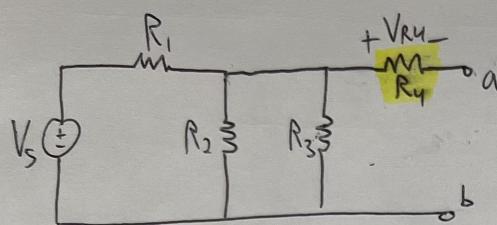


What changes?

- $V_{th}$  does not change
- $I_{R4} = 0A$  (dangling wire)
- So,  $V_{R4} = 0V$  ( $V = IR$ )
- ⇒  $V_a$  Same as before

→  $R_{th}$  does change

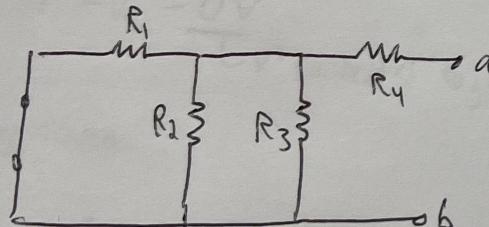


$$R_1/R_2/R_3 = R_{eq}$$

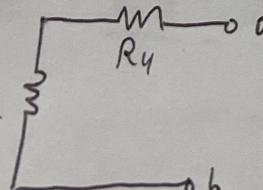

$I_{R4}$

$+V_{R4}$

$R_4$

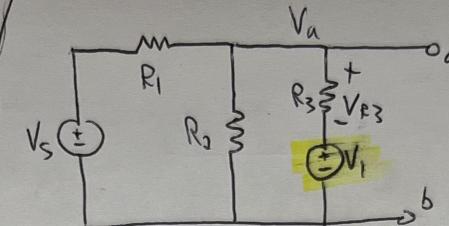

What changes?


~~→  $V_{th}$  does change~~

$$V_{ab} \neq V_{R3}$$

$$V_{ab} = V_i + V_{R3}$$

- do nodal at  $V_a$  to find  $V_{th}$

→  $R_{th}$  does not change

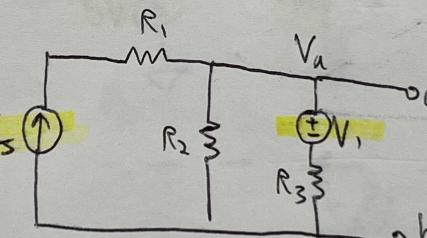

What changes?


~~→  $V_{th}$  does change~~

• Cannot do current divider

~~because voltage barriers~~

- do nodal at  $V_a$  to find  $V_{th}$

→  $R_{th}$  does change

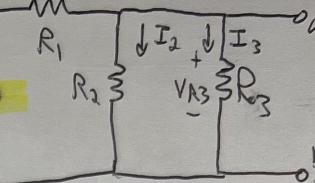

What changes?


→  $V_{th}$  does change

do a current divider

$$I_3 = I_s \frac{R_2}{R_2 + R_3}$$

$$V_{th} = V_{R3} = R_3 \cdot I_3$$


→  $R_{th}$  does change

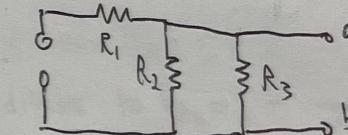

$$R_{th} = R_2 // R_3$$

same  
as  
this

## OP-amps

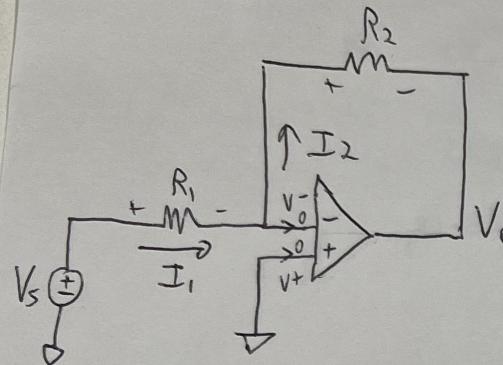

## Goal

- equation for  $V_o$

### ① apply op-amp rules

- $V^+ = V^- = 0V$

$V^+$  connected to ground

- $i^+ = 0A$

- $i^- = 0A \rightarrow I_1 = I_2$

### ② KCL

$$\frac{V_s - V^+}{R_1} = \frac{V^+ - V_o}{R_2}$$

$$V_o = -\frac{R_2}{R_1} V_s$$

## What if's

$V^+ = 5V$  now

$i^+ = 0A$  (rule)

$\text{So } V_R = i^+ \cdot R = 0V$

$$V^+ = 5 \cdot \frac{R_b}{R_a + R_b}$$

- $i^+ = 0A$

- Nonzero current thru  $5V$ ,  $R_a$ ,  $R_b$
- Voltage divider to  $V_{Rb} = V^+$

- $V^+$  still 0V

- KCL is  $I_1 = I_2$

$$I_s = \frac{V^+ - V_o}{R_2}$$

$$V_o = -I_s R_2$$