

# ECE124: Discussion

Discussion #8

Yeonsik Noh, PhD

3.21 Draw (a) the multiple-level NAND circuit for the following expression and (b) repeat (a) for a NOR circuit.


$$w(x + y + z) + xyz$$

$$F(wxyz) = w(x+y+z) + xyz$$

$$(w(x+y+z) + xyz)'$$

$$(wx + wy + wz + xyz)'$$

$$(wz)'(wy)'(wx)'(xyz)'$$

 

$$(F')' = ((wz)'(wy)'(wx)'(xyz)')'$$



$$\begin{aligned} F' &= (w(x'y'z')' + xyz)' \\ &= (w(x'y'z')')'(xyz)' \\ &= ((w(x'y'z')')')(xyz)'' \end{aligned}$$



  3.21 (b) repeat (a) for a NOR circuit.

$$w(x + y + z) + xyz$$

$$\begin{aligned} &F' (w(x+y+z)+xyz)' \\ &(w(x+y+z))'(xyz)' \\ &((w'+(x+y+z)')(x'+y'+z'))' \\ &(((w'+(x+y+z)')'+(x'+y'+z')')')' \end{aligned}$$



3.26 With the use of maps, find the simplest sum-of-products form of the function  $F = fg$ , where






$$a' + c + d'$$

$$1101$$





$$f = abc' + c'd + a'cd' + b'cd'$$

$$g = (a + b + c' + d')(b' + c' + d)(a' + c + d')$$

$$00111111$$

     

    - 5 variables K-map:  $F(A, B, C, D, E) = \Sigma(4, 5, 6, 7, 9, 11, 13, 15, 16, 18, 27, 28, 31)$



- 6 variables K-map:

$$F(A, B, C, D, E, F) = \Sigma(0, 2, 8, 9, 10, 12, 13, 16, 18, 24, 25, 26, 29, 31, 32, 34, 35, 39, 40, 42, 43, 47, 48, 50, 56, 58, 61, 63)$$

$A'B'$

/			/
/	/		
/	/		/

$A'B$


/			/
	/	/	
/	/		/

$AB'$

/		/	/
		/	
		/	
/		/	/

$AB$

/			/
	/	/	
/			/

 

$$C : (A'B' + A'B)$$

$$D (C F F')$$

4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B.

In each case, determine the values of the four SUM outputs,

the carry C, and overflow V.

	M	A	B
(a)	0	0111	0110
(b)	1	1000	1001

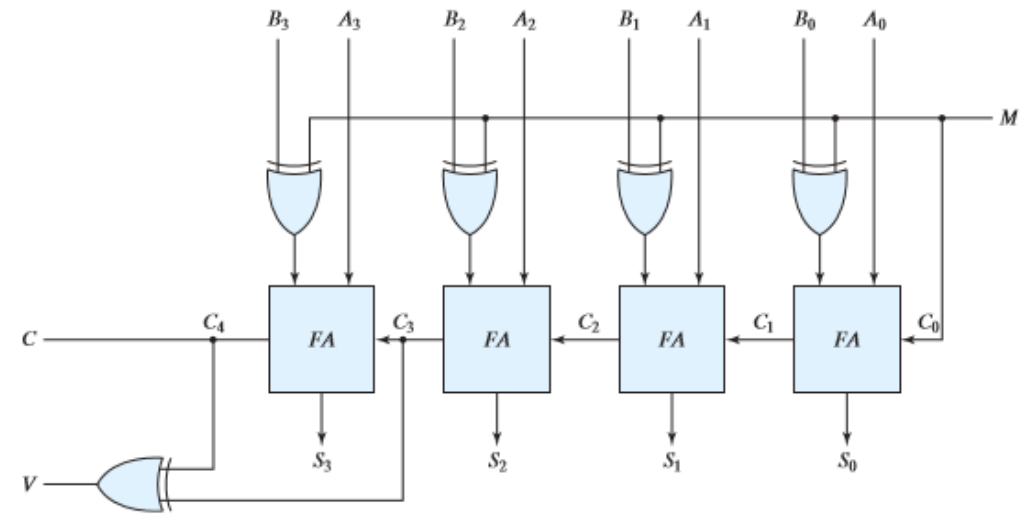


FIGURE 4.13


Four-bit adder-subtractor (with overflow detection)

4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B. determine the values of the four SUM outputs, the carry C, and overflow V.

(a) M = 0, A = 0111, B = 0110  
1011(?)

-8 < 4 bit signed # < +7


$$7 + (-5) = 2$$

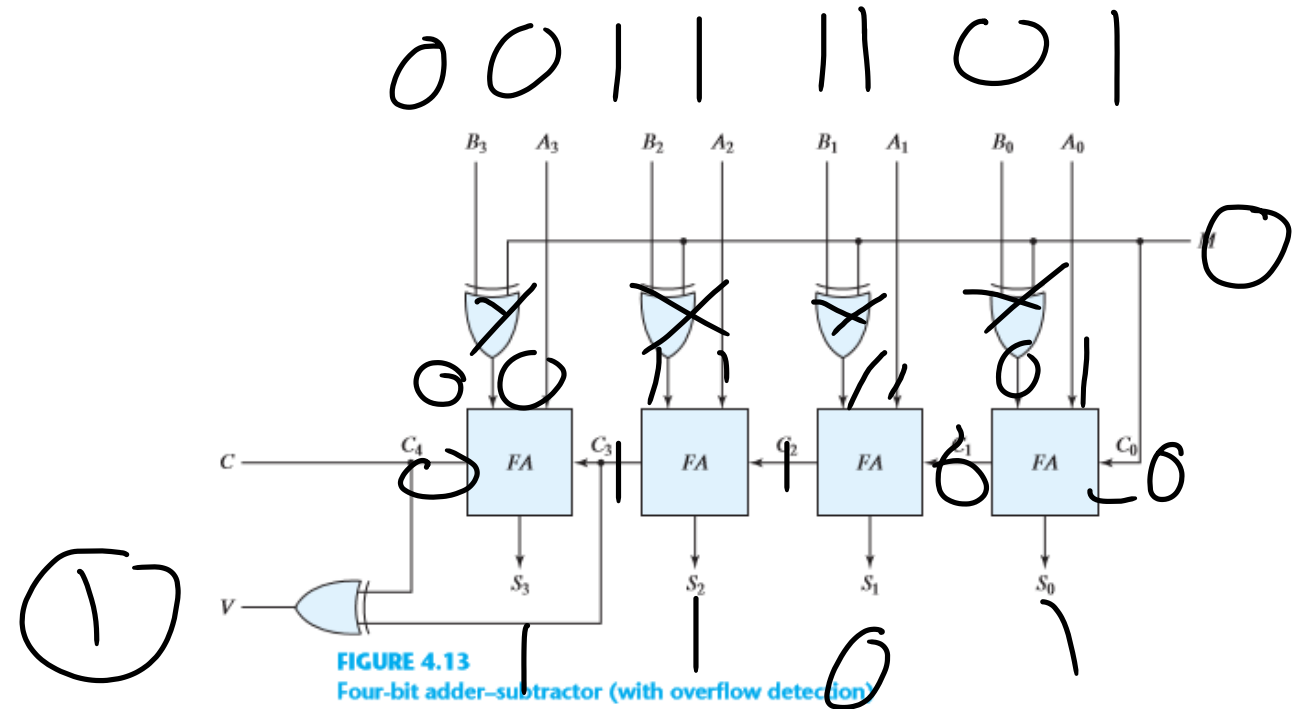



 4.13 The adder-subtractor circuit of Fig. 4.13 has the following values for mode input M and data inputs A and B.

determine the values of the four SUM outputs, the carry C, and overflow V.



(a)-(b)

(-a)-(-b)

(-a)+(-(-b))

1000

1000

1001

0111

 
 


FIGURE 4.13  
Four-bit adder-subtractor (with overflow detection)

- Carry Lookahead Equations

Full adder

$$\begin{cases} C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i \\ S_i = A_i \oplus B_i \oplus C_i \end{cases}$$

Recall

$$\begin{cases} G_i = A_i B_i \leftarrow \text{"carry generate" for stage } i \\ P_i = A_i \oplus B_i \leftarrow \text{"carry propagate" for } i \end{cases}$$

$$\begin{cases} C_{i+1} = G_i + P_i C_i \\ S_i = P_i \oplus C_i \end{cases}$$

$$\begin{cases} C_0 = \text{input carry} \\ C_1 = G_0 + P_0 C_0 \\ C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0 \\ C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \\ C_4 = G_3 + P_3 C_3 = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{cases}$$

$$\begin{cases} S_0 = P_0 \oplus C_0 \\ S_1 = P_1 \oplus C_1 \\ S_2 = P_2 \oplus C_2 \\ S_3 = P_3 \oplus C_3 \end{cases}$$

- Design a combinational circuits for parity generator/checker

