

UMass ECE 210 – Fall 2023

Lab 8: LTSpice – RC, RL, and RLC Circuits

GOALS:

- ☐ Simulate and analyze transient response in RC, RL, RLC circuits
- ☐ Understand voltage/current behavior for L and C in response to change in circuit state

Lab report:

1. Introduce justification for experiment.
 - a. Analyze transient response of RC, RL, and RLC circuits via simulation
2. Properly label and document simulation schematics and simulation results
 - a. Label components, interesting nodes
 - b. Label simulation output plots
 - c. Label specified values (steady state, rise/fall)

You will need to **RECORD all of your data independently.**

The simulation data required for your lab report are listed in black boxes like this throughout the following parts.

FOLLOW ALL STEPS AND INCLUDE ALL REQUIRED DATA IN YOUR REPORT!

Introduction: RC, RL, RLC Transient Response


Most of our circuit analysis so far has focused on resistive circuits (only resistors and DC voltage/current sources). In these circuits, we could “easily” find any voltage/current at any time t using basic techniques like Ohm’s Law ($V=IR$), KVL/KCL, etc. In other words, the voltages/currents would not vary with respect to time.

When we added capacitors and inductors, some voltages/currents would now vary with respect to time, and our circuit analysis became more complicated (i.e., required differential equations to model time dependent voltages/currents). We are usually interested in knowing how these voltages/currents behave after some change occurs in the circuit. For example, if a switch in a circuit closes, a capacitor may begin to discharge (output current) – what will the voltage across the capacitor be 5 seconds after the switch opens? 10 seconds? (in reality the time scale may be in micro- or nanoseconds).

In the homeworks, you have been finding the differential equations and solutions (e.g., $v(t) = B/A + ke^{(-At)}$) that model these voltages and currents after some change in a circuit. To help visualize what these equations mean, you will simulate the voltage/current values in RC, RL, and RLC (from HW9, problem 2) circuits in LTSpice. In each circuit, a voltage source V_s will change values at a specific time ($t = 5s$). Your simulation will show you what happens to the voltages/currents before and after the change ($t < 5s$ and $t > 5s$). You will then perform some analysis to determine initial condition and steady state values.

Reference Lab 3 as you work to remind yourself of how to use LTSpice. You will be doing simulations for 4 circuits – it may save you time in the end if you build a separate schematic for each circuit, rather than doing one, then building onto it to make the next circuit, and so on.

Part 1: Simple R Circuit

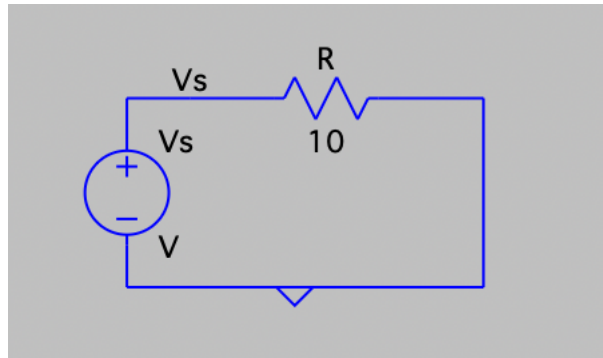


Pictured above is a simple resistive circuit with voltage source V_s and resistor R . The bottom of the circuit is grounded. The node between V_s and R is labeled as V_s (note this is equal to the voltage across R). As a “control,” we will simulate the transient response of this circuit.

- ☐ Before $t = 5s$, $V_s = 1V$ (for a “long” time = steady state)
 - ☐ At $t = 5s$, V_s changes to $5V$ ($t=5$ here will be like $t=0$ in the homeworks)
 - ☐ $R = 10$ ohms
- Simulate the node voltage V_s and current IR (left to right through R)

1. Build the circuit schematic shown above

1.1. For the source value of V_s , replace V with **PULSE(1 5 5 0.1 0.1 30 30 1)**

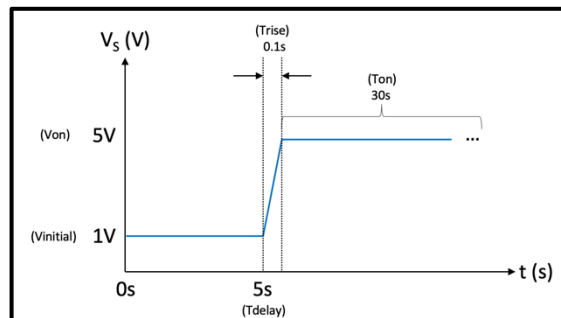1.1.1. This is saying V_s will act like a square wave pulse with the parameters below.



PULSE(V1 V2 Td Tr Tf Ton Tperiod <Ncycles>)									
Vinitial[V]:	1								
Von[V]:	5								
Tdelay[s]:	5								
Trise[s]:	0.1								
Tfall[s]:	0.1								
Ton[s]:	30								
Tperiod[s]:	30								
Ncycles:	1								

1.2. When placing the resistor, LTSpice assigns a polarity (+ on top if you place the resistor vertically as is). In other words, LTSpice will tell you the current flowing down the resistor when you simulate it. To get LTSpice to simulate the current flowing left to right through the resistor (clockwise) in the schematic above, rotate it 270deg before placing it into the circuit. The polarity will be + on the left.

1.2.1. After running the simulation, you can hover your cursor over any component in your schematic – the cursor will change to a symbol indicating the direction of the current that LTSpice is plotting.

1.3. Make sure the node between V_s and R is labeled as V_s .

2. Run the transient simulation

2.1. Add a SPICE directive to measure the transient response for 30s: **.tran 30s**

2.2. Run the simulation. Right click inside the empty simulation pop-up window and select “Add plot pane.” This will split the simulation window into two plots.

2.3. In the top plot, add the voltage trace for node Vs: **V(vs)**.

2.3.1. Right click the y axis and set the following parameters:

Vertical Axis Manual Plot Limits

Top:	6V
Tick:	1V
Bottom:	0V

2.4. In the bottom plot, add the current trace for the resistor current: **I(R)**. You should see positive current if you placed the resistor as directed above.

2.4.1. Right click the y axis and set the following parameters:


Vertical Axis Manual Plot Limits

Top:	550mA
Tick:	100mA
Bottom:	0A


In your lab report, include the following (matching the format below)...

- ☐ Your circuit schematic in the $t > 5s$ box
- ☐ Draw the steady state circuit for $t < 5s$ (you can just include your schematic again for this part, since the resistor will not change).
- ☐ The direction of the simulated current, shown on the schematics.
- ☐ Your voltage plot (with **V(vs)**) and current plot (with **I(R)**).
- ☐ The voltage and current values at the specified times, estimated visually from your plots.

$t < 5s$ (steady state)

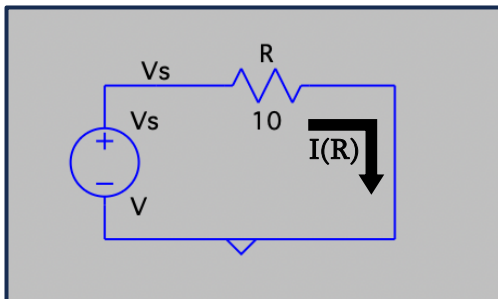

$t > 5s$ (transient)

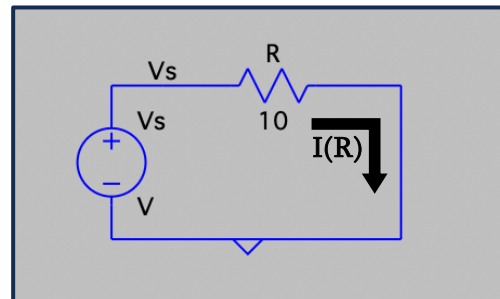

Voltage

V(vs) curve

V(vs) @ $t=0s$?

V(vs) @ $t=10s$?

Current


I(R) curve

I(R) @ $t=0s$?

I(R) @ $t=10s$?

0s 3s 6s 9s 12s 15s 18s 21s 24s 27s 30s

Part 2: RC Circuit

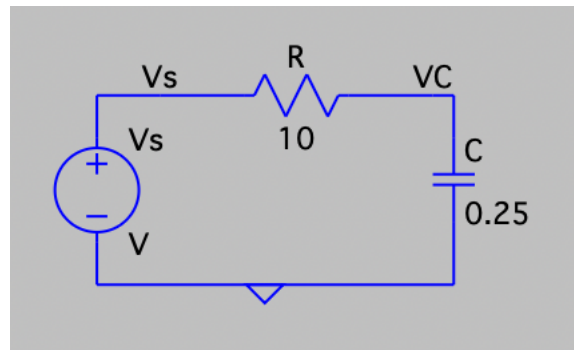

Pictured above is an RC circuit with voltage source V_s , resistor R , and capacitor C . The node between V_s and R is labeled as V_s . The node between R and C is labeled as V_C (equal to the voltage across the capacitor).

- ☐ Before $t = 5s$, $V_s = 1V$ (for a “long” time = steady state)
- ☐ At $t = 5s$, V_s changes to $5V$
- ☐ $R = 10$ ohms
- ☐ $C = 0.25$ F

→ **Simulate the voltages V_s and V_C , and the current I_C (down C)**

1. Build the circuit schematic shown above

- 1.1. For the source value of V_s , replace V with **PULSE(1 5 5 0.1 0.1 30 30 1)** (same as before)
- 1.2. Make sure the nodes are labeled accordingly.

2. Run the transient simulation

- 2.1. Add a SPICE directive to measure the transient response for 30s: **.tran 30s**
- 2.2. Run the simulation. Right click inside the empty simulation pop-up window and select “**Add plot pane.**” This will split the simulation window into two plots.

2.3. In the top plot, add the voltage traces for nodes V_s and V_C : **V(vs)** and **V(vc)**.

- 2.3.1. Right click the y axis and set the following parameters:

Vertical Axis Manual Plot Limits	
Top:	6V
Tick:	1V
Bottom:	0V

2.4. In the bottom plot, add the current trace for the capacitor current: **I(C)**.

- 2.4.1. Right click the y axis and set the following parameters:

Vertical Axis Manual Plot Limits	
Top:	500mA
Tick:	100mA
Bottom:	-100mA

3. Find the rise time of VC

3.1. From your voltage plot, you should see that VC starts a steady state value, $VC(t=5^-)$ (like $VC(t=0^-)$ normally), then rises and settles at a final value after some time.

3.2. Enter the following SPICE directive:

3.2.1. .meas TRAN VC_riseTime FIND time WHEN V(vc)=xV

3.2.2. This statement finds the time when $VC = x$ and returns that in a variable named VC_riseTime, which you can find in your log file (Hotkey: **CMD+L** or **CTRL+L**).

3.2.3. REPLACE x WITH A VALUE SLIGHTLY LESS THAN THE FINAL VALUE YOU SEE IN YOUR PLOT.

For example, if your final value is 5, enter 4.99 for x.

3.3. Re-run the simulation and open the log file. With no errors, you should see:

```
vc_risetime: time=20.0256 at 20.0256
```

4. Find the fall time of IC

4.1. From your current plot, you should see that IC starts at some steady state value, spikes to some maximum at $t=5s$, and then falls until it settles at a final value after some time.

4.2. Enter the following SPICE directive:

4.2.1. .meas TRAN IC_fallTime FIND time WHEN I(c)=xmA cross=last

4.2.2. This statement finds the time when $IC = x$ and returns that in a variable named IC_fallTime, which you can find in your log file (Hotkey: **CMD+L** or **CTRL+L**). The “cross=last” parameter is needed because $IC = x$ earlier in the plot (before $t=5s$), but we want the time when $IC = x$ afterwards (after $t=5s$).


4.2.3. REPLACE x WITH A VALUE SLIGHTLY GREATER THAN THE FINAL VALUE YOU SEE IN YOUR PLOT.

For example, if your final value is 0, enter 0.1 for x.


4.3. Re-run the simulation and open the log file to check your results.

In your lab report, include the following (matching the format below)...

- ☐ Your circuit schematic in the $t > 5s$ box
- ☐ Draw the steady state circuit for $t < 5s$ (remember what capacitors act like at steady state).
- ☐ The direction of the simulated current, shown on the schematics.
- ☐ Your voltage plot (with $V(vs)$, $V(vc)$) and current plot (with $I(C)$).
- ☐ The log file including the indicated rise and fall times.
- ☐ The capacitor voltage at $t = 5^-$ (think $V_c(0^-)$ from the homeworks; list next to or indicate on your plot)

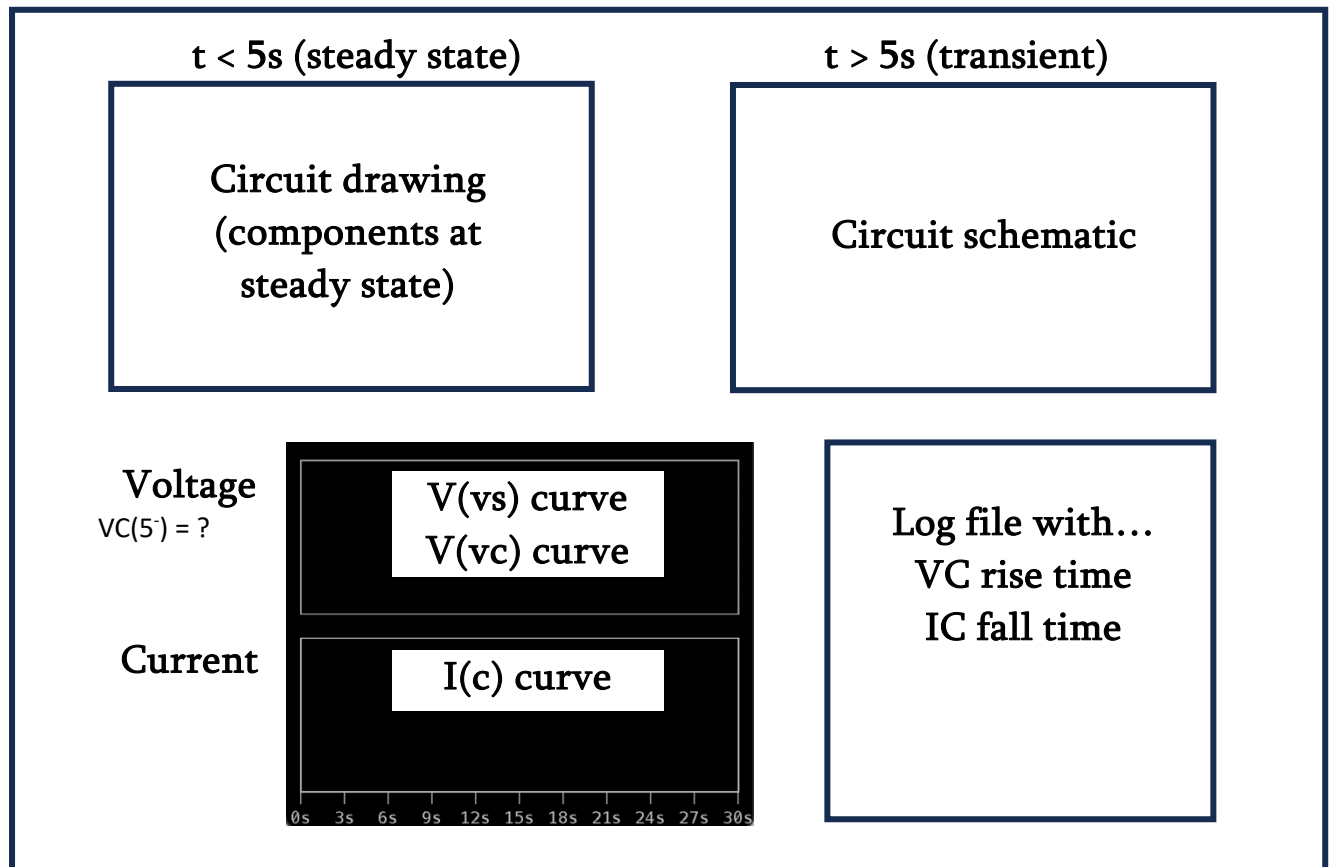

Part 3: RL Circuit

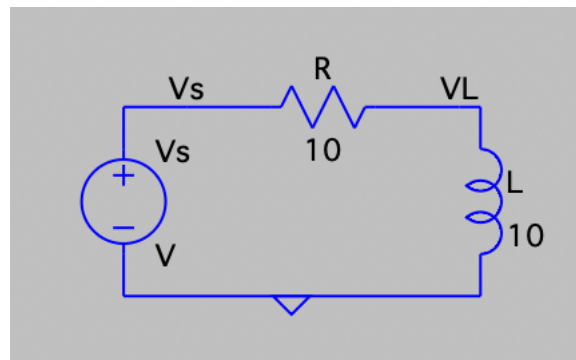

Pictured above is an RL circuit with voltage source V_s , resistor R , and inductor L . The node between V_s and R is labeled as V_s . The node between R and L is labeled as V_L (equal to the voltage across the inductor).

- ☐ Before $t = 5\text{s}$, $V_s = 1\text{V}$ (for a “long” time = steady state)
- ☐ At $t = 5\text{s}$, V_s changes to 5V
- ☐ $R = 10\text{ ohms}$
- ☐ $L = 10\text{ H}$

→ **Simulate the voltages V_s and V_L , and the current I_L (down through L)**

5. Build the circuit schematic shown above

- 5.1. For the source value of V_s , replace V with **PULSE(1 5 5 0.1 0.1 30 30 1)** (same as before)
- 5.2. Make sure the nodes are labeled accordingly.

6. Run the transient simulation


- 6.1. Add a SPICE directive to measure the transient response for 30s: **.tran 30s**
- 6.2. Run the simulation. Right click inside the empty simulation pop-up window and select “**Add plot pane.**” This will split the simulation window into two plots.
- 6.3. In the top plot, add the voltage traces for nodes V_s and V_L : **V(vs)** and **V(vl)**.

6.3.1. Right click the y axis and set the following parameters:

Vertical Axis Manual Plot Limits	
Top:	5V
Tick:	2V
Bottom:	-1V

6.4. In the bottom plot, add the current trace for the inductor current: **I(l)**.

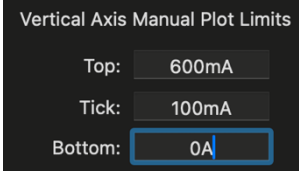6.4.1. Right click the y axis and set the following parameters:



Vertical Axis Manual Plot Limits

Top: 600mA

Tick: 100mA

Bottom: 0A


7. Find the fall time of VL and the rise time of IL

7.1. Using similar **.meas** SPICE directives as in the RC circuit, find the fall time of VL and rise time of IL. You can eyeball the final values easily from the plots (if you set the y-axes as above). For VL, make sure to use “**cross=last**” in your statement.


7.2. Re-run the simulation and open the log file to check your results.

In your lab report, include the following (matching the format below)...

- ☐ Your circuit schematic in the $t > 5s$ box
- ☐ Draw the steady state circuit for $t < 5s$ (remember what inductors act like at steady state).
- ☐ The direction of the simulated current, shown on the schematics.
- ☐ Your voltage plot (with **V(vs)**, **V(vl)**) and current plot (with **I(l)**).
- ☐ The log file including the indicated rise and fall times.
- ☐ The inductor current at $t = 5^-$ (think $IL(0^-)$ from the homeworks; list next to or indicate on your plot)

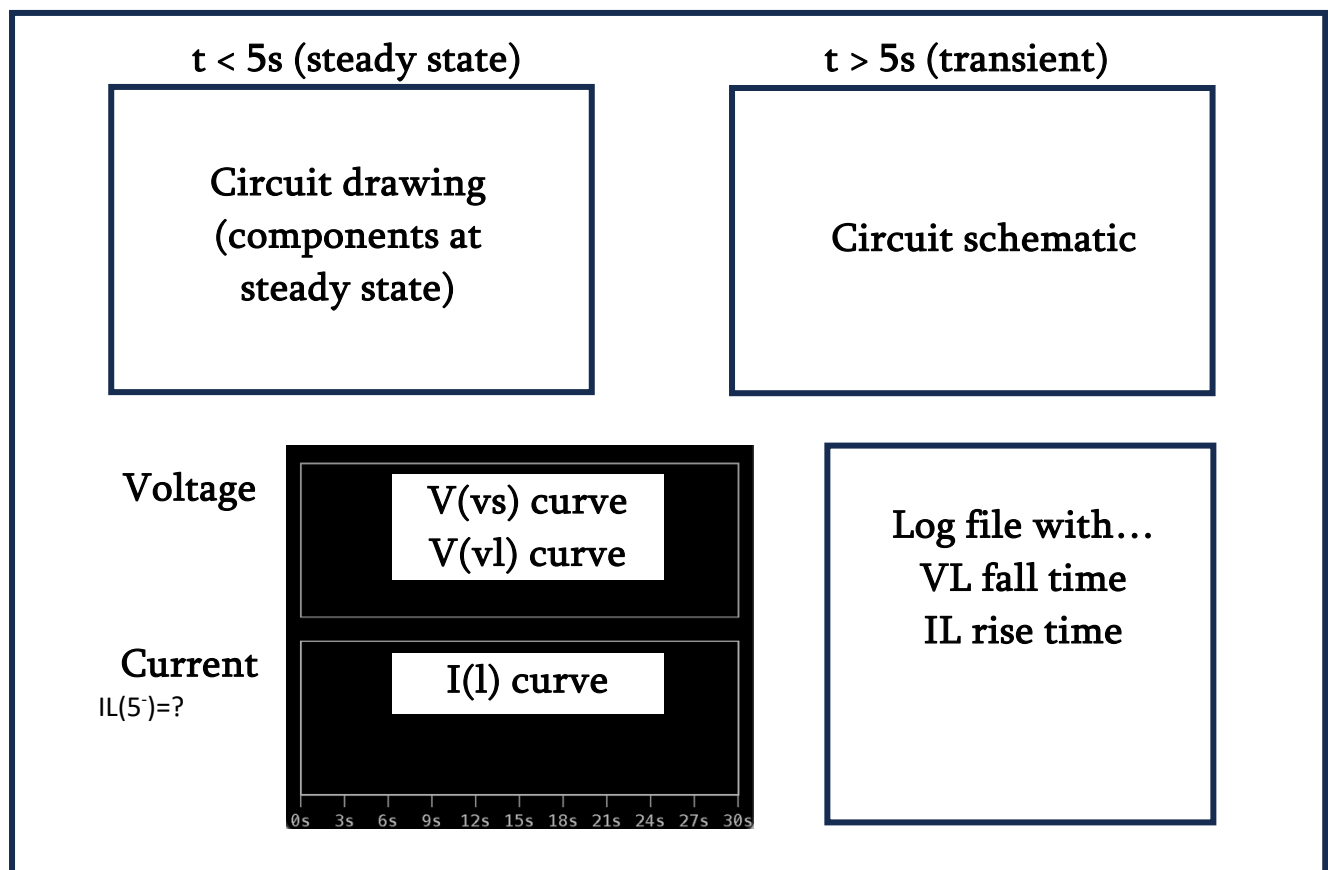

Part 4: RLC Circuit

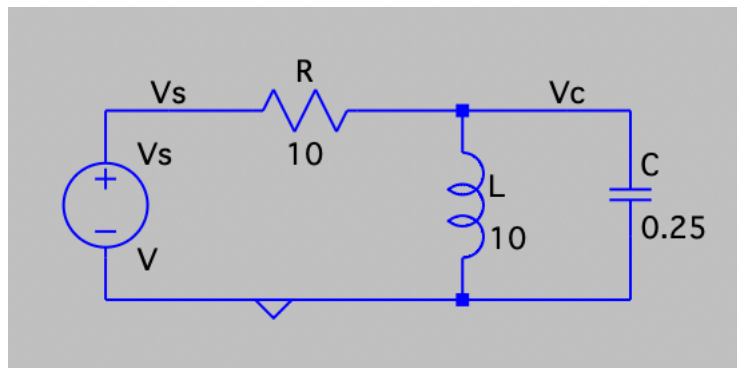

Pictured above is an RLC circuit (problem 2 in HW9) with voltage source V_s , resistor R , capacitor C , and inductor L . The node between V_s and R is labeled as V_s . The node between R , L , and C is labeled as V_c (voltage across both the inductor and capacitor, which are in parallel).

- ☐ Before $t = 5s$, $V_s = 1V$ (for a “long” time = steady state)
- ☐ At $t = 5s$, V_s changes to $5V$
- ☐ $R = 10$ ohms
- ☐ $L = 10$ H
- ☐ $C = 0.25$ F

→ **Simulate the node voltages V_s and V_c , and the currents I_R (left to right), I_L (down), and I_C (down)**

8. Build the circuit schematic shown above

- 8.1. For the source value of V_s , replace V with **PULSE(1 5 5 0.1 0.1 30 30 1)** (same as before)
- 8.2. Make sure the nodes are labeled accordingly.

9. Run the transient simulation

- 9.1. Add a SPICE directive to measure the transient response for 30s: **.tran 30s**
- 9.2. Run the simulation. Right click inside the empty simulation pop-up window and select “**Add plot pane.**” This will split the simulation window into two plots.
- 9.3. In the top plot, add the voltage traces for nodes V_s and V_c : **V(vs), V(vc)**.

9.3.1. Right click the y axis and set the following parameters:

Vertical Axis Manual Plot Limits	
Top:	5V
Tick:	2V
Bottom:	-1V

9.4. In the bottom plot, add the current traces for the resistor, inductor, and capacitor currents: **I(R), I(L), and I(C).**

9.4.1. The default y axis values should be okay, but you can change them if you want.


10. Find the rise times of IR and IL, and fall times of VC and IC

10.1. Using similar **.meas** SPICE directives as in the RC and RL circuits, find the specified rise and fall times. You can hover your cursor over the curves to estimate each final value, and then enter just above/below that for your **.meas** statement. In each **.meas** statement, use “**cross=last.**”

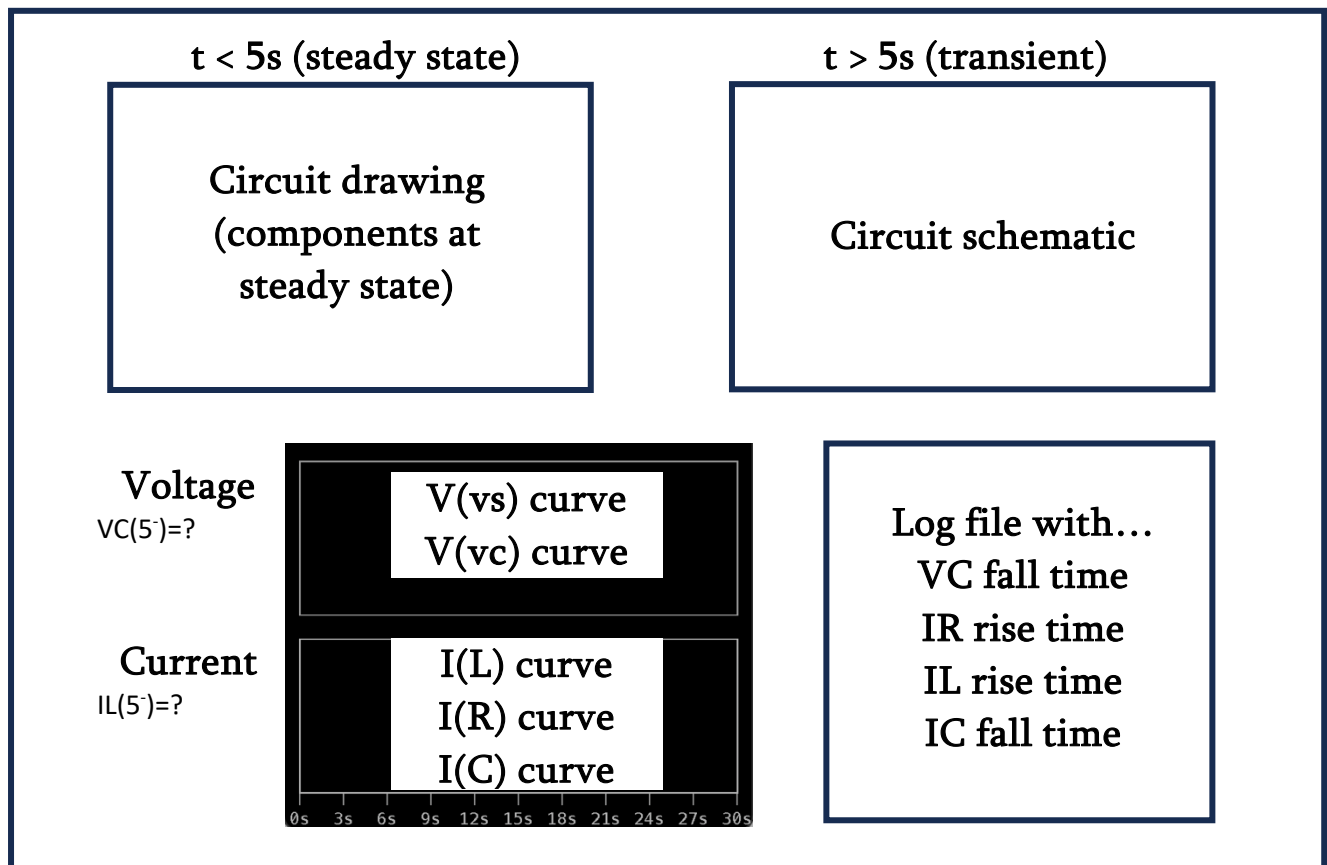10.2. Re-run the simulation and open the log file to check your results.

In your lab report, include the following (matching the format below)...

- ☐ Your circuit schematic in the $t > 5s$ box
- ☐ Draw the steady state circuit for $t < 5s$ (remember what inductors/capacitors act like at steady state).
- ☐ The direction of the simulated currents, shown on the schematics.
- ☐ Your voltage plot (with **V(vs)**, **V(vc)**) and current plot (with **I(R)**, **I(L)**, and **I(C)**).
- ☐ The log file including the indicated rise and fall times.
- ☐ The inductor current at $t = 5^-$ (think $IL(0^-)$ in the homeworks; list next to or indicate on your plot)
- ☐ The capacitor voltage at $t = 5^-$ (think $VC(0^-)$ in the homeworks; list next to or indicate on your plot)



LAB REPORT DUE NEXT WEEK

LAB REPORT 8 – RUBRIC


































































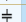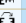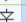
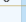


















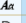



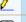












2,000-word limit 1 report per person

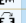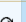Submission contents listed briefly below, but double check the black box for each section!

Part	Submission Material	Points
	Introduce and define concept (transient analysis)	2.5
	Motivation for experiment	2.5
1	R Circuit	15
	Two schematics	5
	Voltage and current plots	5
	Specified voltage/current values	5
2	RC Circuit	20
	Two schematics	5
	Voltage and current plots	5
	Log file	5
	Specified voltage/current values	5
3	RL Circuit	20
	Two schematics	5
	Voltage and current plots	5
	Log file	5
	Specified voltage/current values	5
4	RLC Circuit	20
	Two schematics	5
	Voltage and current plots	5
	Log file	5
	Specified voltage/current values	5

Appendix

Helpful list of LTspice syntax and shortcuts

COMMANDS		SHORTCUTS	
SPICE Analysis		Schematic and Symbol Editing Modes	
.OP	find the DC operating point	  or  or 	cut/delete 
.TRAN	perform nonlinear transient analysis	 or 	copy/duplicate* 
.AC	perform small signal AC analysis		move* unselected wires remain 
.DC	perform DC source sweep analysis		drag* connected wires adjust 
.TF	find the DC small-signal transfer function		exit current mode or right-click 
.NOISE	perform noise analysis	Zoom and Grid	
SPICE Directives			
.BACKANNO	annotate subcircuit pin names on port currents	Zoom in and out with scroll wheel or track pad pinch	
.END	end of netlist		
.ENDS	end of subcircuit definition	Schematic zoom area (drag over area) zoom in (click on scheme)	
.FOUR	compute fourier component		
.FUNC	user defined functions		
.FERRET	download a file from URL		
.GLOBAL	declare global nodes		
.IC	set initial conditions	Waveform zoom area is default mode (F9) for previous zoom	
.INCLUDE	include file		
.LIB	include library		
.LOADBIAS	load a previously solved DC solution		
.MACHINE	arbitrary state machine		
.MEASURE	evaluate user-defined electrical quantities	toggle grid	
.MODEL	define a SPICE model	Tricks	
.NET	compute network parameters in .AC analysis	Waveforms	
.NODESET	supply hints for initial DC solution		
.OPTIONS	set simulator options	when clicking waveform label	
.PARAM	user-defined parameters	click	click
.SAVE	limit the quantity of saved data	 click	 click
.SAVEBIAS	save operating point to disk	 click	 click
.STEP	parameter sweeps	Schematics	
.SUBCKT	define a subcircuit		
.TEMP	temperature sweeps	 click	 click
.TEXT	user-defined string	hold 	hold 
.WAVE	write selected nodes to a .WAV file	 	 
any text preceded by an underscore, e.g. "_FAULT" is displayed with an overbar, active low, signal		any text preceded by an underscore, e.g. "_FAULT" is displayed with an overbar, active low, signal	
Place Component Modes*		*Rotate and Mirror	
	Press  or right-click to exit place component mode		*enabled in place modes
	 resistor 		 rotate 
	 capacitor 		 mirror 
	 inductor 	Undo/Redo	
	 diode 		### Levels of Undo
	 ground 		undo 
	 voltage 		redo 
	 spice directive right-click text field to open "Help me Edit" dialog 		redo 
	 text/comment 	NUMBERS	
	 component 	Prefixes (Case Insensitive)	
	 draw wire 	LTspice	Means
	 label net 	T or t	tera 10 ¹²
	 bus tap 	G or g	giga 10 ⁹
		meg	mega 10 ⁶
		K or k	kilo 10 ³
		M or m	milli 10 ⁻³
		U or u	micro 10 ⁻⁶
		N or n	nano 10 ⁻⁹
		P or p	pico 10 ⁻¹²
		F or f	femto 10 ⁻¹⁵
		Constants	
		LTspice	Means
		e	Euler's number
		pi	π
		k	Boltzmann constant
		q	charge constant
		true	1
		false	0
		mil	25.4×10 ⁻⁶ m