

ECE124: Discussion

Discussion #7

Yeonsik Noh, PhD

Minimization via K-Maps


To obtain minimized SOP expression for a Boolean function F...

- Step1: Translate truth table to K-map
- Step2: Cover all 1's in the smallest number of largest blocks
- Step3: Extract one product term for each block
- Step4: Sum of extracted product terms=minimized SOP expression!

3.1 Simplify the following Boolean functions, using three-variable K-maps:

(a) $F(x, y, z) = \sum (0, 2, 4, 5)$


$$\cancel{xy'} + \cancel{xz'}$$

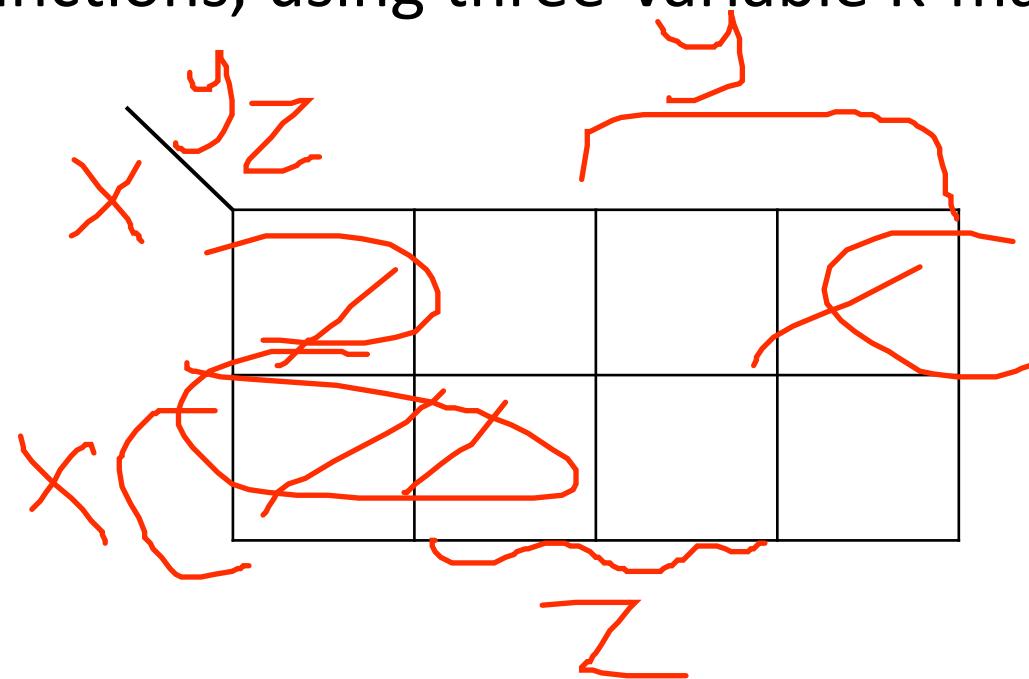

3.1 Simplify the following Boolean functions, using three-variable K-maps:

(b) $F(x, y, z) = \sum (0, 2, 4, 5, 6)$


$$F = \bar{z}' + x\bar{y}'$$

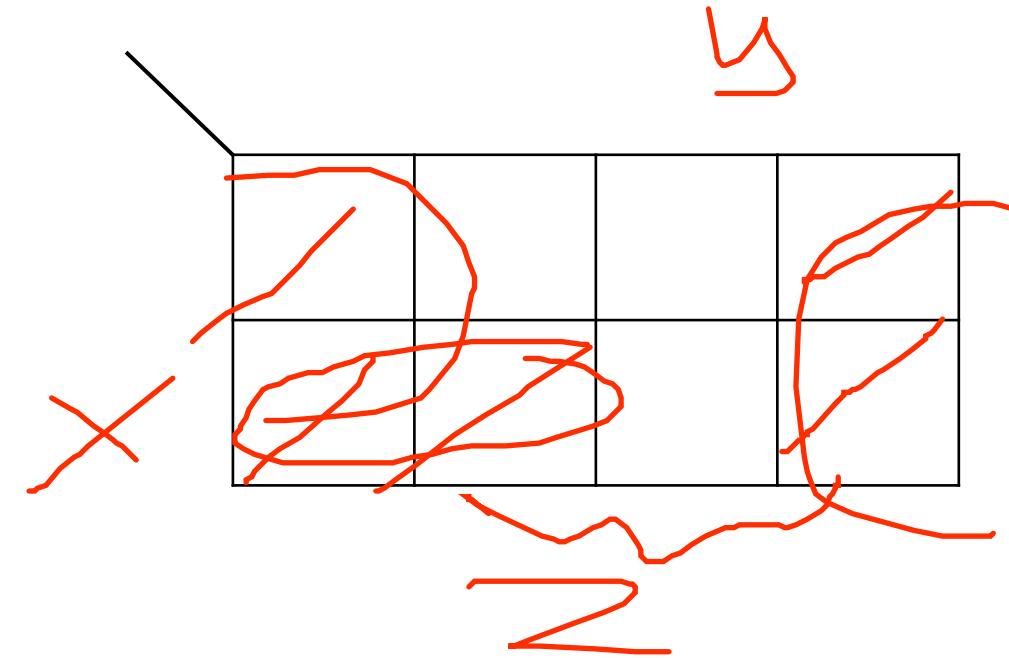

3.1 Simplify the following Boolean functions, using three-variable K-maps:

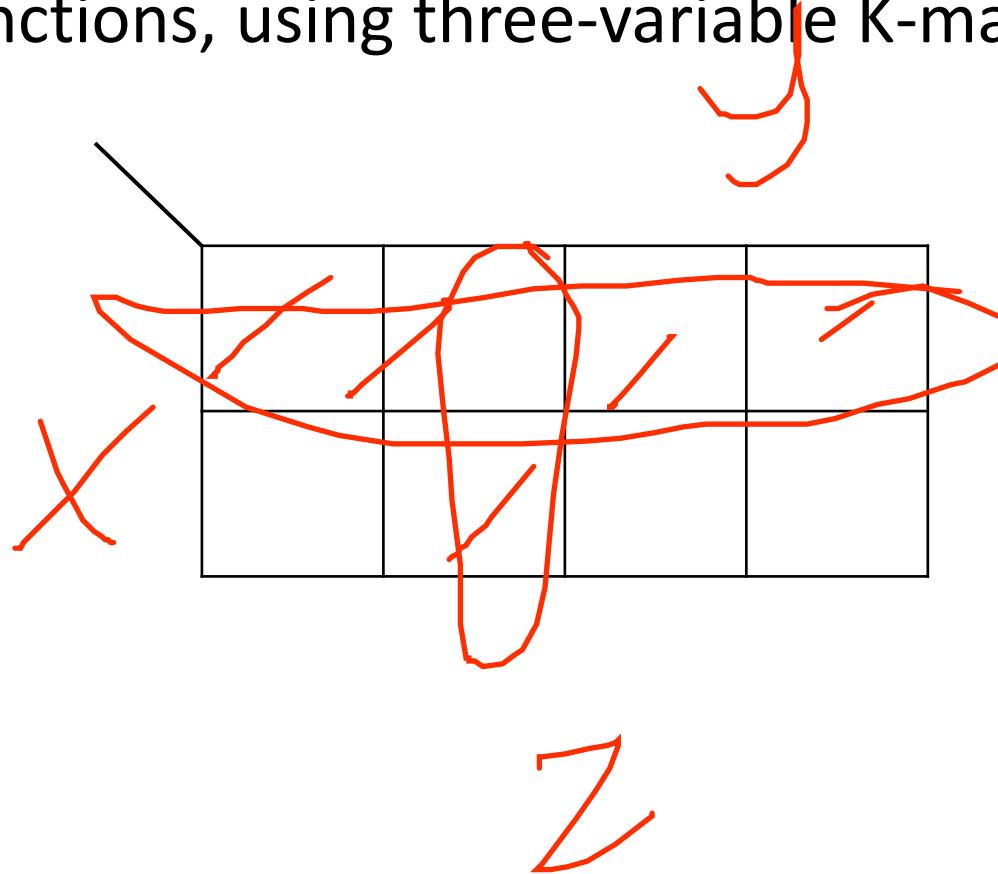(c) $F(x, y, z) = \sum (0, 1, 2, 3, 5)$


$$F = \overline{x} \cdot \overline{y} + x \cdot \overline{y} \cdot z$$



3.1 Simplify the following Boolean functions, using three-variable K-maps:

(d) $F(x, y, z) = \sum (1, 2, 3, 7)$

$$f = x'z + yz + x'z$$

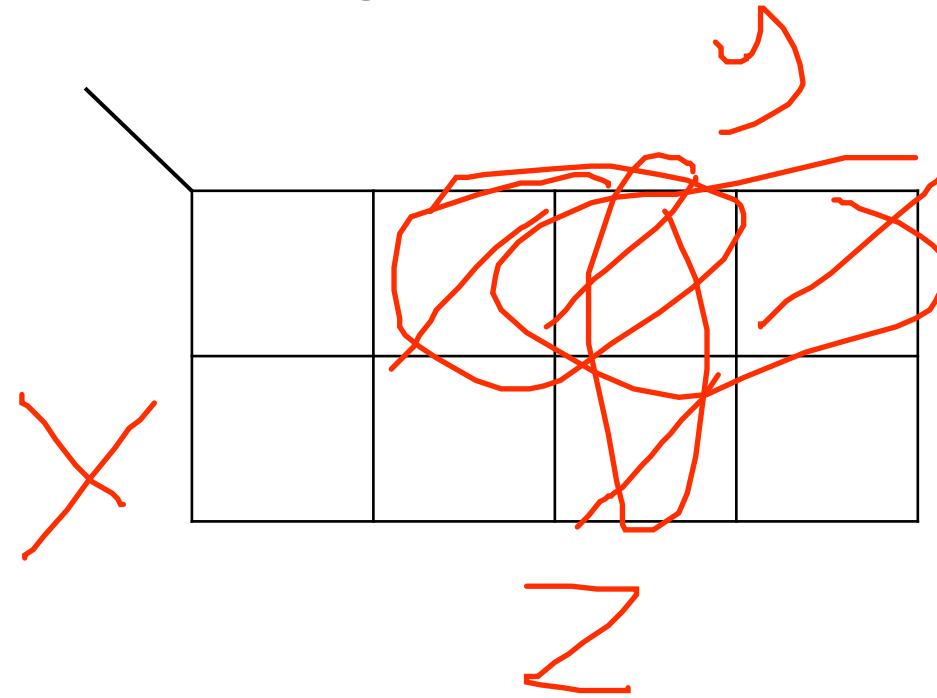

- 1(b). Boolean expression for F.

	m_1		m_2
m_4		m_7	
m_8	m_3		m_{14}
	m_1	m_4	

* All minterms are exclusive.

$$\begin{aligned}
 F &= m_1 + m_2 + m_4 + m_7 + m_8 + m_{11} + m_{13} + m_{14} \\
 &= u'x'y'z + u'x'y'z' + u'xy'z' + u'xyz + u'x'y'z' + u'xyz + ux'y'z + ux'yz' + ux'yz' \\
 &\stackrel{\textcircled{1}}{\underset{=}{\text{L}}} \quad \stackrel{\textcircled{1}}{\underset{=}{\text{L}}} \\
 &= u'x'(y'z + yz') + u'x(y'z' + yz) + ux'(y'z' + yz) + ux(y'z + yz') \\
 &\stackrel{\textcircled{2}}{\underset{=}{\text{L}}} = (u'x' + ux)(y'z + yz') + (u'x + ux')(y'z' + yz) \\
 &= \frac{(u \oplus x)'}{A'} \left(\frac{y \oplus z}{B} \right) + \frac{(u \oplus x)}{A} \left(\frac{y \oplus z}{B'} \right)
 \end{aligned}$$


$$\begin{aligned}
 * A \oplus B &= A'B + AB' \\
 (\underline{A \oplus B})' &= A'B' + AB \\
 &= A \odot B
 \end{aligned}$$

$$\begin{aligned}
 * A'B' + AB &\neq 1 \\
 \text{if, } A=B &\rightarrow A'B' + AB = 1 \\
 &= (u \oplus x) \oplus (y \oplus z) \\
 &= \underline{u \oplus x \oplus y \oplus z}
 \end{aligned}$$


- 1(c). Draw a logic diagram for F.

$$F = u \oplus x \oplus y \oplus z$$


i)

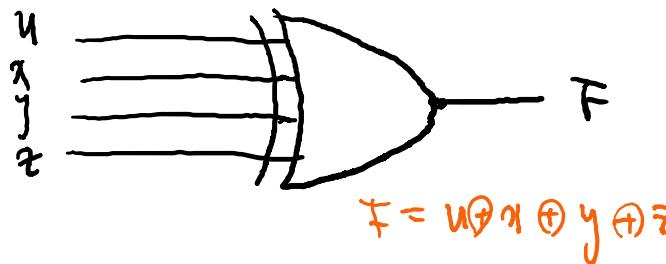

ii)

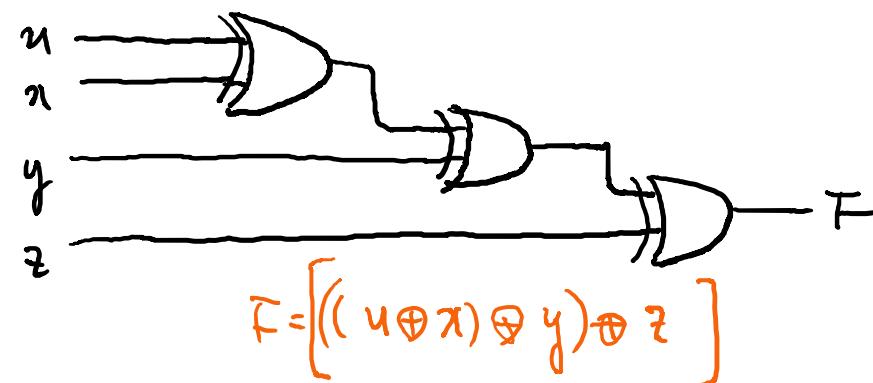


iii)

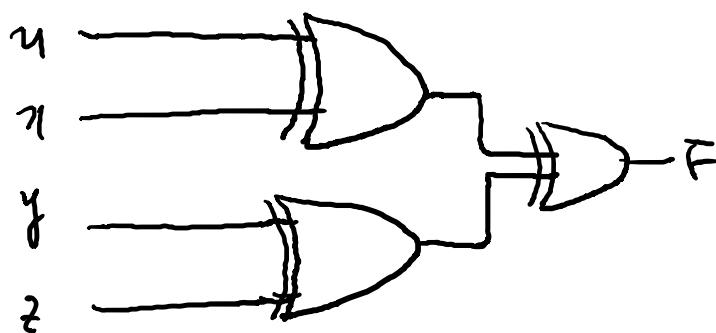

$$F = (u \oplus x) \oplus (y \oplus z)$$

iv)

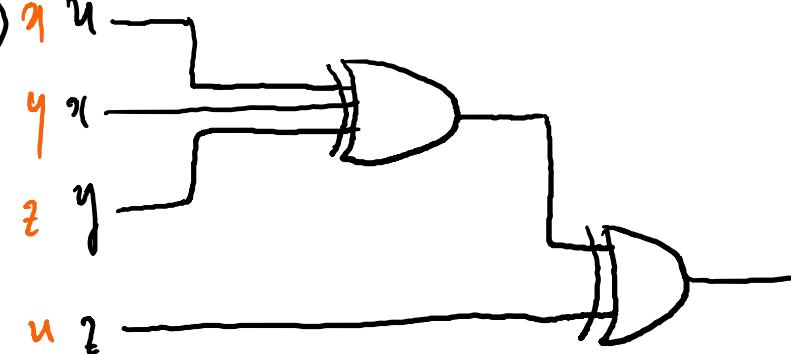


$$\begin{aligned} F &= (u \oplus x \oplus y) \oplus z \\ &= u \oplus (x \oplus y \oplus z) \end{aligned}$$

- 1) Consider the Boolean function: $F(A, B, C, D) = AB + B'C + ACD + ABD' + ACD'$
- 2) Extract a minimized Boolean expression for F using the Karnaugh map of 1).
- 3) Simplify the Boolean expression F and Compare it with the minimized Boolean expression of 2)

$$F = AB + B'C + ACD + ABD' + ACD'$$

$$AB(1+D') + AC(D+D') + B'C$$

$$AB + AC + B'C$$

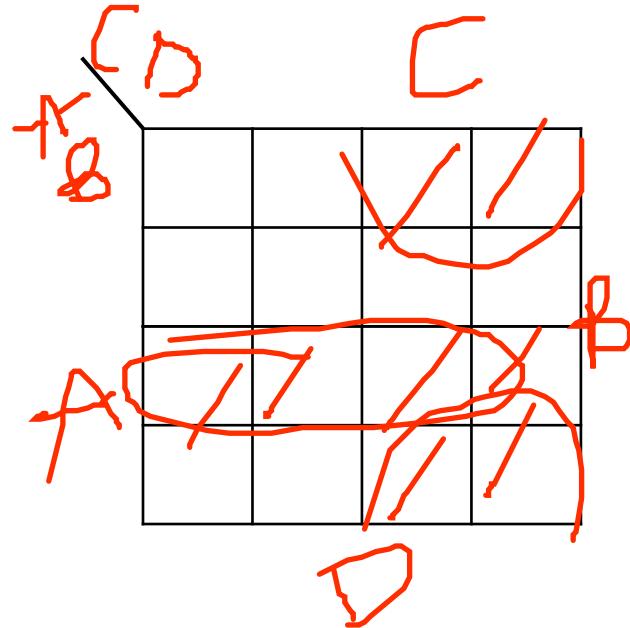

$$F = AB + B'C$$

ABCD	abcd	$AB'CD$
1100	1010	0010
1101	1011	0011
1110	1110	1010
1111	1111	1011

consensus

$$AB + AC + B'C$$

$$(A+B)(A+C)(B'+C)$$

$$x'y + yz + xz$$

$$A'B + (B+B')AC + B'C$$

$$AB + ABC + AB'C + B'C$$



$$AB(1+C) + B'C(A+1)$$

- 2(a). Consider the Karnaugh map for F together with the don't care conditions, d. Show the Karnaugh map for G.


$$F(u, x, y, z) = \sum(0, 2, 5, 7, 10, 15)$$

$$d(u, x, y, z) = \sum(1, 3, 4, 6, 11, 13)$$

$$G(u, x, y, z) = F + d$$

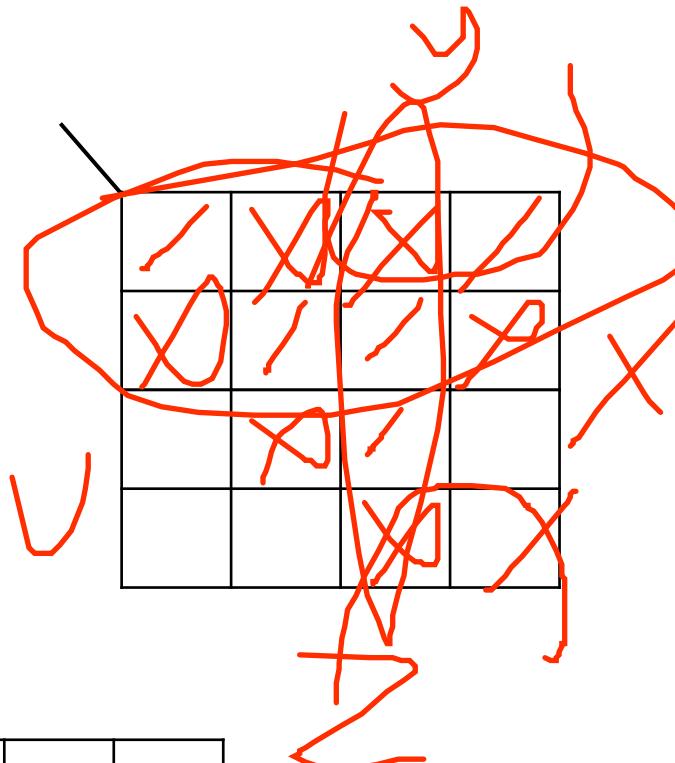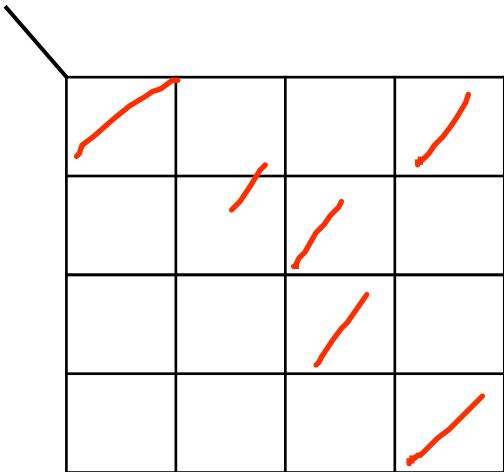


$$F = u' + yz + x'y$$

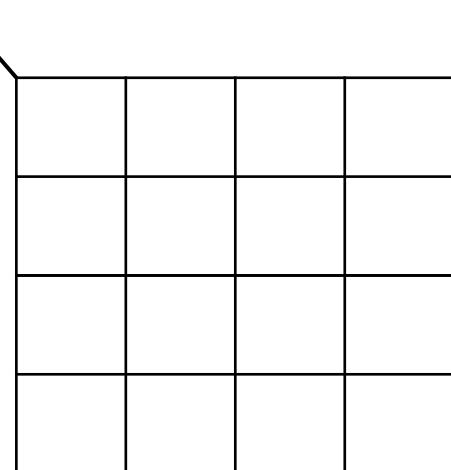

3.15 Simplify the following Boolean function F, together with the don't care conditions d, and then express the simplified function in sum-of-minterms form:


$$(d) F(A, B, C, D) = \Sigma(4, 12, 7, 2, 10)$$

$$d (A, B, C, D) = \Sigma(0, 6, 8)$$

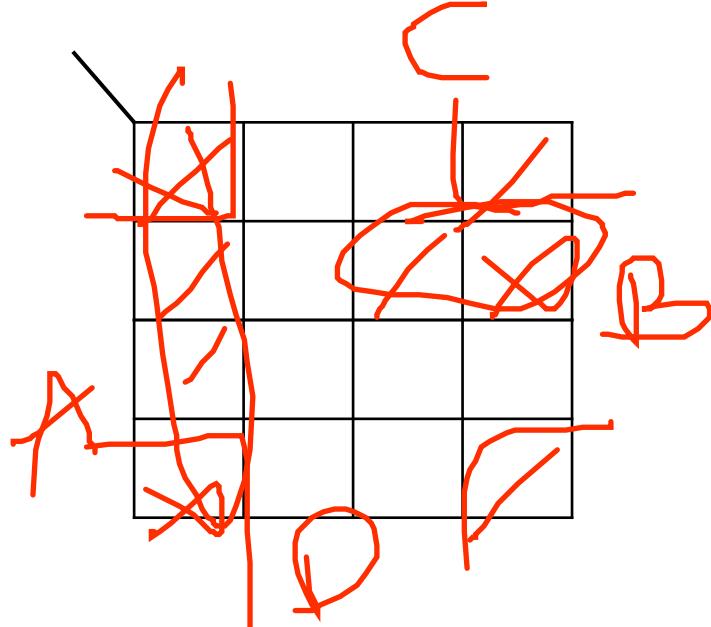

$$F = B'D' + C'D' + A'BC$$

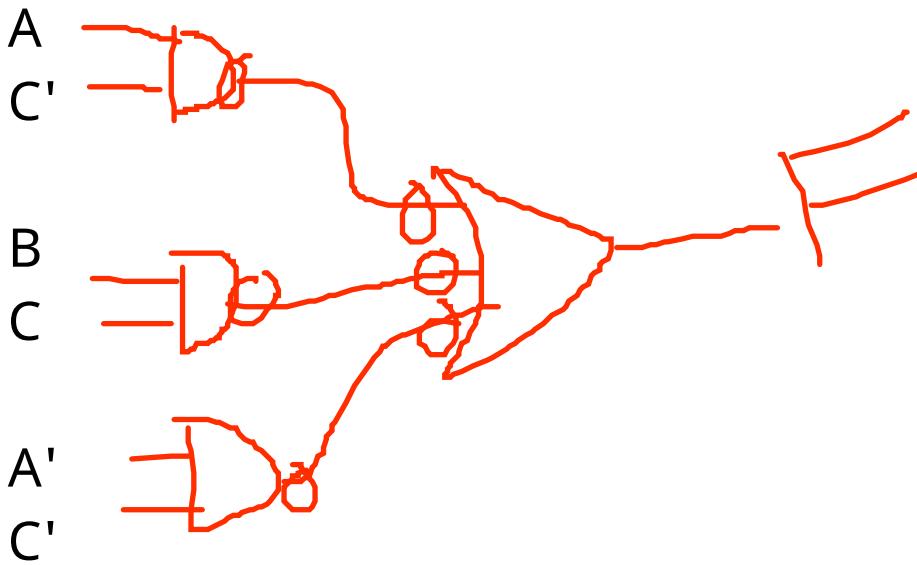
- Convert the Boolean expression $F=AC' + BC + A'C'$ to only NAND gates.



$$F = AC' + BC + A'C'$$

$$F = (F')' = \{(AC' + BC + A'C')\}' = \{(AC')'(BC)'(A'C')'\}'$$

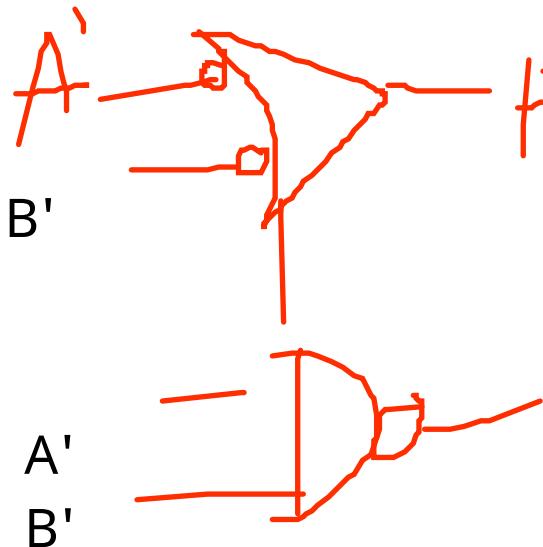
- Draw a logic diagram for $F = A + B$ using only NAND gates.



$$F' = (A + B)'$$


$$F = (A'B')'$$

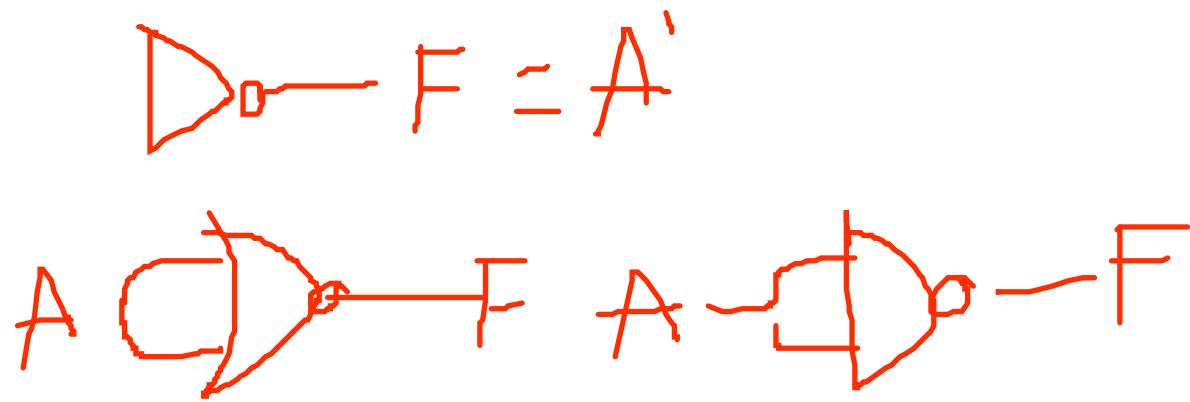- Draw a logic diagram for $F=A'$ using only NOR gates.



X	Y	NOR	NAND
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

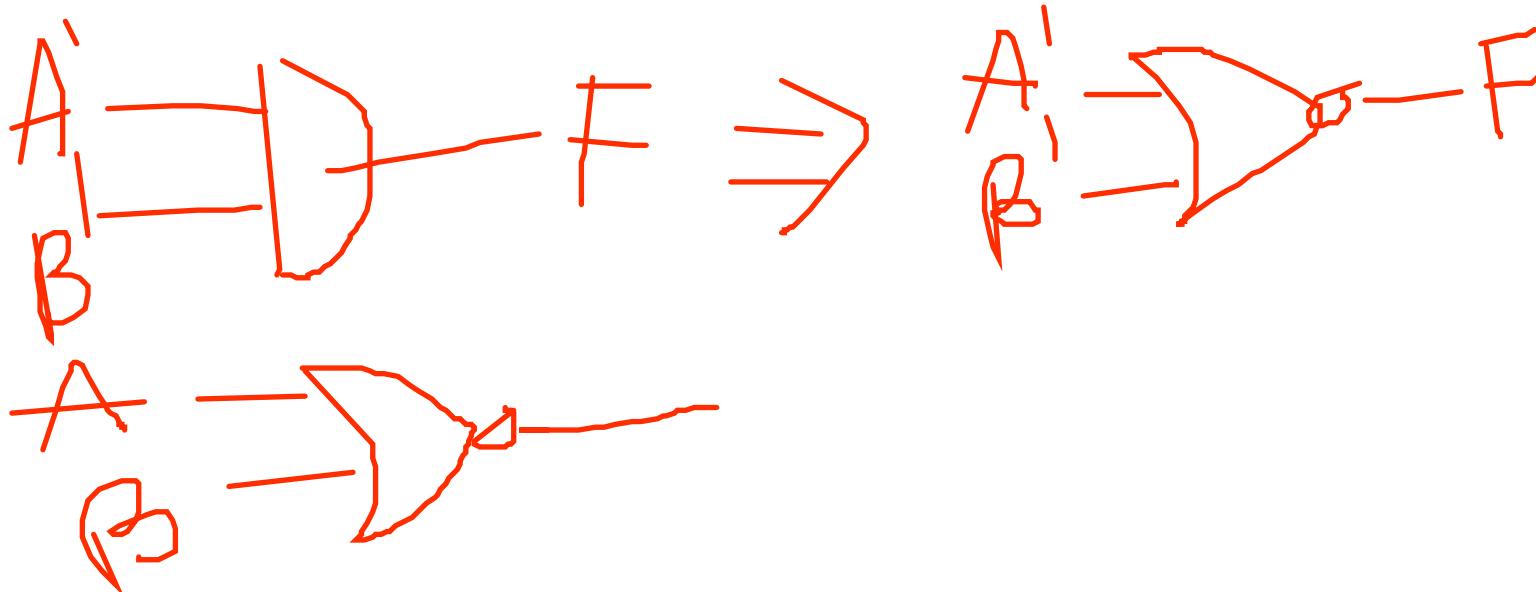- Draw a logic diagram for $F=AB$ using only NOR gates.




$$\begin{aligned}A'B' &= (A+B)' \\F &= (A'+B')'\end{aligned}$$

3.21 Draw (a) the multiple-level NAND circuit for the following expression and (b) repeat (a) for a NOR circuit.

$$w(x + y + z) + xyz$$

$$X+Y+Z = (X'Y'Z')'$$
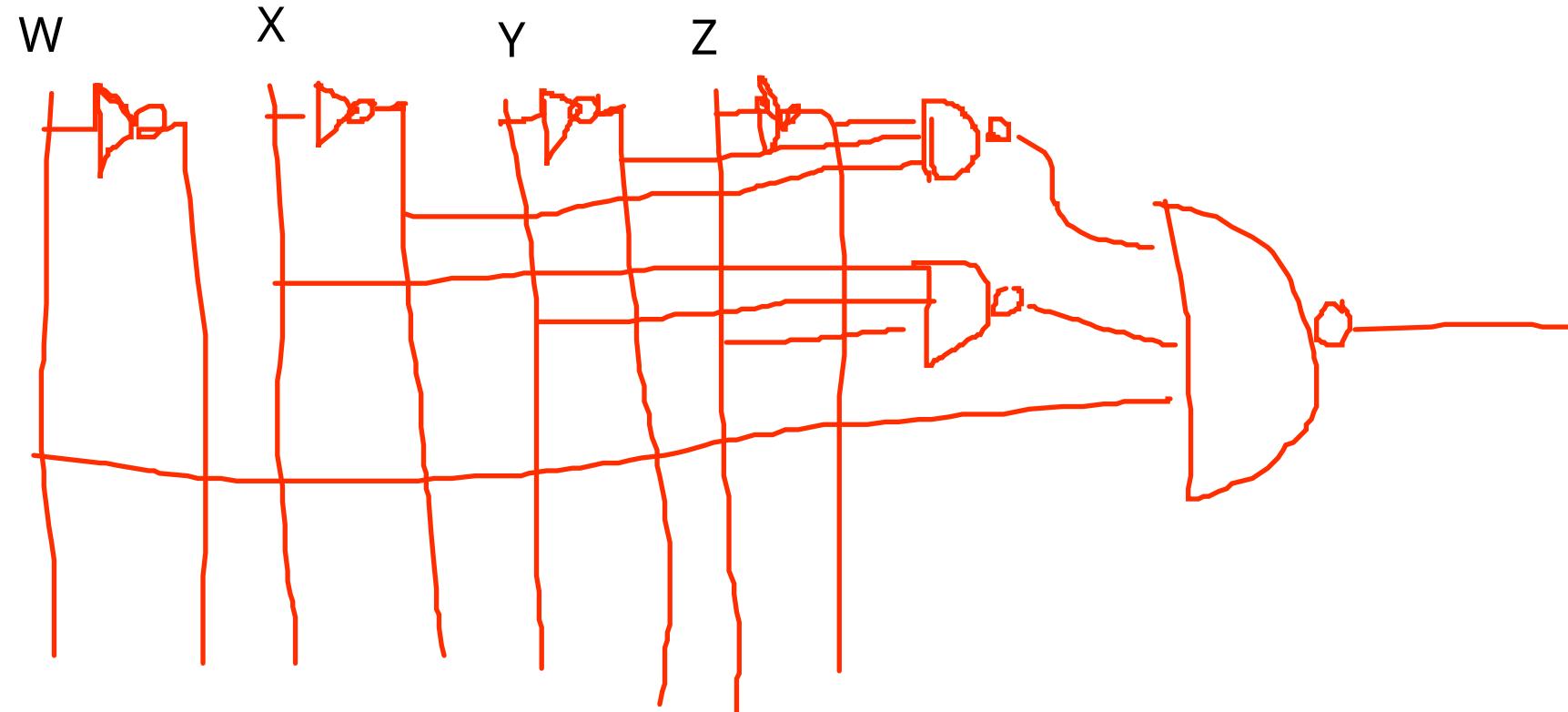
$$W(X'Y'Z')' + xyz = (W(X'Y'Z')'(XYZ))'$$



3.21 (b) repeat (a) for a NOR circuit.

$$w(x + y + z)' + xyz$$

$$W(X+Y+Z) = (W' + (X+Y+Z)')'$$

$$xyz = (X'+y'+z')'$$

$$(W' + (X+Y+Z)')' + (X'+y'+z')'$$

