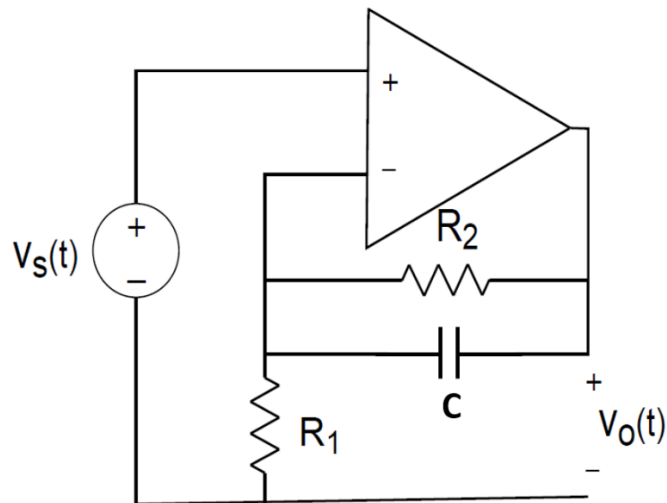


Homework 5

Problem 1 (4 pt)

Find the differential equation for v_o in the opamp circuit below (You don't need to solve the equation). Assume the opamp is ideal with infinite gain.




Problem 2 (5 pt)

The circuit below is a model of a MOS common drain amplifier where v_s is the input voltage and v_o is the output.


a) Find the differential equation for v_o . (3 pt)

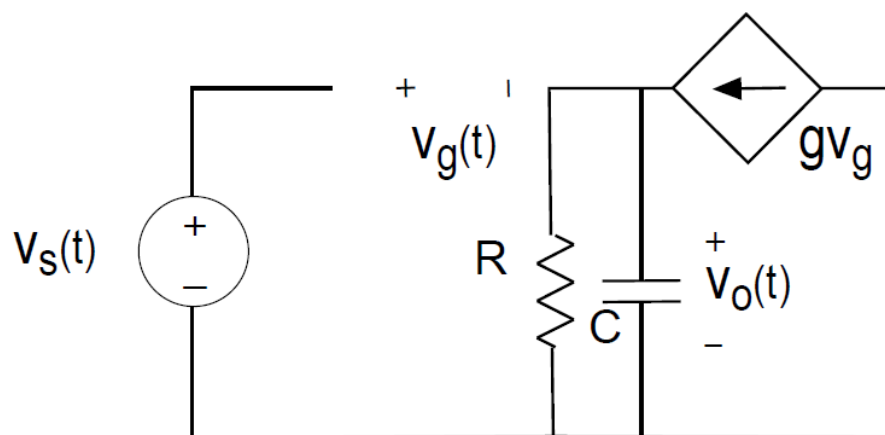b) If $v_o(0) = 0$ and if $v_s(t) = 1$ V for $t > 0$, what is the solution for $v_o(t)$ for $t > 0$. (Consider R , C , g are known; **note** that V_g is not known) (2 pt)



Problem 3 (5 pt)

In the circuit below, $R_1 = 1 \text{ K}\Omega$, $R_2 = 2 \text{ K}\Omega$, and $C = 3 \text{ }\mu\text{F}$. Assume the initial rest conditions (namely v_1 has been 0 V for a long time), and assume that v_1 has a 6-volt step at $t = 0$ (namely it jumps from 0 to 6 V). Find $v_2(t)$ for $t > 0$. Show the details (4 pt). Also please sketch $v_2(t)$ (1 pt).

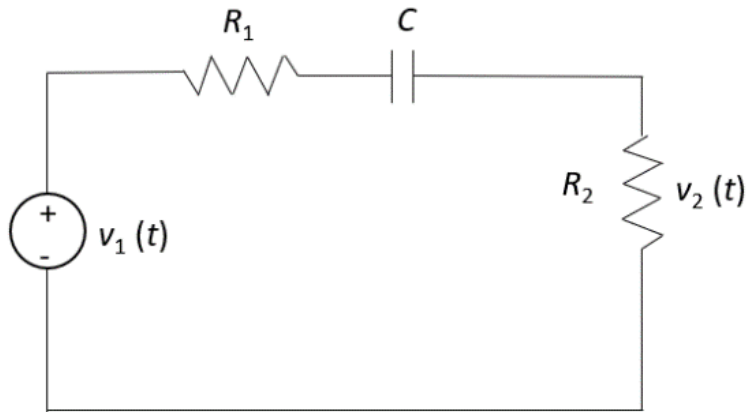**Problem 4** (6 pt)

In the circuit below, R_1 , R_2 , C_1 , C_2 and V_o are known. Assume that the switch has stayed at **1** for a long time and now at $t = 0$ moves from 1 to 2. Find $v(t)$ for $t > 0$.

