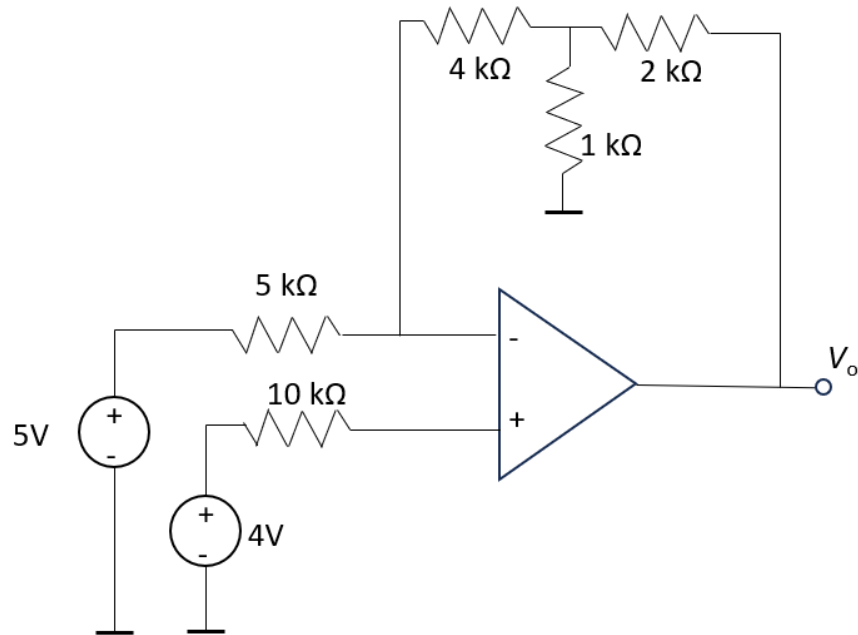


Homework 6

Problem 1 (10 pt) In the following OpAmp circuit, find the numerical output of V_o (provide detailed process).



Problem 2 (10 pt) In the following OpAmp circuit, suppose R_1 , R_2 , R_3 , R_4 , I_1 , I_2 and V_1 are known. Find V_o in terms of these known parameters (provide detailed process).

