

# UMass ECE 210 – Fall 2023

---

## Lab 10: LTSpice – Diodes

### GOALS:

- ☐ Simulate and analyze diode-based circuits
- ☐ Understand how to characterize diode turn-on voltage and on/off characteristics (voltage and current)

### Lab report:

1. Introduce justification for experiment.
  - a. Analyze diode-based circuits via simulation
2. Properly label and document simulation schematics and simulation results
  - a. Label components, interesting nodes
  - b. Label simulation output plots
  - c. Label specified values

**You will need to **RECORD** all of your data independently.**

The simulation data required for your lab report are listed in black boxes like this throughout the following parts.

**FOLLOW ALL STEPS AND INCLUDE ALL REQUIRED DATA IN YOUR REPORT!**

## **Introduction: Diodes**

Diodes are useful circuit components that can act as switches (i.e., on or off) and conduct current in only one direction. Since the diode can be on or off, we need to do a few additional steps when analyzing circuits with diodes by hand: we first have to guess whether the diode is on or off, then solve the circuit based on this guess (enforce some condition on the circuit), and finally check to see if the guess was valid. Some details may change depending on how we model the diode, but they will generally follow the table below.

The main parameter of interest is the diode turn-on voltage – when the voltage across the diode equals this value, it is on and conducts current. If the voltage across the diode is less than this value, then the diode is off and does not conduct current (it acts like an open circuit).


For a diode with turn-on voltage = 0.7 V...

Diode Mode	Enforce	Check
ON	$V_{\text{diode}} = 0.7 \text{ V}$	$I_{\text{diode}} > 0 \text{ A?}$
OFF	$I_{\text{diode}} = 0 \text{ A}$	$V_{\text{diode}} < 0.7 \text{ V?}$

When simulating diode-based circuits, however, we will not need to guess and check the mode. Instead, we will use the simulations to characterize the diode voltage/current in on and off modes, and look at how the mode is affected by other circuit components.

Reference Lab 3 and Lab 8 as you work to remind yourself of how to use LTSpice. Nothing new will be introduced in terms of LTspice, so use this as an opportunity to help you better understand diodes in conjunction with the homework (and practice using LTspice).
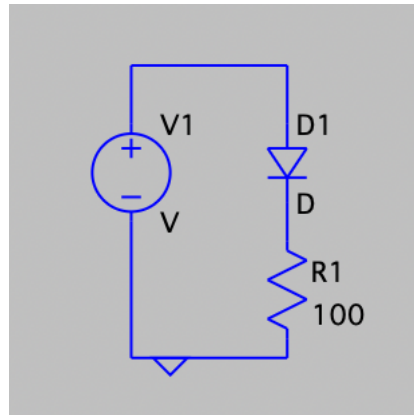
## **Part 1: Identify Diode Turn-on Voltage**



Pictured above is a simple circuit with a DC voltage source V1, diode D1, and 100ohm resistor R1. The bottom of the circuit is grounded. The main characteristic of a diode (for our purposes) is the voltage that causes it to turn on and conduct current (turn-on voltage). We will use this circuit to identify the turn-on voltage.

→ **Simulate the voltage across and the current through the diode**

**Voltage polarity: + on top;      Current direction: + to – (down)**

→ **Identify the approximate turn-on voltage**

### **1. Build the circuit schematic shown above**

- 1.1. For the diode, type **diode** into the component search menu and place the default option that comes up. You do not need to edit any parameters.
- 1.2. For the source value of V1, we will do a DC sweep.
  - 1.2.1. Write a SPICE statement to sweep **the value of V1 from 0 to 1.5V**, with **0.01V step**
- 1.3. Label the two unlabeled nodes (i.e., between V1 and D1; between D1 and R1). Just make it so the labels are understandable for your simulation legend.

### **2. Run the DC simulation**

- 2.1. Add another SPICE statement **.op** in addition to your sweep statement.
- 2.2. Run the simulation. Plot the diode voltage and current in the same plot.

### **In your lab report, include the following...**

- ☐ Your circuit schematic (with labeled nodes!)
- ☐ Simulation plot with diode voltage and diode current
- ☐ Using the table on page 1 to help define on/off, what is the turn-on voltage for this diode?
  - You can be approximate and read from the plot, or use a .meas statement!

## **Part 2: Rectifier Circuits**

A useful application of diodes is to convert an AC signal to DC – these are called rectifiers. A simple AC signal (e.g., a sine wave) will alternate between positive and negative voltages (and thus forward/reverse-going current). We can use diodes to “rectify” the AC signal into an entirely positive voltage signal with forward-going current. Depending on the amount and configuration of diodes, we can build different types of rectifier circuits.

→ **Simulate a half-wave rectifier (using the same circuit schematic from part 1)**

→ **Identify the approximate turn-on voltage**

### 1. Change some values

1.1. For the source value of V1, change the value to **SINE(0 5 100)**

1.1.1. V1 is now a 100Hz sine wave with  $V_{\text{peak}} = 5 \text{ V}$

1.2. Delete your SPICE directives (**.op, DC sweep, etc.**)

1.3. Add a SPICE directive to measure the transient response for 40ms: **.tran 0.04s**

1.3.1. This will include 4 periods of V1

### 2. Run the transient simulation

2.1. Separate the simulation window into two plot panes.

2.1.1. In one pane, plot the diode current and diode voltage.

2.1.2. In the other pane, plot the source voltage V1 and the voltage across resistor R1.

In your V1/resistor plot, you should see the entire V1 sine wave, but only the positive halves of this sine wave for the resistor voltage. When V1 goes negative, the resistor voltage goes to 0V.

If we treat the resistor voltage as our output and V1 as our input, then we are only outputting the positive parts of V1, i.e., we are rectifying *half* the input signal! The slight mismatch in voltage is coming from the voltage drop across R1. More diodes (in a specific configuration) could be used to rectify the negative halves into positive halves – this would be a full-wave rectifier.

From your diode voltage/current plot, you can see when the diode is off (current = 0A; voltage < turn-on value). You can also see when the diode is on (voltage  $\approx$  turn-on value; current > 0A).

### 3. Check the turn-on voltage

3.1. In the diode voltage/current plot, what is the turn-on voltage, approximately?

3.1.1. You can indicate this on the plot, or with a .meas statement. It should be similar to the turn-on voltage from part 1 (no comparison needed).


3.2. In the V1/resistor voltage plot, you should be able to see a mismatch between the two voltages. In particular, the resistor voltage starts rising after V1. Why?

3.2.1. This should be a simple answer – think about the diode switching between on/off. What must happen for the resistor voltage to start rising?

3.2.2. You should indicate a value on the diode voltage/current plot or use a .meas statement to prove this (e.g., what is the value of V1 once resistor voltage starts changing?)

**In your lab report, include the following...**

- ☐ Your circuit schematic (nodes labeled!)
- ☐ Simulation plot with diode voltage and diode current
- ☐ Simulation plot with V1 voltage and resistor voltage
- ☐ Diode turn-on voltage – shown by indicating on voltage/current plot OR .meas statement
- ☐ Answer to question – explained using either diode voltage/current plot OR .meas statement

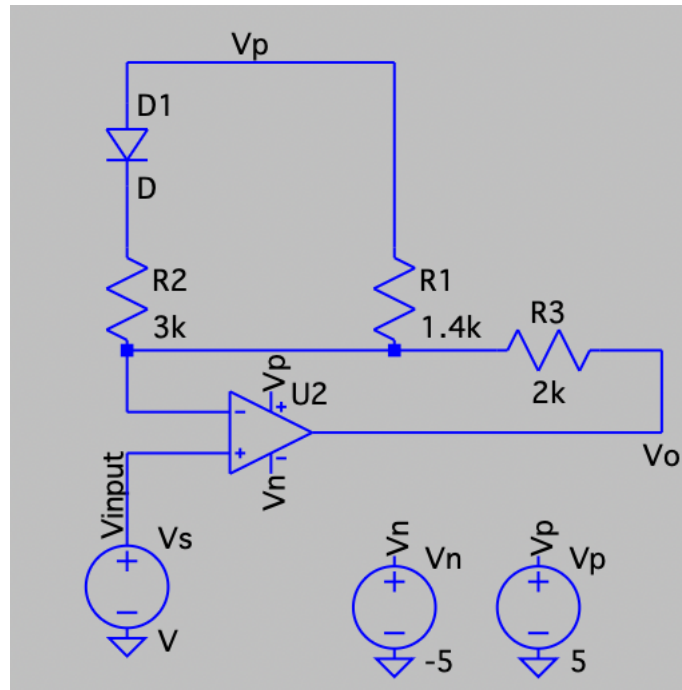**Part 3: Diode + Op-amp Circuit**

Pictured above is an op-amp circuit with a diode and some resistors. Two DC voltage sources,  $V_p$  and  $V_n$ , are built “separate” from the main circuit, but they are just used to supply voltage to the three nodes labeled  $V_p$  or  $V_n$ . This is simply a cleaner way of making the schematic – we essentially have a +5V or -5V source going to each node labeled  $V_p$  or  $V_n$ , respectively.

In this circuit, it turns out that the value of the input voltage source  $V_s$  will determine the diode mode (on or off). We will see what value of  $V_s$  causes the diode to switch modes.

→ Simulate the diode voltage, diode current, and input voltage  $V_s$

→ Identify the  $V_s$  value that causes the diode mode to switch

1. Build the circuit schematic shown above
  - 1.1. For the source value of  $V_s$ , we will do a DC sweep.
    - 1.1.1. Write a SPICE statement to sweep **the value of  $V_s$  from 1 to 6V, with 0.1V step**
  - 1.2. Make sure the nodes are labeled accordingly.
2. Run the transient simulation
  - 2.1. Add a SPICE directive to measure DC values: **.op**
  - 2.2. Run the simulation.
  - 2.3. Plot the diode voltage, diode current, and input voltage  $V_s$ .
3. Identify the diode modes relative to  $V_s$ 
  - 3.1. Based on parts 1 and 2, you should be able to identify when the diode is on/off in the plot.
    - 3.1.1. Indicate on your plot when the diode is on, and when it is off.
  - 3.2. You should also be able to identify what  $V_s$  is when the diode switches modes.
    - 3.2.1. Use a .meas statement to find this value of  $V_s$ . You can base it off of either the diode voltage or the diode current (or use two statements and do both!)

**In your lab report, include the following...**

- ☐ Your circuit schematic (nodes labeled!)
- ☐ Simulation plot with diode voltage, diode current, and  $V_s$  voltage
- ☐ Diode modes shown on the simulation plot
- ☐  $V_s$  value that causes diode to switch modes (exact value shown by a .meas statement)

## LAB REPORT DUE NEXT WEEK

### LAB REPORT 10 – RUBRIC













 

 












 

 



























































**2,000-word limit 1 report per person**

**Submission contents listed briefly below, but double check the black box for each section!**

<b>Part</b>	<b>Submission Material</b>	<b>Points</b>
	Introduce and define concept (transient analysis)	2.5
	Motivation for experiment	2.5
<b>1</b>	Diode turn-on voltage	15
	Schematic	5
	Simulation plot (with specified voltages/currents)	5
	Turn-on voltage value	5
<b>2</b>	Half-wave Rectifier	20
	Schematic	5
	Simulation plots (with specified voltages/currents)	5
	Turn-on voltage value	5
	Plot analysis (answer the question as specified)	5
<b>3</b>	Diode + Op-amp	20
	Schematics	5
	Simulation plot (with specified voltages/currents)	5
	Diode modes (indicated on plot)	5
	Vs value	5

# Appendix

## Helpful list of LTspice syntax and shortcuts

COMMANDS		SHORTCUTS	
SPICE Analysis		Schematic and Symbol Editing Modes	
.OP	find the DC operating point	  or  or  or  or 	 
.TRAN	perform nonlinear transient analysis		
.AC	perform small signal AC analysis		
.DC	perform DC source sweep analysis		
.TF	find the DC small-signal transfer function		
.NOISE	perform noise analysis		
SPICE Directives		Zoom and Grid	
.BACKANNO	annotate subcircuit pin names on port currents	 	
.END	end of netlist		
.ENDS	end of subcircuit definition		
.FOUR	compute fourier component		
.FUNC	user defined functions		
.FERRET	download a file from URL		
.GLOBAL	declare global nodes	TRICKS	
.IC	set initial conditions	Waveforms	
.INCLUDE	include file	 	 
.LIB	include library		
.LOADBIAS	load a previously solved DC solution		
.MACHINE	arbitrary state machine	Schematics	
.MEASURE	evaluate user-defined electrical quantities	 	 
.MODEL	define a SPICE model		
.NET	compute network parameters in .AC analysis		
.NODESET	supply hints for initial DC solution	any text preceded by an underscore, e.g. "_FAULT" is displayed with an overbar, active low, signal	
.OPTIONS	set simulator options		
.PARAM	user-defined parameters		
.SAVE	limit the quantity of saved data		
.SAVEBIAS	save operating point to disk		
.STEP	parameter sweeps		
.SUBCKT	define a subcircuit		
.TEMP	temperature sweeps		
.TEXT	user-defined string		
.WAVE	write selected nodes to a .WAV file		
		Place Component Modes*	
		 	 
			
			
			
			
			
			
			
			
			
			
			
		*Rotate and Mirror	
		 	 
			
		Undo/Redo	
		 	 
			
			
			
		NUMBERS	
		Prefixes (Case Insensitive)	
		LTspice	Means
		T or t	tera 10 <sup>12</sup>
		G or g	giga 10 <sup>9</sup>
		meg	mega 10 <sup>6</sup>
		K or k	kilo 10 <sup>3</sup>
		M or m	milli 10 <sup>-3</sup>
		U or u	micro 10 <sup>-6</sup>
		N or n	nano 10 <sup>-9</sup>
		P or p	pico 10 <sup>-12</sup>
		F or f	femto 10 <sup>-15</sup>
		Constants	
		LTspice	Means
		e	Euler's number
		pi	π
		k	Boltzmann constant
		q	charge constant
		true	1
		false	0
		mil	25.4×10 <sup>-6</sup> m