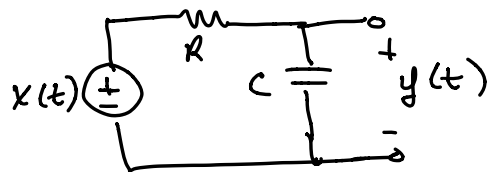


Example 2.4: Find the impulse response $h(t)$ of the RC circuit shown below with $y(0^-) = 0$.



Solution: Kirchhoff's voltage law gives

$$RC \frac{dy(t)}{dt} + y(t) = x(t), \quad (\text{E1})$$

or

$$\frac{dy(t)}{dt} + \frac{1}{RC}y(t) = \frac{1}{RC}x(t). \quad (\text{E2})$$

The impulse response satisfies

$$\frac{dh(t)}{dt} + \frac{1}{\tau_c}h(t) = \frac{1}{\tau_c}\delta(t), \quad (\text{E3})$$

where $\tau_c = RC$ is the time constant.

A zero initial condition means that

$$h(t) = 0, \quad t < 0. \quad (\text{E4})$$

At any time $t > 0$, (E3) becomes

$$\frac{dh(t)}{dt} + \frac{1}{\tau_c}h(t) = 0. \quad (\text{E5})$$

The solution to the homogeneous differential equation (E5) is

$$h(t) = Ce^{-t/\tau_c}, \quad t > 0 \quad (\text{E6})$$

for any constant C .

At any time $t \neq 0$, $h(t)$ is given by (E4) and (E6). Here, only a single value of the constant C satisfies (E3) at all t , including $t = 0$. Integrate (E3) from $t = 0^-$ to $t = 0^+$:

$$\int_{0^-}^{0^+} \frac{dh(t)}{dt} dt + \int_{0^-}^{0^+} \frac{1}{\tau_c} h(t) dt = \int_{0^-}^{0^+} \frac{1}{\tau_c} \delta(t) dt, \quad (\text{E7})$$

or

$$h(0^+) - h(0^-) = C - 0 = \frac{1}{\tau_c}. \quad (\text{E8})$$

Finally, we find

$$h(t) = \frac{1}{\tau_c} e^{-t/\tau_c} u(t), \quad \tau_c = RC. \quad (\text{E9})$$

