

Aidan Chin	compute i(t), v(t), p(t), and the final energy stored in the inductor (after a very, very long time)				
45259					
ECE 202					
t initial (milliseconds)	t final (milliseconds)	V_0 (volts)	R (Ohms)	L (Millihenries)	
0	=10*B9	5	2	10	
t step	tau				
=B7/400	=E7/D7				
		voltage across inductor	power absorbed by inductor	total energy stored in inductor after inf time	final energy stored in inductor
t (ms)	e(-t/tau)	i(t) (amps)	v(t) (volts)	p(t) (watts)	P Final (watts)
=A7	=EXP(-A12/\$B\$9)	=((\$C\$7*(1-B12)))/\$D\$7	=\$C\$7*B12	=C12*D12	=0.5*E7*F14^2
=A12+\$A\$9	=EXP(-A13/\$B\$9)	=((\$C\$7*(1-B13)))/\$D\$7	=\$C\$7*B13	=C13*D13	i(t) when t = inf (amps)
=A13+\$A\$9	=EXP(-A14/\$B\$9)	=((\$C\$7*(1-B14)))/\$D\$7	=\$C\$7*B14	=C14*D14	=\$C\$7/\$D\$7
=A14+\$A\$9	=EXP(-A15/\$B\$9)	=((\$C\$7*(1-B15)))/\$D\$7	=\$C\$7*B15	=C15*D15	measured P Final (watts)
=A15+\$A\$9	=EXP(-A16/\$B\$9)	=((\$C\$7*(1-B16)))/\$D\$7	=\$C\$7*B16	=C16*D16	=0.5*E7*(SUM(E12:E412)/(B7/A9))*10
=A16+\$A\$9	=EXP(-A17/\$B\$9)	=((\$C\$7*(1-B17)))/\$D\$7	=\$C\$7*B17	=C17*D17	Percent Error check of P Final
=A17+\$A\$9	=EXP(-A18/\$B\$9)	=((\$C\$7*(1-B18)))/\$D\$7	=\$C\$7*B18	=C18*D18	=ABS((F12-F16)/F12)*100
=A18+\$A\$9	=EXP(-A19/\$B\$9)	=((\$C\$7*(1-B19)))/\$D\$7	=\$C\$7*B19	=C19*D19	
=A19+\$A\$9	=EXP(-A20/\$B\$9)	=((\$C\$7*(1-B20)))/\$D\$7	=\$C\$7*B20	=C20*D20	
=A20+\$A\$9	=EXP(-A21/\$B\$9)	=((\$C\$7*(1-B21)))/\$D\$7	=\$C\$7*B21	=C21*D21	
=A21+\$A\$9	=EXP(-A22/\$B\$9)	=((\$C\$7*(1-B22)))/\$D\$7	=\$C\$7*B22	=C22*D22	