

RC/RL

- ① 1st order diff. eq., $t > 0$

$$\boxed{\frac{d}{dt}V(t) + A \cdot V(t) = B}$$

- ② Write Solution $t_0, t > 0$


$$\boxed{V(t) = \frac{B}{A} + K e^{-At}}$$

- ③ Find K using initial conditions

- Need $V(0^+)$

- Use $i_L(0^-) = i_L(0^+)$

$$V_c(0^-) = V_c(0^+)$$

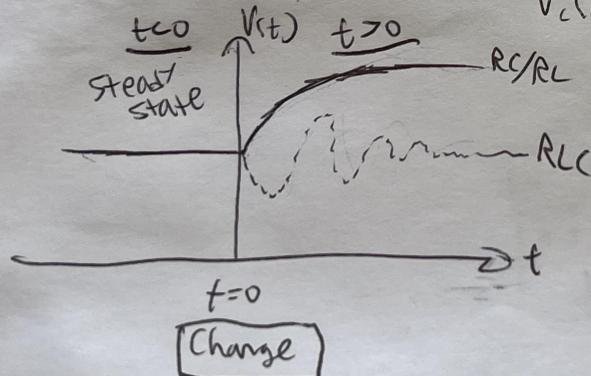

RLC

- ① 2nd order diff. eq., $t > 0$

$$\boxed{\frac{d^2}{dt^2}V(t) + A \frac{d}{dt}V(t) + BV(t) = C}$$

- ② Determine damping

$$2\alpha = A, \quad \omega_0^2 = B$$

$\alpha^2 > \omega_0^2 \rightarrow$ Overdamped

$\alpha^2 < \omega_0^2 \rightarrow$ Underdamped

$\alpha^2 = \omega_0^2 \rightarrow$ Critically damped

- ③ Write Solution $t_0, t > 0$

$$V(t) = \frac{C}{B} + A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

- ③ Find A_1, A_2 Using initial conditions


- Need $V(0^+), \frac{d}{dt}V(0^+)$

- Use $i_L(0^-) = i_L(0^+)$

$$V_c(0^-) = V_c(0^+)$$


Hw9 Q1

- ① Apply op-amp rules
- ② Solve RLC Ckt

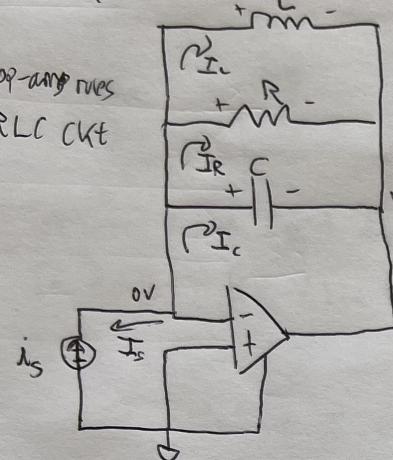

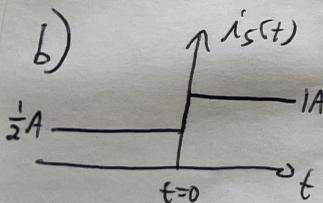a) Find diff. eq.

Goal: $\frac{d^2}{dt^2}V_o + A\frac{d}{dt}V_o + BV_o = 0$



Find initial conditions

- $V_o(0^+)$
- $\frac{d}{dt}V_o(0^+)$

c) damping?

α vs ω_0

Q?

$$Q = \frac{\omega_0}{2\alpha} = \# \text{ cycles}$$

Q/T = answer
Sine wave P.D.F.M.C

a) ① $V^+ = 0V = V^-$
 $i^- = 0A$
 $V_c = V_R = V_L = 0 - V_o = -V_o$

② $I_s + I_c + I_R + I_L = 0$

$$\begin{aligned} -i_s + C \frac{d}{dt}V_c + \frac{V_R}{R} + i_c(0) + \frac{1}{L} \int V_o dt &= 0 \\ -i_s - C \frac{d}{dt}V_o - \frac{V_o}{R} + i_c(0) + \frac{1}{L} \int V_o dt &= 0 \\ -\frac{d}{dt}i_s - C \frac{d^2}{dt^2}V_o - \frac{1}{R} \frac{d}{dt}V_o + 0 - \frac{1}{L}V_o &= 0 \end{aligned}$$

rearrange

$$\left. \begin{aligned} \frac{d^2}{dt^2}V_o + \underbrace{\frac{1}{RC}}_A \frac{d}{dt}V_o + \underbrace{\frac{1}{LC}}_B V_o &= -\frac{1}{C} \frac{d}{dt}i_s \\ C & \end{aligned} \right\}$$

@ 0^+

$$\begin{aligned} i_s &= i_c + i_R + i_L \\ i_c &= i_s - i_R - i_L \end{aligned}$$

b) ① $V_c = -V_o$


$V_c(0^-) = V_c(0^+)$

$V_L(0^-) = 0V = V_c(0^-) = V_c(0^+) = V_o(0^+) = 0V$


given $i_c(0^-)$
 $i_c(0^+)$

② $\frac{d}{dt}V_o(0^+) = \frac{d}{dt}V_c(0^+) = \frac{i_c(0^+)}{C} = \frac{i_s(0^+) - i_R(0^+) - i_L(0^+)}{C}$

$\frac{d}{dt}V_o(0^+)$

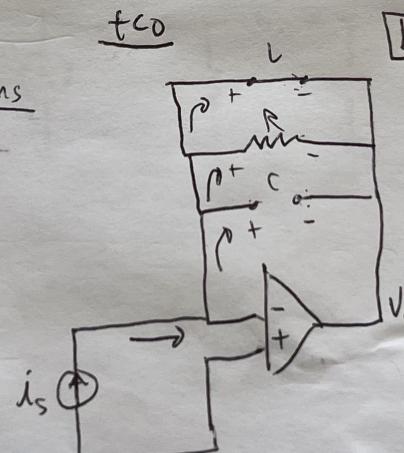

[HW9 P2]

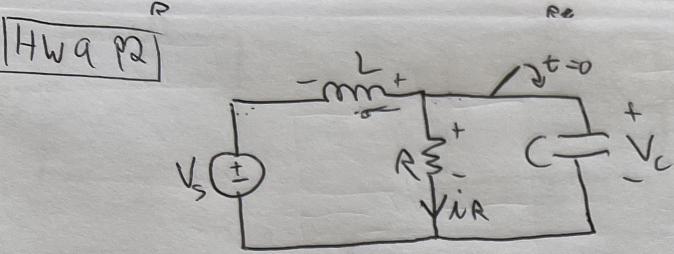

Goal: equation for $i_R(t)$, $t > 0$

$$V_c(t) = \text{~~~}$$

$$i_R(t) \cdot R = \text{~~~}$$

div by R

$$i_R(t) = \frac{V_c(t)}{R}$$

①

$$\frac{d}{dt} [i_L(0) + \frac{1}{L} \int (V_c - V_s) dt + \frac{V_c}{R} + C \frac{d}{dt} V_c] = 0$$


- Rearrange into std. form

- determine damping

- write solution

② Initial Conditions





$t < 0$

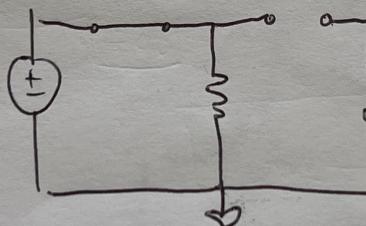

$$^o V_c(0^+) = V_c(0^-) = 1V$$

$$^o \frac{d}{dt} V_c(0^+) = 0,4V$$
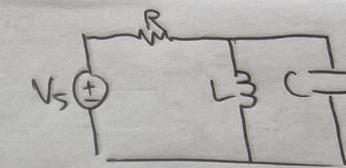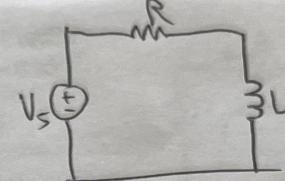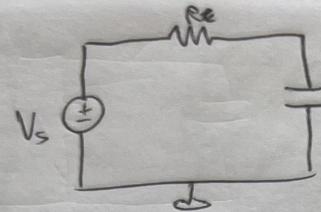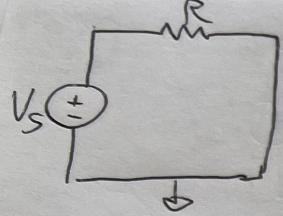
$$\frac{d}{dt} V_c(0^+) = \frac{i_c(0^+)}{C}$$



$$\rightarrow V_s = 1V \quad (t < 5s)$$


$$\rightarrow V_s = 5V \quad (t > 5s)$$

\boxed{R}

$$R = 10\Omega$$

$$V_R = V_s$$

$$I_R = \frac{V_s}{R}$$

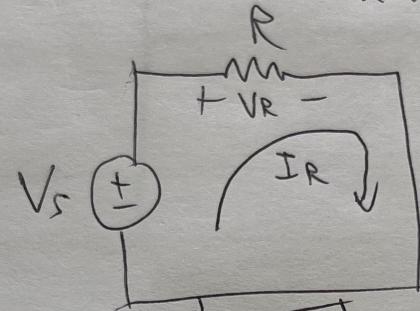

$$V_s = V_R$$

$$5V$$

V

$$t=0$$

Current


$$I_R = \frac{5}{10} A$$

$$\frac{1}{10} A$$


$$t=0$$

$\Rightarrow t$

RC

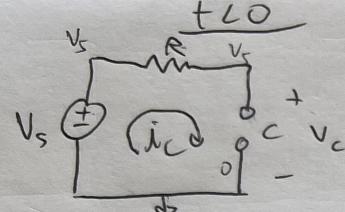


$$V_c(0^-) = V_s(0^-) = 1V$$

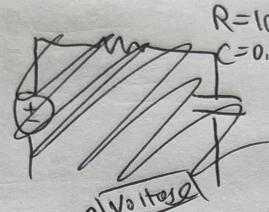

$$R = 10\Omega$$

$$C = 0.25F$$

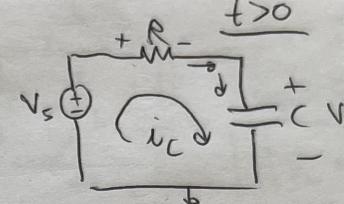

$$V_s \quad V_c$$

$$IR = i_c$$

$$\frac{V_s - V_c}{R} = C \frac{d}{dt} V_c$$



$$\frac{1}{R} V_c + \frac{1}{RC} V_c = \frac{V_s}{RC}$$

$$V_c(t) = V_s + k e^{-t/RC}$$

$$V_c(0^+) = V_c(0^-) = V_s(0^-) = 1V$$

$$k = -4$$


$$V_c(t) = 5 - 4 e^{-t/2.5}$$

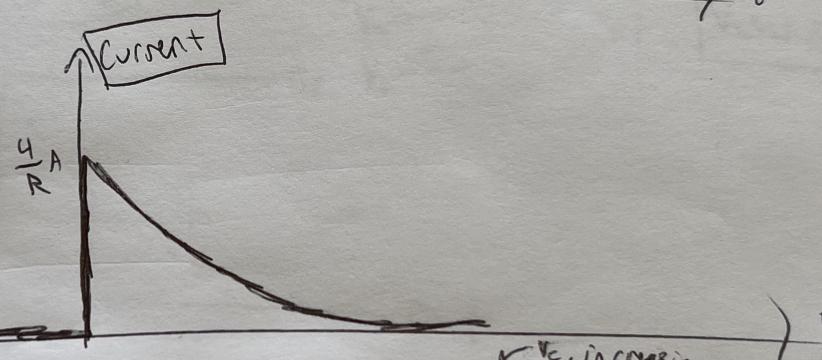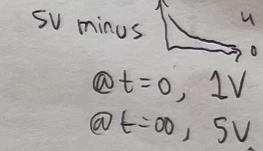

$$@ t=0^+, i_c = \frac{V_s - V_c}{R} = \frac{5 - 1}{R} = \frac{4}{R}$$

V_c increasing

RL

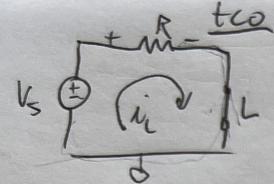


$$R = 10 \Omega$$

$$L = 10 \text{ H}$$

$$v_L(0^-) = i_L(0^+)$$
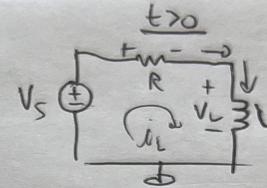
$$i_L(0^-) = \frac{V_s(0^-)}{R} = 0.1 \text{ A} = i_L(0^+)$$



$$IR = I_L$$

$$\frac{V_s - V_L}{R} = i_L(0) + \frac{1}{L} \int v_L dt$$

$$\frac{d}{dt} V_L + \frac{R}{L} V_L = 0$$



$$V_L(t) = 0 + K e^{-t \frac{R}{L}}$$

$V_L(0^+)$ ← use $i_L(0^+)$ to get →

$$V_L(0^+) = V_s - i_L(0^+) \cdot R = 5 - 0.1 \cdot 10 = 4 \text{ V}$$

$$K = 4$$


$$V_L(t) = 4 e^{-t}$$

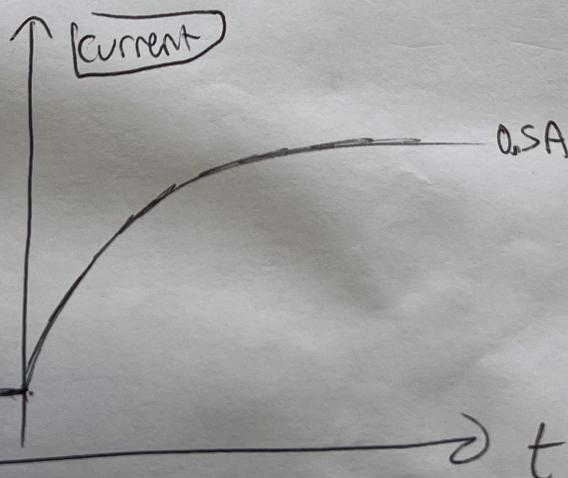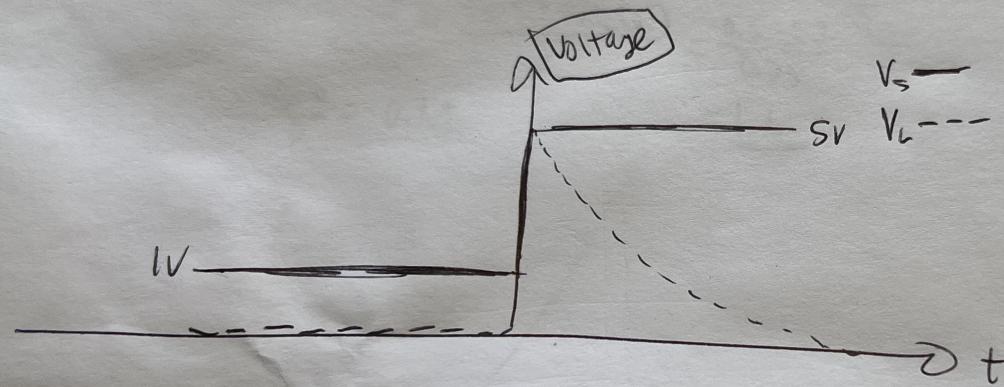

0.5A

$$i_L = \frac{V_s - V_L}{R} = \frac{5 - 4}{10} = 0.1 \text{ A}$$

RLC

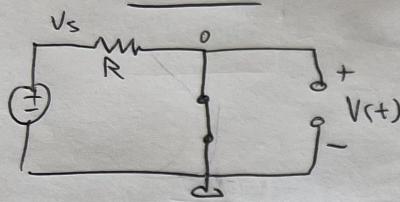

$$R = 10\Omega$$


$$L = 10H$$

$$C = 0.25F$$

$$\textcircled{1} \quad V_{c(0^+)} = \underline{0V} \quad \text{Inductor} \quad = V_{c(0^+)} = \underline{V_{c(0^+)}} \quad \checkmark$$

$$\textcircled{2} \quad \frac{d}{dt} V_{c(0^+)} = \frac{d}{dt} V_{c(0^+)} = \frac{i_c(0^+)}{C} = \frac{i_R(0^+) - i_L(0^+)}{C} = \frac{0.5 - 0.1}{0.25} = \underline{1.6}$$
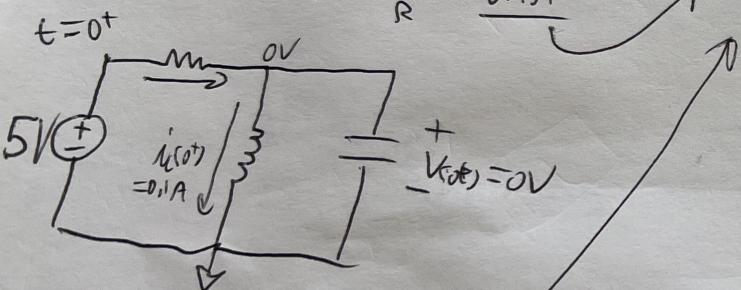
$$i_c(0^+) = i_L(0^-) = \frac{V_s - 0}{R} = \underline{0.1A}$$




$$i_R(0^+) = \frac{5 - 0}{R} = \underline{0.5A}$$

$$\textcircled{1} \quad V_{c(0^+)} = e^{-\alpha t_0} \left[A_1 \cos(\omega_d t_0) + A_2 \sin(\omega_d t_0) \right]$$

$$0 = A_1, \quad \underline{A_1}$$

$$\textcircled{2} \quad \frac{d}{dt} V_{c(t)} = 1.6 \quad 0.1 A_2 e^{-\alpha t_0} \left[2 \cos(\omega_d t_0) - \sin(\omega_d t_0) \right]$$

$$\boxed{A_2 = 8}$$

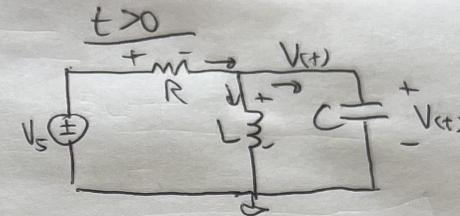

$$\frac{d}{dt} \left[\frac{V_s - V(t)}{R} \pm i(t) + \frac{1}{L} \int V(t) dt + C \frac{d}{dt} V(t) \right] = 0$$

rearrange

$$\left[\frac{d^2}{dt^2} V(t) + \frac{1}{RC} \frac{d}{dt} V(t) + \frac{1}{LC} V(t) = 0 \right]$$

$$2\alpha = A, \quad \omega_0^2 = B$$

$$\alpha = 0.1, \quad \omega_0 = 0.632$$

$\alpha < \omega_0 \rightarrow \text{Underdamped}$

$$V(t) = \frac{C}{B} e^{At} + e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$


$$A_1 = ? \quad A_2 = ?$$

$$V_{c(0^+)} = 0V$$


$$\frac{d}{dt} V_{c(0^+)} = 1.6$$

$$V(t) = e^{-0.1t} [8 \sin(\omega_d t)]$$

[RLC]

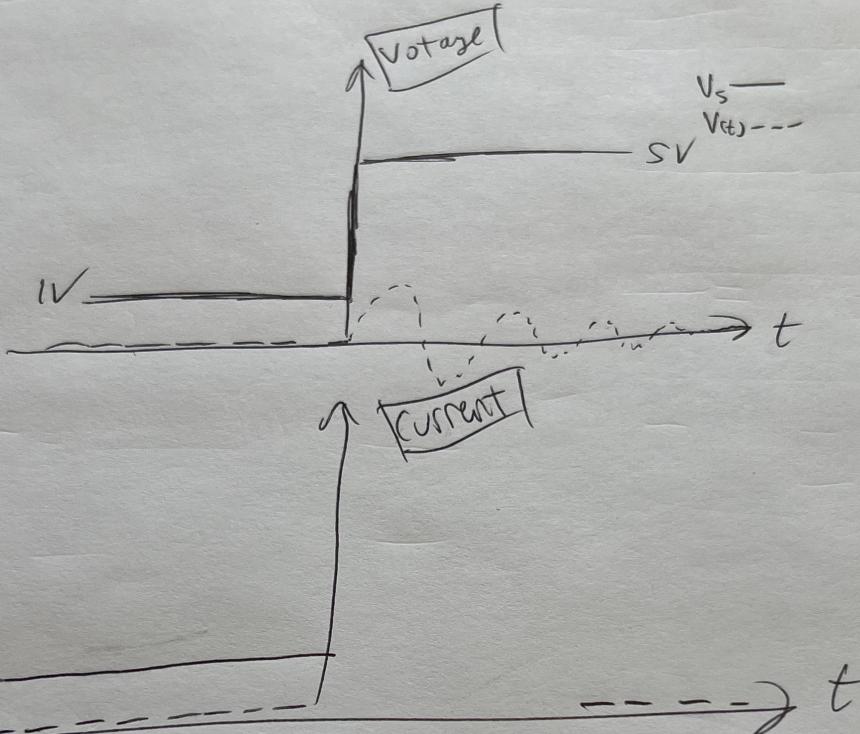
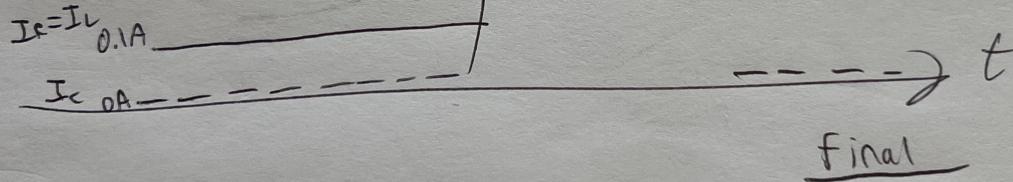
$$V(t) = e^{-0.1t} [8 \sin(\omega_0 t)]$$



final

$$I_c(\text{final}) = 0 \text{ A}$$

$$I_L = I_R(\text{final}) = \frac{5 \text{ V}}{10 \Omega} = 0.5 \text{ A}$$