

## Op-amps

1)  $G_{out} \geq$

$$V_{out} = \underline{\underline{m}}$$

2) know?

a)  $i^+ = i^- = 0A$


b)  $V^+ = V^-$  (not always 0V!)

c) Voltage/current source values /resistor

Make observations

3) Solve

-nodal, KVL/KCL, dividers, etc.

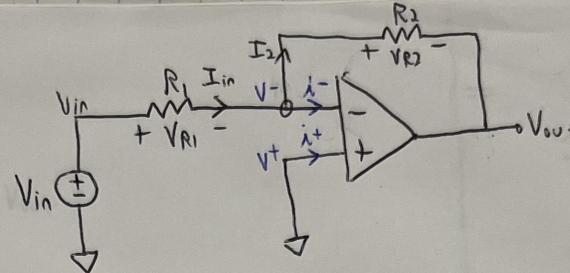

1)  $V_{out} = \underline{\underline{m}}$   
 $(V_{in}, R_1, R_2)$

2) a)  $i^+ = i^- = 0A$

KCL @  $V^-$

$$I_{in} = I_2 + i^-$$

$$\underline{\underline{I_{in} = I_2}}$$

b)  $V^+ = V^-$

$V^+ = 0V$  (given)

$\underline{\underline{V^- = 0V}}$

3) nodal at  $V^-$

$$I_{in} = I_2$$

$$\frac{V_{R1}}{R_1} = \frac{V_{R2}}{R_2}$$

$$\frac{V_{in} - V^-}{R_1} = \frac{V^- - V_{out}}{R_2}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_2}$$

$$\boxed{V_{out} = -\frac{R_2}{R_1} V_{in}}$$

OR

3) work backwards

-equation involving  $V_{out}$


$$I_2 = \frac{V^- - V_{out}}{R_2} = -\frac{V_{out}}{R_2}$$

$$I_1$$

$$\frac{V_{in} - V^-}{R_1} = -\frac{V_{out}}{R_2}$$

:
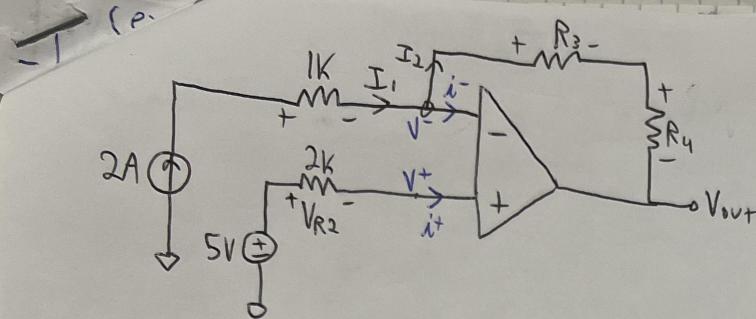
$$\boxed{V_{out} = -\frac{R_2}{R_1} V_{in}}$$



$$1) V_{out} = \underline{\underline{\quad}}$$

(source values  
R values)

$$2) \begin{cases} i^+ = 0 \\ i^- = 0 \end{cases}$$

KCL @  $V^-$

$$\begin{aligned} \rightarrow V_{R2} &= i^+ R_2 = 0V \\ \rightarrow V^+ &= 5 - V_{R2} \\ V^+ &= \cancel{5V} \\ \rightarrow V^- &= V^+ = \cancel{5V} \end{aligned}$$

3) nodal @  $V^-$

$$I_1 = I_2$$


$$2 = \frac{V^- - V_{out}}{R_3 + R_4}$$

$$2 = \frac{5 - V_{out}}{R_3 + R_4}$$

$$\boxed{V_{out} = 5 - 2(R_3 + R_4)}$$

Check  
units.
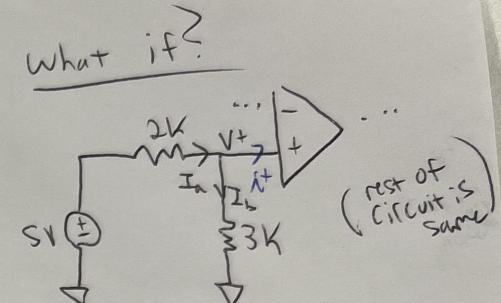
$$\begin{aligned} V &= V - A(\Omega) \\ V &= V - V \\ V &= V \end{aligned}$$




KCL @  $V^+$

$$\begin{aligned} I_a &= I_b + i^+ \\ I_a &= I_b \end{aligned}$$

Voltage divider applies here!

$$V^+ = 5 \cdot \frac{3k}{2k+3k} = \underline{\underline{3V}}$$

- Rest of analysis is unchanged.

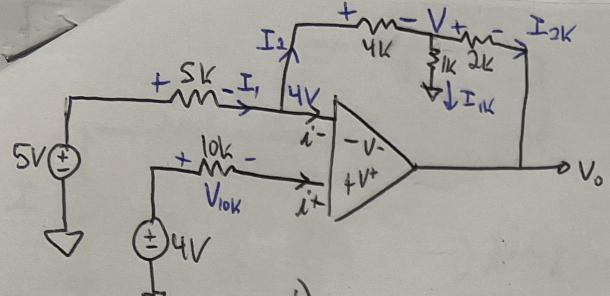

$$\begin{aligned} 1) \quad i^+ &= i^- = 0 \\ 2) \quad V^+ &= V^- \end{aligned}$$

①  $i^+ = 0$

$$V_{10k} = 0V$$

$$\hookrightarrow V^+ = 4V \rightarrow V^- = 4V$$

②  $\boxed{V^+ = V^-}$

③  $i^- = 0$   
 $I_1 = I_2$

$$I_1 = I_2 = \frac{5-4}{5k} = 0.2mA$$

$$4V - \frac{0.8}{0.2k \cdot 4k} V = V$$

$$\underline{3.2V = V}$$

goal ↓ known ↓ unknown ↓ but can find

$$I_{2k} = I_2 - I_{1k}$$

$$\textcircled{6} \quad I_{1k} = \frac{3.2 - 0}{1k} = 3.2mA$$


↓

$$I_{2k} = I_2 - I_{1k}$$

$$= 0.2mA - 3.2mA = -3mA$$

$$\frac{V - V_o}{2k} = I_{2k}$$
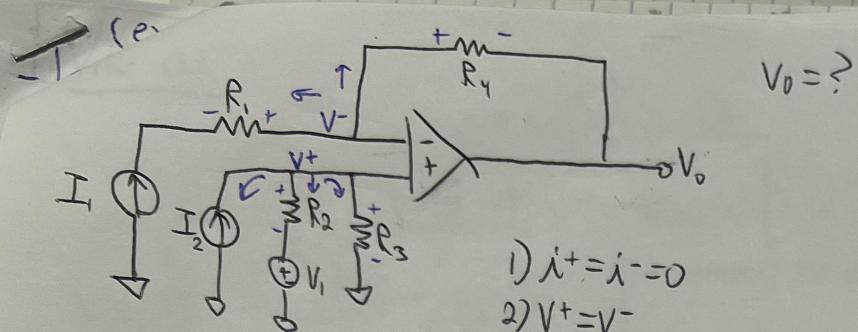
$$\begin{aligned} V_o &= V - 2k \cdot I_{2k} \\ &= 3.2V - 2k \cdot (-3mA) \\ &= 3.2V + 6 = \underline{9.2V} \end{aligned}$$



$V^-$

$$-I_1 + \frac{V^- - V_0}{R_4} = 0 \rightarrow V_0 = V^- - I_1 R_4$$

$$\frac{V^-}{R_4} - \frac{V_0}{R_4} = I_1 - \frac{V^-}{R_4}$$

$$-I_2 + \frac{V^+ - V_1}{R_2} + \frac{V^+ - 0}{R_3} = 0$$

$$V^+ \left( \frac{1}{R_2} + \frac{1}{R_3} \right) = I_2 + \frac{V_1}{R_2}$$

$$V^+ = \frac{I_2 + \frac{V_1}{R_2}}{\left( \frac{1}{R_2} + \frac{1}{R_3} \right)} = V^-$$

$$R_{eq} = \left( \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3}$$

$$V_0 = \frac{I_2 + \frac{V_1}{R_2}}{\left( \frac{1}{R_2} + \frac{1}{R_3} \right)} - I_1 R_4$$

$$= \frac{R_2 R_3 I_2 + R_3 V_1}{R_2 + R_3} - I_1 R_4$$

$$\frac{[A] + [A]}{\frac{1}{[A]}} - [V] \quad \checkmark$$

$$\frac{\cancel{A} + \cancel{V}}{\cancel{A}} - V \quad \checkmark$$