

(Always follow Associated Variable Convention)

$$i = \frac{1}{R} \cdot V \quad i = C \cdot \frac{dV}{dt}$$

(G)

$V \rightarrow$  Voltage drop across the Dev.  
or Branch Voltage

Current is proportional to  $\left\{ \begin{array}{l} \text{Voltage} \\ \text{voltage change} \end{array} \right\}$  for  $\left\{ \begin{array}{l} R \\ C \end{array} \right\}$

Given Current. to find Voltage (Integral form)


$$i_{(0)} \quad \boxed{\frac{1}{C} \quad V(t)} \quad V_{(+)} = C \cdot \frac{dV}{dt}$$

$$\int_0^t i_{(0)} dt = C \cdot \int_0^t \frac{dV}{dt} dt = C(V_{(+)} - V_{(0)})$$

$$\boxed{V_{(+)} = V_{(0)} + \frac{1}{C} \int_0^t i_{(0)} dt}$$

E.g. 1  $C = \alpha F$ , stores  $q_{(0)} = 2C$ .

Input a current:

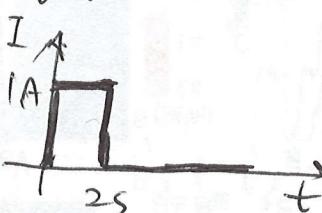

What is  $V_{(+)}$ ?

For  $0 < t < 2$

For  $t > 2$

$$V_{(+)} = V_0 + \frac{1}{C} \int_0^t 1A dt$$

$$= \frac{Q_{(0)}}{C} + \frac{1}{C} \int_0^t 1A dt$$

$$= \frac{Q_{(0)}}{C} + \frac{1}{C} \cdot t$$


$$= \frac{2}{0.1} + \frac{1}{0.1} \cdot t = 20 + 10t$$

$$V_{(+)} = \frac{Q_{(0)}}{C} + \frac{1}{C} \int_0^2 1A dt + \frac{1}{C} \int_2^t 0A dt$$


$$= \frac{Q_{(0)}}{C} + \frac{1}{C} (2 - 0)$$

$$= 20V + 20V$$

$$= 40V$$

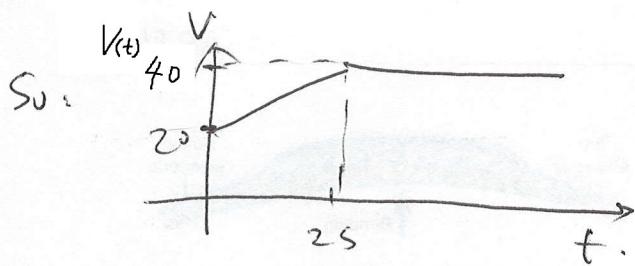

## 2. Energy stored in a capacitor.

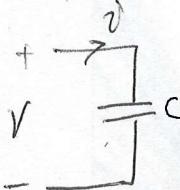  $W = \int_0^t P(t) dt = \int_0^t i \cdot V dt$  (Work done to any circuit)

$$= \int_0^t C \cdot \frac{dV}{dt} \cdot V \cdot dt = C \int_0^t V \cdot \frac{dV}{dt} \cdot dt$$


$$= C \int_{V(0)}^{V(t)} V \cdot dV = \frac{C}{2} (V(t)^2 - V(0)^2)$$

Assume Initially,  $V(0) = 0$

S<sub>0</sub>:  $E = C \cdot \frac{V^2}{2} = \frac{Q^2}{2C}$

[e.g.] 100 μF,  $V = 200 V$ :  $E = \frac{1}{2} \times (200 V)^2 \times 10^{-4} F = 2 J$ .
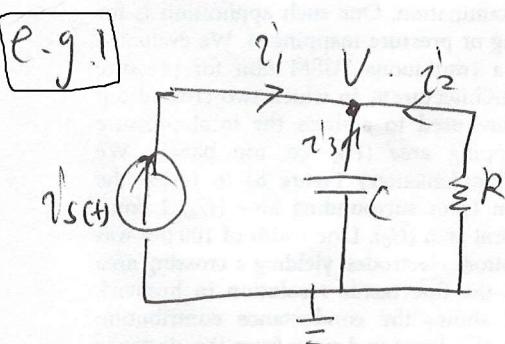
## 3. Differential equation for RC circuit.




KCL:  $i_1 + i_2 + i_3 = 0$

$$i_s(t) + \frac{0-V}{R} + C \cdot \frac{d(0-V)}{dt} = 0$$

$$i_s(t) - \frac{V}{R} - C \cdot \frac{dV}{dt} = 0$$

e.g.2

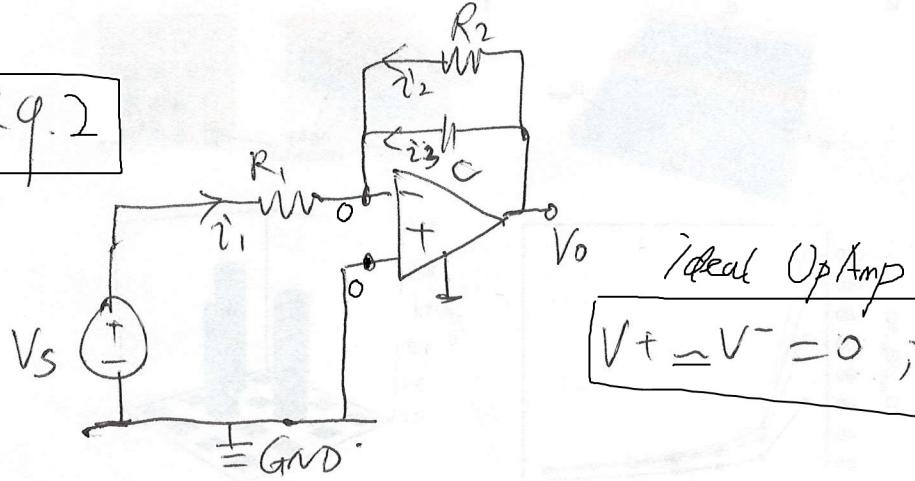

$$V_+ = V_- = 0 ; \quad i^+ = i^- = 0$$

$$KCL: \quad i_1 + i_2 + i_3 = 0$$

$$\frac{V_s - 0}{R_1} + \frac{V_o - 0}{R_2} + C \cdot \frac{d(V_o - 0)}{dt} = 0$$


$$\frac{dV_o}{dt} + \frac{V_o}{R_2 \cdot C} = -\frac{V_s}{R_1 \cdot C}$$

A special case:

$$If \ R_2 \rightarrow \infty.$$

$$\frac{dV_o}{dt} = -\frac{V_s}{R_1 \cdot C} \Rightarrow \text{Integrator.}$$

e.g.3

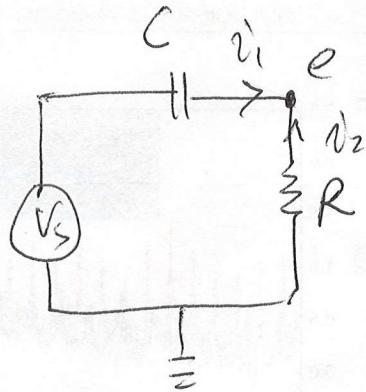

.KCL:

$$i_1 + i_2 = 0$$

$$\frac{0 - e}{R} + C \cdot \frac{d(V_s - e)}{dt} = 0$$