

# ECE124: Discussion

Discussion #7

Yeonsik Noh, PhD

# Minimization via K-Maps


To obtain minimized SOP expression for a Boolean function F...

- Step1: Translate truth table to K-map
- Step2: Cover all 1's in the smallest number of largest blocks
- Step3: Extract one product term for each block
- Step4: Sum of extracted product terms=minimized SOP expression!

### 3.1 Simplify the following Boolean functions, using three-variable K-maps:

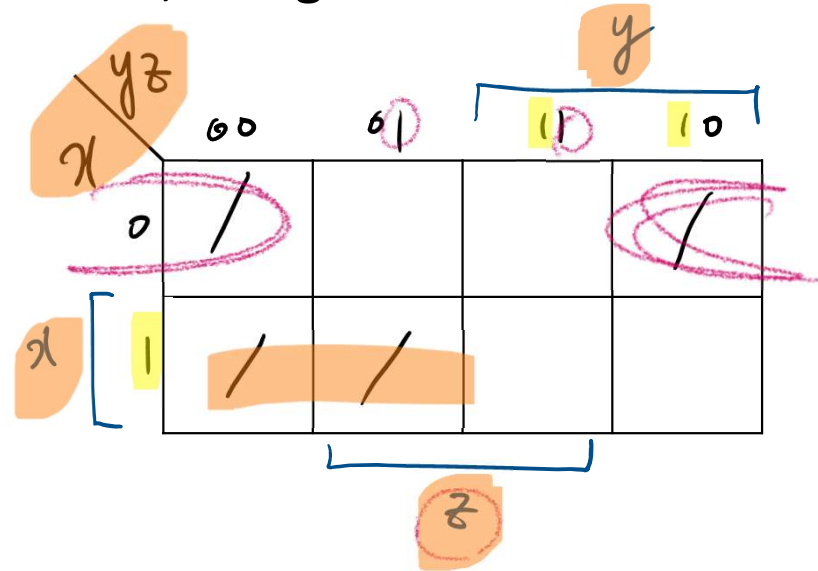(a)  $F(x, y, z) = \sum(0, 2, 4, 5)$


$$F = \text{orange square} + \text{pink circle}$$
$$= x \cdot y' + x'z'$$



3.1 Simplify the following Boolean functions, using three-variable K-maps:


(b)  $F(x, y, z) = \sum (0, 2, 4, 5, 6)$

$$F = z' + xy'$$

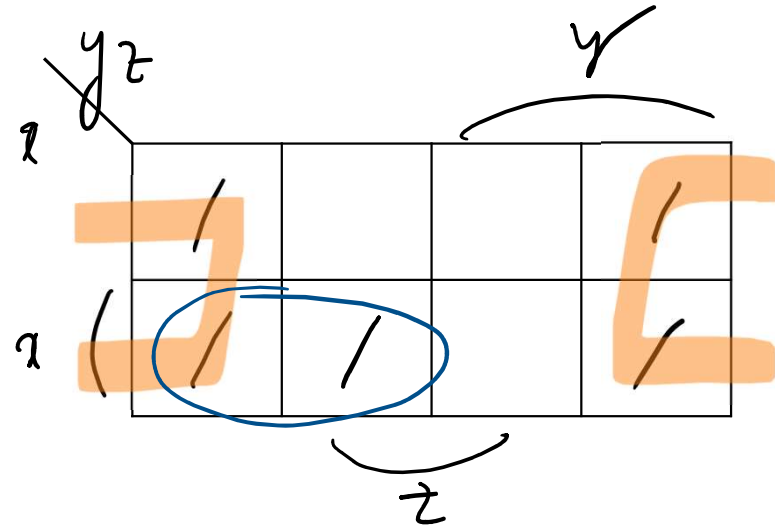

3.1 Simplify the following Boolean functions, using three-variable K-maps:

(c)  $F(x, y, z) = \sum (0, 1, 2, 3, 5)$

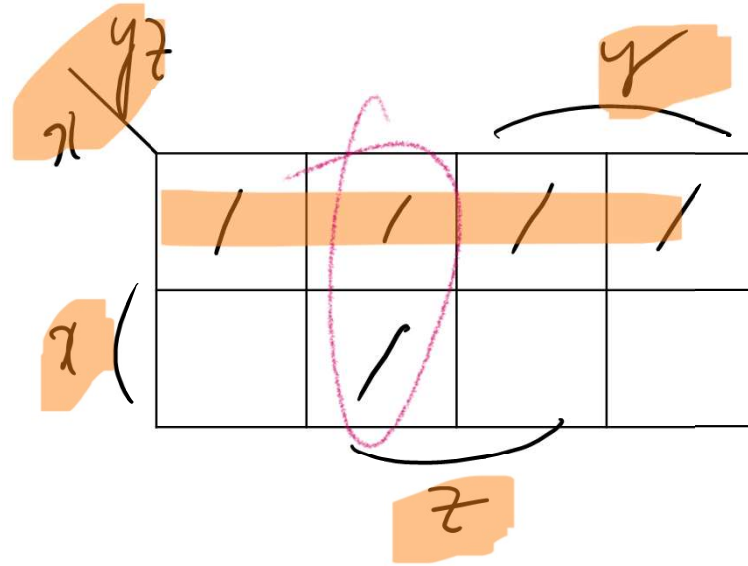


$F = x' + y'z$

3.1 Simplify the following Boolean functions, using three-variable K-maps:

(d)  $F(x, y, z) = \sum (1, 2, 3, 7)$

$$F = x'z + yz + x'y$$

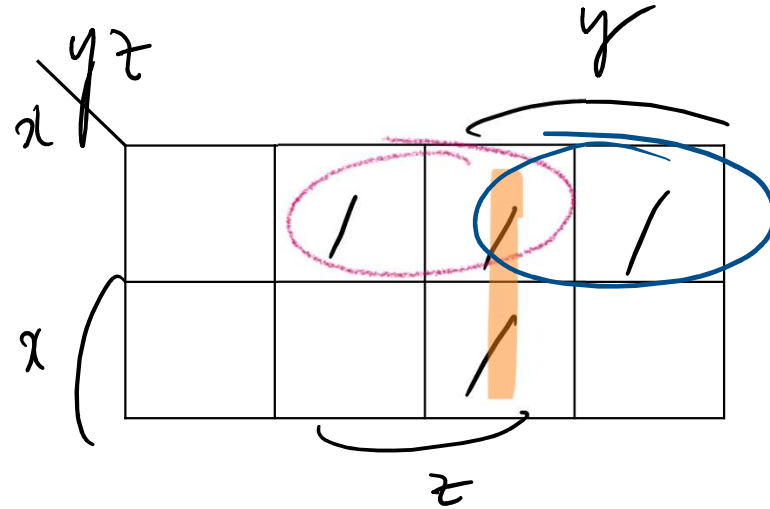

- 1(b). Boolean expression for F.

$u$   $x$   $y$   $z$

	$m_1$		$m_2$
$m_4$		$m_7$	
	$m_3$		$m_6$
$m_8$		$m_5$	

\* All minterms are exclusive.

$$F = m_1 + m_2 + m_4 + m_7 + m_8 + m_{11} + m_{13} + m_{14}$$

$$= u'x'y'z + u'x'yz' + u'xy'z' + u'xyz + ux'y'z' + ux'yz + uxy'z + uxyz'$$

$$\begin{array}{cccccccc} 0001_{(1)} & 0010_{(2)} & 0100_{(4)} & 0111_{(7)} & 1000_{(8)} & 1011_{(11)} & 1101_{(13)} & 1110_{(14)} \\ \hline = 1_{(10)} & = 2_{(10)} & = 4_{(10)} & = 7_{(10)} & = 8_{(10)} & = 11_{(10)} & = 13_{(10)} & = 14_{(10)} \end{array}$$

① L

$$= u'x'(y'z + yz') + u'x(y'z' + yz) + ux'(y'z' + yz) + ux(y'z + yz')$$

② L

$$= (u'x' + ux)(y'z + yz') + (u'x + ux')(y'z' + yz)$$

③ L

$$= \frac{(u \oplus x)'}{A'} \frac{(y \oplus z)}{B} + \frac{(u \oplus x)}{A} \frac{(y \oplus z)'}{B'}$$

$$= (u \oplus x) \oplus (y \oplus z)$$

$$= \underline{u \oplus x \oplus y \oplus z}$$

\*  $A \oplus B = A'B + AB'$

$(A \oplus B)' = A'B' + AB$

$= A \odot B$


\*  $A'B' + AB \neq 1$

if,  $A=B \rightarrow A'B' + AB = 1$


- 1(c). Draw a logic diagram for F.

$$F = x \oplus a \oplus y \oplus z$$


i)

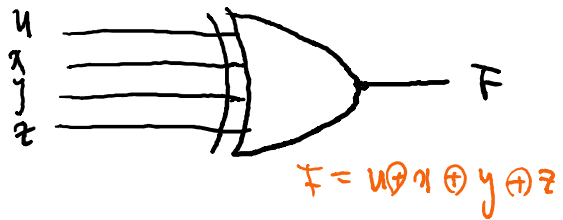


ii)

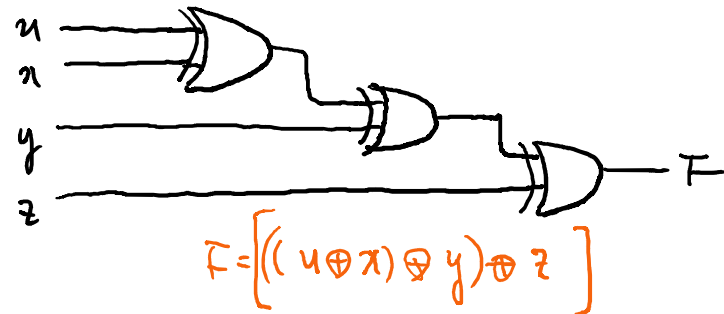

iii)

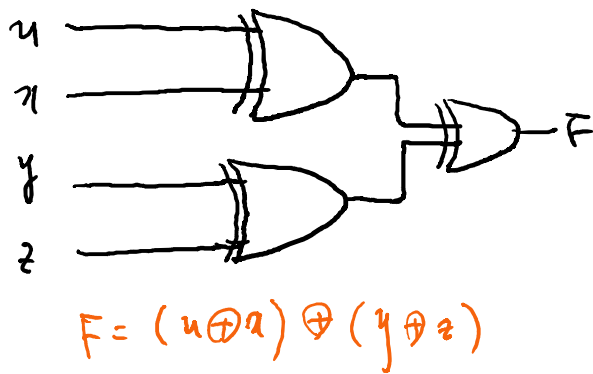

iv)

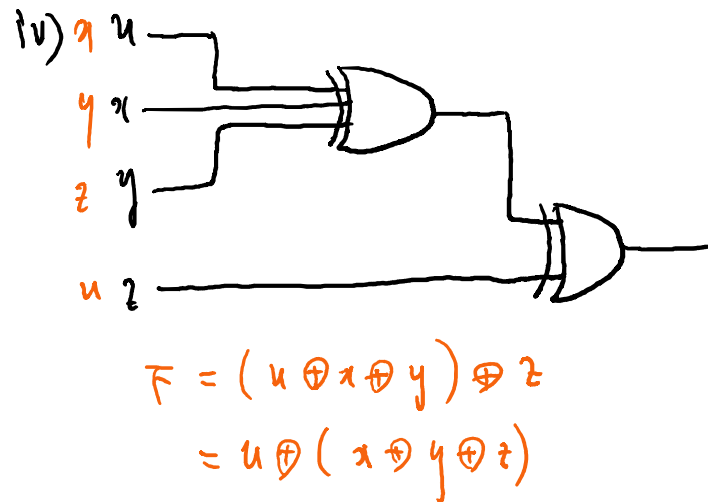



- 1) Consider the Boolean function:  $F(A, B, C, D) = AB + B'C + ACD + ABD' + ACD'$
- 2) Extract a minimized Boolean expression for F using the Karnaugh map of 1).
- 3) Simplify the Boolean expression F and Compare it with the minimized Boolean expression of 2)

		C			
		D			
		00	01	11	10
A	AB			/	/
	00			/	/
	01				
	11	/	/	/	/
10				/	/
				/	/

$$F = AB + B'C$$

$$\begin{aligned}
 F &= AB + B'C + ACD + ABD' + ACD' \\
 &= AB(\cancel{1 + D'}) + AC(\cancel{D + D'}) + B'C \\
 &= AB + AC + B'C
 \end{aligned}$$

$$\begin{array}{ccc}
 ABCD & ABCD & AB'CD \\
 \begin{array}{c} 1100 \\ 1101 \\ 1110 \\ 1111 \end{array} & \begin{array}{c} 1010 \\ 1011 \\ 1101 \\ 1111 \end{array} & \begin{array}{c} 0010 \\ 0011 \\ 0101 \\ 0111 \end{array}
 \end{array}$$

$$= AB + (B + B')AC + B'C$$

$$= AB + ABC + AB'C + B'C$$

$$= \cancel{AB(1 + C)} + \cancel{B'C(A + 1)}$$

\* Consensus Th.

$$\cancel{AB + AC + B'C}$$

$$\cancel{(A + B) \cdot (A + C) \cdot (B' + C)}$$


$$\cancel{x'y + yz + xz}$$

- 2(a). Consider the Karnaugh map for F together with the don't care conditions, d. Show the Karnaugh map for G.

$$F(u, x, y, z) = \sum(0, 2, 5, 7, 10, 15)$$

$$d(u, x, y, z) = \sum(1, 3, 4, 6, 11, 13)$$

$$G(u, x, y, z) = F + d$$

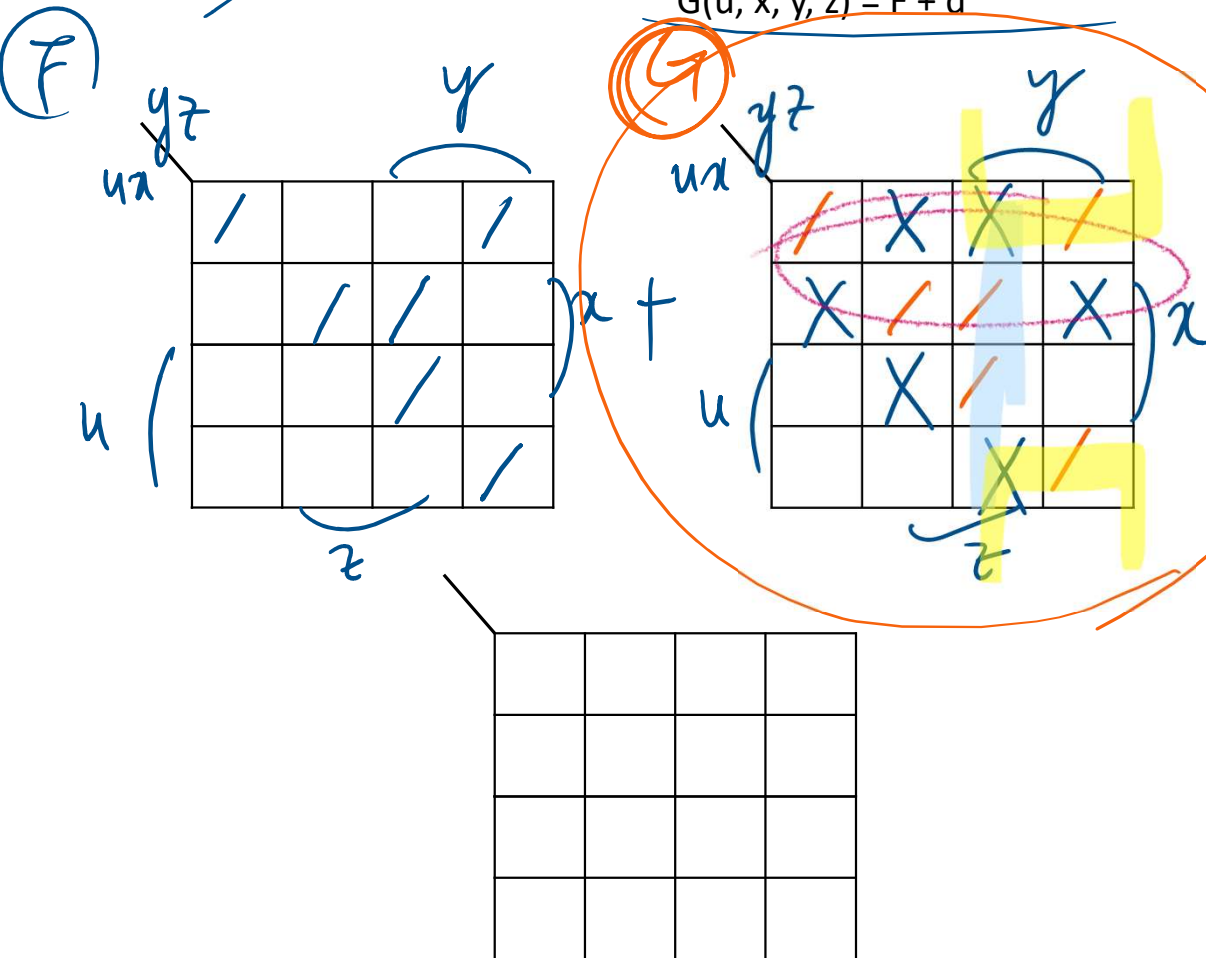


$$F = u' + yz + x'y$$

3.15 Simplify the following Boolean function F, together with the don't care conditions d, and then express the simplified function in sum-of-minterms form:

(d)  $F(A, B, C, D) = \Sigma(4, 12, 7, 2, 10)$



$d(A, B, C, D) = \Sigma(0, 6, 8)$

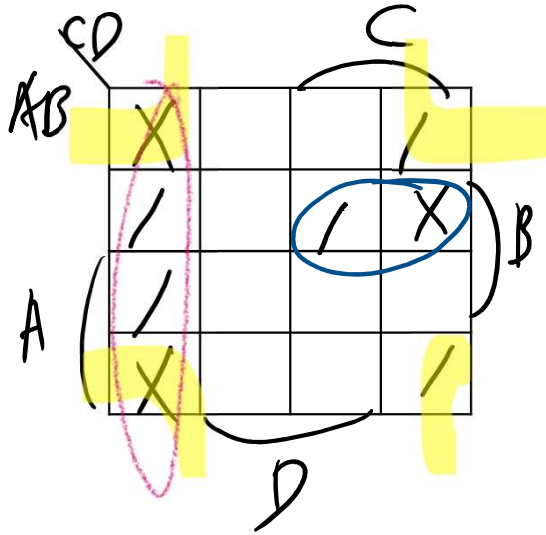


$\text{---} + \text{---} + \text{---}$

$$F = B'D' + C'D' + A'BC$$

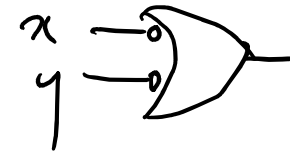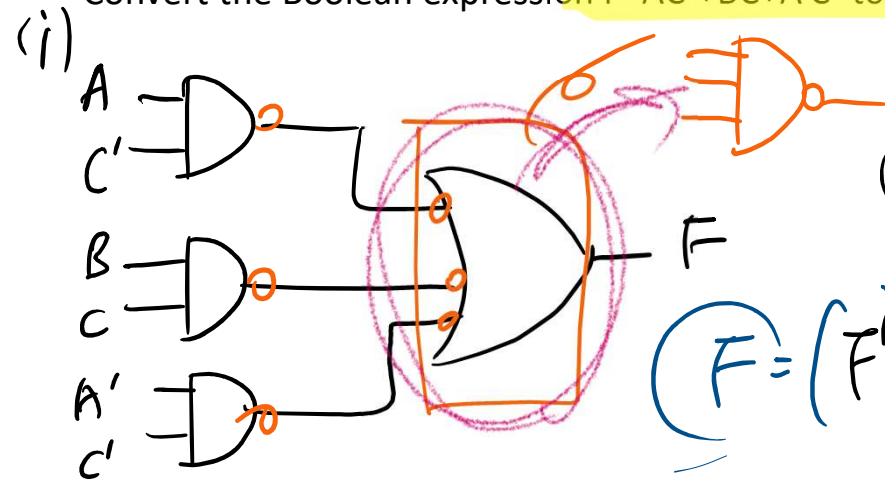- Convert the Boolean expression  $F = AC' + BC + A'C'$  to only NAND gates.



$$x' + y'$$

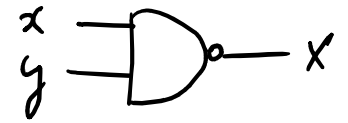


$$(x \cdot y)'$$

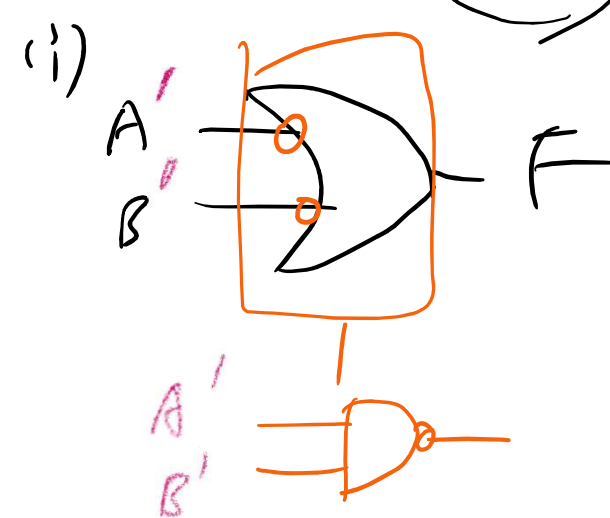(ii)  $F = AC' + BC + A'C'$


$$F = (F')' = (AC' + BC + A'C')' = \left( (A \cdot C')' \cdot (B \cdot C)' \cdot (A' \cdot C')' \right)'$$

- Draw a logic diagram for  $F = A + B$  using only NAND gates.





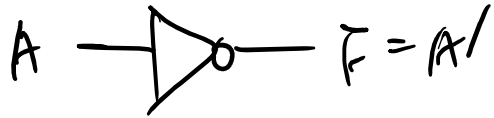
(ii)  $F' = (A + B)'$   
 $F = (A' \cdot B')'$

- Draw a logic diagram for  $F=A'$  using only NOR gates.



$x$	$y$	NOR	NAND
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0

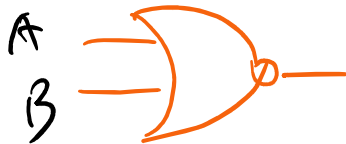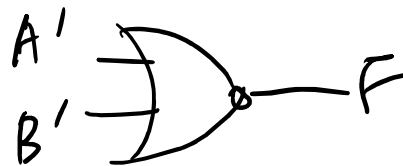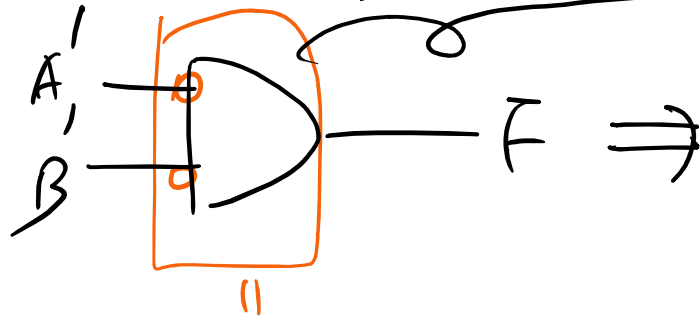- Draw a logic diagram for  $F=AB$  using only NOR gates.



$$A' + B' = (AB)'$$

$$(ii) \quad F = AB$$

$$F' = (AB)' = A' + B'$$

$$F = (A' + B')'$$