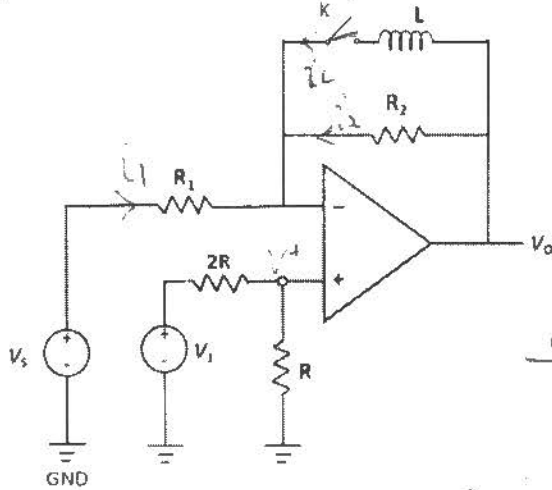


## Homework 8

## Problem 1 (4 pt)

Find the differential equation for  $v_o$  in the opamp circuit below for  $t > 0$  when the switch  $K$  is closed (You don't need to solve the equation). Assume the opamp is ideal with infinite gain.



① For  $V^+$ :

Voltage Divider:  $V^+ = \frac{R}{R+2R} \times V_1 = \frac{1}{3} V_1 = V^-$

② KCL @  $V^-$ :

$$i_1 + i_2 + i_L = 0$$

$$\frac{V_s - V^+}{R_1} + \frac{V_s - V^+}{R_2} + i_L(t^+) + \frac{1}{L} \int_0^t (V_s - V^+) dt = 0$$

$$\frac{1}{R_2} \frac{dv_o}{dt} + \frac{1}{L} (V_s - V^+) = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \frac{dV^+}{dt} - \frac{1}{R_1} \frac{dV_s}{dt}$$

$$\frac{dv_o}{dt} + \frac{R_2}{L} \cdot v_o = \left( \frac{R_1 + R_2}{R_1} \right) \cdot \frac{dV^+}{dt} - \frac{R_2}{R_1} \frac{dV_s}{dt} + \frac{R_2}{L} \cdot V^+$$


Suppose.  $V_s, V_1$  are time independent.

$$\frac{dv_o}{dt} + \frac{R_2}{L} \cdot v_o = \frac{R_2}{L} \cdot V^+$$

$$\frac{dv_o}{dt} + \frac{R_2}{L} \cdot v_o = \frac{R_2}{L} \cdot \frac{1}{3} V_1$$

$$\frac{dv_o}{dt} + \frac{R_2}{L} \cdot v_o = \frac{1}{3} \cdot \frac{R_2 \cdot V_1}{L}$$

Problem 2:

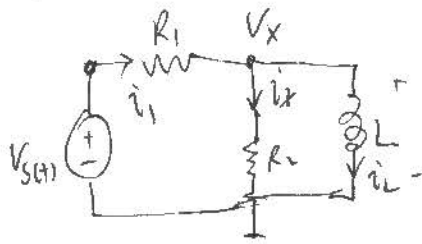

KCL @  $V_X$ :

$$i_1 - i_L - i_X = 0$$

$$\frac{V_S - V_X}{R_1} - (i_L(t) + \frac{1}{L} \int_0^t (V_X - 0) dt) - \frac{V_X - 0}{R_2} = 0$$

Differential:

$$\frac{1}{R_1} \frac{d(V_S - V_X)}{dt} - \frac{1}{L} V_X - \frac{1}{R_2} \frac{dV_X}{dt} = 0$$

$$- \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \frac{dV_X}{dt} + \frac{1}{R_1} \frac{dV_S}{dt} - \frac{1}{L} V_X = 0$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \frac{dV_X}{dt} - \frac{1}{R_1} \frac{dV_S}{dt} + \frac{1}{L} V_X = 0$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right) \cdot \frac{dV_X}{dt} + \frac{1}{L} \cdot V_X = \frac{1}{R_1} \frac{dV_S}{dt}$$

$$\frac{dV_X}{dt} + \frac{R_1 R_2}{L(R_1 + R_2)} \cdot V_X = \frac{R_2}{R_1 + R_2} \cdot \frac{dV_S}{dt}$$


Since:  $i_X = \frac{V_X}{R_2} \Rightarrow \underline{V_X = i_X \cdot R_2}$

$$\frac{d(i_X \cdot R_2)}{dt} + \frac{R_1 R_2}{L(R_1 + R_2)} \cdot i_X \cdot R_2 = \frac{R_2}{R_1 + R_2} \cdot \frac{dV_S}{dt}$$

$$\Rightarrow \frac{di_X}{dt} + \frac{R_1 R_2}{L(R_1 + R_2)} \cdot i_X = \frac{1}{R_1 + R_2} \cdot \frac{dV_S}{dt}$$

# Problem 3

$V_{LH}$  when  $t > 0$

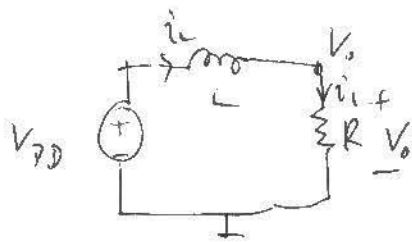

KCL:  $i_L - i_1 = 0$

$$i_L(0^+) + \frac{1}{L} \int_0^t (V_{DD} - V_o) dt - \frac{V_o - 0}{R} = 0$$

Differential:

$$\frac{1}{L} (V_{DD} - V_o) - \frac{dV_o}{dt} \cdot \frac{1}{R} = 0$$

$$\Rightarrow \frac{dV_o}{dt} + \frac{R}{L} \cdot V_o = \frac{R}{L} \cdot V_{DD}$$


$$V_o(t) = V_{DD} + k \cdot e^{-\frac{R}{L} \cdot t}$$

find initial condition:  $V_o(0^+)$ : (relate  $V_o(0^+)$  to  $i_L(0^+)$ )

$$i_1(0^+) = i_L(0^+)$$

$$\frac{V_o(0^+)}{R} = i_L(0^+) \Rightarrow V_o(0^+) = i_L(0^+) \cdot R = i_L(0^-) \cdot R$$

find  $i_L(0^-)$ : (when  $t < 0$ ;) .

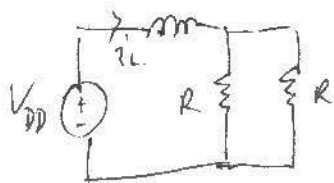


For steady state: inductor acts like short-circuit

$$i_{L(0^-)} = \frac{V_{DD}}{\frac{R}{2}} = \frac{2V_{DD}}{R}$$

$$\text{So: } V_o(0^+) = \frac{2V_{DD}}{R} \times R = 2V_{DD}$$


$$V_o(0^+) = 2V_{DD} = V_{DD} + k \Rightarrow k = V_{DD}$$

$$\text{So: } V_o(t) = V_{DD} + V_{DD} \cdot e^{-\frac{R}{L} \cdot t}$$

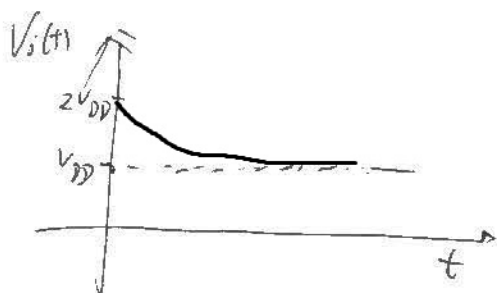

Problem 4

At  $t > 0$ .

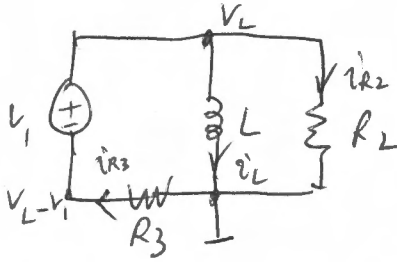

KCL:

$$-\dot{i}_L - \dot{i}_{R2} + \dot{i}_{R3} = 0 \quad \text{--- (1)}$$

$$-\dot{i}_L(t) - \frac{1}{L} \int_0^t V_L dt - \frac{V_L}{R_2} + \frac{0 - (V_L - V_1)}{R_3} = 0$$

$$\text{diff: } -\frac{1}{L} V_L - \frac{1}{R_2} \frac{dV_L}{dt} - \frac{1}{R_3} \frac{dV_L}{dt} = 0$$

$$\left(\frac{1}{R_2} + \frac{1}{R_3}\right) \frac{dV_L}{dt} + \frac{1}{L} V_L = 0$$

$$\left(\frac{1}{4k} + \frac{1}{4k}\right) \frac{dV_L}{dt} + \frac{1}{2mH} V_L = 0$$

$$\frac{1}{2k} \frac{dV_L}{dt} + \frac{1}{2mH} V_L = 0 \Rightarrow \frac{dV_L}{dt} + 10^6 V_L = 0$$

$$V_L(t) = k \cdot e^{-10^6 t}$$

find:  $V_L(0^+)$ :


from (1) we have:  $i_L(0^+) = i_{R3}(0^+) - i_{R2}(0^+) = \frac{0 - (V_L(0^+) - V_1)}{R_3} - \frac{V_L(0^+)}{R_2}$

$$i_L(0^+) = i_L(0^-)$$

$$= -\left(\frac{1}{R_3} + \frac{1}{R_2}\right) V_L(0^+) + \frac{V_1}{R_3}$$

②  $t = 0^-$  (steady state)
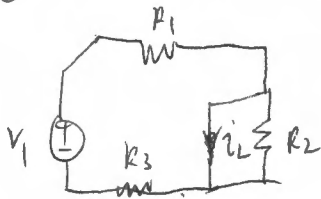
$$= -\frac{1}{2k} V_L(0^+) + \frac{3}{4k}$$



$$i_L(0^-) = \frac{V_1}{R_1 + R_3} = \frac{3}{6k\Omega} = 0.5 \text{ mA}$$

$$\text{So: } 0.5 \text{ mA} = -\frac{1}{2k} V_L(0^+) + \frac{3}{4k} \Rightarrow 2 = -2 V_L(0^+) + 3 \Rightarrow V_L(0^+) = \frac{1}{2} \text{ (V)}$$

$$\text{So: } V_L(0^+) = k = \frac{1}{2}$$

$$\text{So } V_L(t) = \frac{1}{2} \cdot e^{-10^6 t}$$